

DESIGN OF ANALOG FILTERS

Passive, Active RC, and Switched Capacitor

ROLF SCHAUMANN

Department of Electrical Engineering
Portland State University

M. S. GHAUSI

Department of Electrical Engineering
University of California at Davis

KENNETH R. LAKER

Department of Electrical Engineering
University of Pennsylvania



Prentice-Hall International, Inc.

DESIGN OF ANALOG FILTERS

PASSIVE, ACTIVE RC, AND SWITCHED CAPACITOR



Prentice-Hall International Editions

**ROLF SCHAUMANN
MOHAMMED S. GHAUSI
KENNETH R. LAKER**

Contents

Preface xi

Fundamental Concepts and Tools for the Design of Linear Analog Filters

ONE

- 1.1 Introduction 1
- 1.2 Classification of Systems 5
 - 1.2.1 Linear and Nonlinear Systems 5
 - 1.2.2 Continuous-Time and Discrete-Time or Sampled-Data Systems 6
 - 1.2.3 Time-Invariant and Time-Varying Systems 6
- 1.3 Representations of Linear Continuous-Time-Invariant Systems 8
 - 1.3.1 Frequency-Domain Concepts 9
 - 1.3.2 Time-Domain Concepts 15
- 1.4 Normalization 22
- 1.5 Types of Filters 24
 - 1.5.1 Filter Magnitude Specifications 25
 - 1.5.2 Filter Phase or Delay Specifications 27
 - 1.5.3 Second-Order Filters 30
- 1.6 Approximation Methods 36
 - 1.6.1 The Lowpass Magnitude Approximation 37
 - 1.6.2 Frequency Transformations 56
- 1.7 Summary 64
 - Problems 64

This edition may be sold only in those countries to which it is consigned by Prentice-Hall International. It is not to be re-exported and it is not for sale in the U.S.A., Mexico, or Canada.

Material in this book adapted in part from MODERN FILTER DESIGN by M. S. Ghausi and K. R. Laker. Prentice Hall 1981.

M. S. Ghausi/K. R. Laker, MODERN FILTER DESIGN: Active RC and Switched Capacitor © 1981
Figures 1-1, 1-6, 1-7, 1-8, 1-9, 1-14, 1-26, 1-27, 1-28, 1-29, 1-30, 1-32, 1-33, 1-36, 1-37, 1-38, 2-3, 5-14, 5-16, 5-25, P1-3, B-1 and tables 1-1, 1-3, B1, B2, B3, B4, and B5 adapted by permission of Prentice Hall, Inc., Englewood Cliffs, NJ.



© 1990 by Prentice-Hall, Inc.
A Division of Simon & Schuster
Englewood Cliffs, New Jersey 07632

All rights reserved. No part of this book may be reproduced, in any form or by any means, without permission in writing from the publisher.

Printed in the Republic of Singapore.

10 9 8 7 6 5 4 3 2 1

ISBN 0-13-201591-9

Prentice-Hall International (UK) Limited, London
Prentice-Hall of Australia Pty. Limited, Sydney
Prentice-Hall Canada Inc., Toronto
Prentice-Hall Hispanoamericana, S.A., Mexico
Prentice-Hall of India Private Limited, New Delhi
Prentice-Hall of Japan, Inc., Tokyo
Simon & Schuster Asia Pte. Ltd., Singapore
Editora Prentice-Hall do Brasil, Ltda., Rio de Janeiro
Prentice-Hall, Inc., Englewood Cliffs, New Jersey

- 4.2.2 Real Operational Amplifiers 201
- 4.2.3 Transconductance Amplifiers 212
- 4.3 Active Building Blocks Using Op Amps 216
 - 4.3.1 Summers and Related Circuits 218
 - 4.3.2 Integrators 223
 - 4.3.3 Gyration and Imittance Converters 228
- 4.4 Active Building Blocks Using Transconductances 235
- 4.5 Summary 240
- Problems 241

Second-Order Active Filter Sections

FIVE 249

- 5.1 Introduction 249
- 5.2 Single-Amplifier Biquad Configurations 250
 - 5.2.1 Generation of Transfer Function Zeros 251
 - 5.2.2 Generation of Transfer Function Poles 253
 - 5.2.3 Sensitivity Considerations and Optimization 261
 - 5.2.4 The Effects of Finite Op Amp Bandwidth 269
 - 5.2.5 Passive RC Twoports 273
- 5.3 Multiplier Circuits 285
 - 5.3.1 Biquads Using a Composite Amplifier 286
 - 5.3.2 Biquads Based on the General Impedance Converter 291
 - 5.3.3 Biquads Using Three Op Amps 298
- 5.4 Circuits Using Transconductances 308
- 5.5 Summary 313
- Problems 314

The Design of High-Order Filters

SIX 319

- 6.1 Introduction 319
- 6.2 Cascade Realizations 321
 - 6.2.1 Pole-Zero Pairing 324
 - 6.2.2 Section Ordering 330
 - 6.2.3 Gain Assignment 332
 - 6.2.4 An Exact Approach to Dynamic Range Optimization 336
- 6.3 Multiple-Loop Feedback Realizations 339
 - 6.3.1 The FLF Topology 340

The Design of LC Filters

TWO

- 2.1 Introduction 71
- 2.2 Realization of LC Imittance Functions 73
- 2.3 Derivation of the Twoport Parameters of LC Filters 80
- 2.4 Realization of LC Ladders 86
- 2.5 Realization of LC Allpass Circuits 111
- 2.6 Summary 116
- Problems 117

Sensitivity

THREE

- 3.1 Introduction 124
- 3.2 Single-Parameter Sensitivity 130
 - 3.2.1 Sensitivity Invariants 131
 - 3.2.2 The Gain-Sensitivity Product 134
 - 3.2.3 Transfer Function Sensitivity 137
 - 3.2.4 Root Sensitivity 140
 - 3.2.5 Second-Order Active Filters 143
 - 3.2.6 High-Order Active Filters 149
- 3.3 Multiparameter Sensitivity 161
 - 3.3.1 Deterministic Case 162
 - 3.3.2 Statistical Case 165
 - 3.3.3 Monte Carlo Analysis 174
 - 3.3.4 Sensitivity Optimization 177
 - 3.3.5 Design Centering 181
- 3.4 Large-Change Sensitivity 188
- 3.5 Summary 190
- Problems 192

Operational Amplifiers and Fundamental Active Building Blocks

FOUR

- 4.1 Introduction 197
- 4.2 Op Amp Notation and Characteristics 199
 - 4.2.1 The Ideal Operational Amplifier 199

- 8.5.4 Noise 568
- 8.5.5 Tuning and Programming 569
- 8.5.6 Comparison with Other Techniques 569
- 8.6 Summary 571
- Problems 572

References 577

Laplace Transforms

APPENDIX I 589

z-Transforms

APPENDIX II 591

Tables of Classical Filter Functions

APPENDIX III 593

Index 602

- 6.4 LC Ladder Simulations 350
 - 6.4.1 LC Ladder Simulation by Signal-Flow Graphs 350
 - 6.4.2 LC Ladder Simulation by Element Substitution 385
- 6.5 Summary 399
- Problems 401

Fully Integrated Continuous-Time Filters

SEVEN

- 7.1 Introduction 410
- 7.2 Single-Ended Versus Fully Balanced Designs 413
 - 7.2.1 Fully Differential Op Amp Integrators 414
 - 7.2.2 Fully Balanced Transconductance-C Circuits 416
- 7.3 Automatic Tuning 418
 - 7.3.1 The Frequency-Control Block 429
 - 7.3.2 The Q-Control Block 434
- 7.4 Monolithic Filters Based on Op Amps 446
- 7.5 Monolithic Filters Based on Transconductances 457
 - 7.5.1 Cascade Design 458
 - 7.5.2 Ladder Simulation Using Gyration 464
 - 7.5.3 Ladder Simulation by Signal-Flow Graph Methods 469
- 7.6 Summary 482
- Problems 484

Switched-Capacitor Filters

EIGHT

- 8.1 Introduction 487
- 8.2 The Effect of Parasitics-Parasitics-Insensitive Building Blocks 492
- 8.3 Discrete-Time (Sampled-Data) Operation 500
 - 8.3.1 The Sampling Process 500
 - 8.3.2 Application of the z-Transform in Sampled-Data Systems 507
- 8.4 Design of Switched-Capacitor Filters 519
 - 8.4.1 The z-Domain Transfer Function 520
 - 8.4.2 Biquad Building Blocks and Cascade Design 524
 - 8.4.3 Ladder Simulations 534
- 8.5 Some Practical Observations, Precautions, and Limits 562
 - 8.5.1 Design and Layout Precautions 562
 - 8.5.2 Effects of Nonideal Op Amps 564
 - 8.5.3 Frequency Limitations 567