



DESIGN OF ANALOG FILTERS

Rolf Schaumann
Portland State University

Mac E. Van Valkenburg

New York Oxford
OXFORD UNIVERSITY PRESS
2001

THE OXFORD SERIES IN ELECTRICAL AND COMPUTER ENGINEERING

ADEL S. SEDRA, Series Editor, Electrical Engineering

Allen and Holberg, *CMOS Analog Circuit Design*
 Bobrow, *Elementary Linear Circuit Analysis, 2nd Ed.*
 Bobrow, *Fundamentals of Electrical Engineering, 2nd Ed.*
 Burns and Roberts, *An Introduction to Mixed-Signal IC Test and Measurement*
 Campbell, *The Science and Engineering of Microelectronic Fabrication, 2nd Ed.*
 Chen, *Analog & Digital Control System Design*
 Chen, *Digital Signal Processing*
 Chen, *Linear System Theory and Design, 3rd Ed.*
 Chen, *System and Signal Analysis, 2nd Ed.*
 Comer, *Digital Logic and State Machine Design, 3rd Ed.*
 Cooper and McGillem, *Probabilistic Methods of Signal and System Analysis, 3rd Ed.*
 DeCarlo and Lin, *Linear Circuit Analysis, 2nd Ed.*
 Dimitrijevic, *Understanding Semiconductor Devices*
 Fortney, *Principles of Electronics: Analog & Digital*
 Franco, *Electric Circuits Fundamentals*
 Granzow, *Digital Transmission Lines*
 Guru and Hiziroglu, *Electric Machinery & Transformers, 2nd Ed.*
 Hoole and Hoole, *A Modern Short Course in Engineering Electromagnetics*
 Jones, *Introduction to Optical Fiber Communication Systems*
 Krein, *Elements of Power Electronics*
 Kuo, *Digital Control Systems, 3rd Ed.*
 Lathi, *Modern Digital and Analog Communications Systems, 3rd Ed.*
 Martin, *Digital Integrated Circuit Design*
 McGillem and Cooper, *Continuous and Discrete Signal and System Analysis, 3rd Ed.*
 Miner, *Lines and Electromagnetic Fields for Engineers*
 Roberts and Sedra, *SPICE, 2nd Ed.*
 Roulston, *An Introduction to the Physics of Semiconductor Devices*
 Sadiku, *Elements of Electromagnetics, 3rd Ed.*
 Santina, Stubberud, and Hostetter, *Digital Control System Design, 2nd Ed.*
 Sarma, *Introduction to Electrical Engineering*
 Schaumann and Van Valkenburg, *Design of Analog Filters*
 Schwarz, *Electromagnetics for Engineers*
 Schwarz and Oldham, *Electrical Engineering: An Introduction, 2nd Ed.*
 Sedra and Smith, *Microelectronic Circuits, 4th Ed.*
 Stefani, Savant, Shahian, and Hostetter, *Design of Feedback Control Systems, 3rd Ed.*
 Van Valkenburg, *Analog Filter Design*
 Warner and Grung, *Semiconductor Device Electronics*
 Wolovich, *Automatic Control Systems*
 Yariv, *Optical Electronics in Modern Communications, 5th Ed.*

CONTENTS

Preface	xi
1 INTRODUCTION	1
1.1 Fundamentals	1
1.2 Types of Filters and Descriptive Terminology	5
1.3 Why We Use Analog Filters	9
1.4 Circuit Elements and Scaling	10
Problems	13
2 OPERATIONAL AMPLIFIERS	15
2.1 Operational Amplifier Models	16
2.1.1 The Integrator Model	17
2.1.2 The Ideal Operational Amplifier	24
2.2 Opamp Slew Rate	26
2.3 The Operational Amplifier with Resistive Feedback: Noninverting and Inverting Amplifiers	28
2.3.1 The Noninverting Amplifier	29
2.3.2 The Inverting Amplifier	37
2.4 Analyzing Opamp Circuits	40
2.5 Block Diagrams and Feedback	43
2.6 The Voltage Follower	47
2.7 Addition and Subtraction	49
2.8 Applications of Opamp Resistor Circuits	52
Problems	59
3 FIRST-ORDER FILTERS: BILINEAR TRANSFER FUNCTIONS AND FREQUENCY RESPONSE	64
3.1 Bilinear Transfer Function and Its Parts	65
3.2 Realization with Passive Elements	67
3.3 Bode Plots	78
6.4 Lowpass Filter Specifications	261
6.5 Arbitrary Transmission Zeros	267
Problems	274
7 LOWPASS FILTERS WITH EQUAL-RIPPLE (CHEBYSHEV) MAGNITUDE RESPONSE	277
7.1 The Chebyshev Polynomial	277
7.2 The Chebyshev Magnitude Response	280
7.3 Location of Chebyshev Poles	284
7.4 Comparison of Maximally Flat and Equal-Ripple Responses	287
7.5 Chebyshev Filter Design	291
Problems	296
8 INVERSE CHEBYSHEV AND CAUER FILTERS	298
8.1 The Inverse Chebyshev Response	300
8.2 From Specifications to Pole and Zero Locations	304
8.3 Cauer Magnitude Response	310
8.4 Chebyshev Rational Functions	314
8.5 Cauer Filter Design	318
8.6 Comparison of the Classical Filter Responses	328
8.6.1 Degree	330
8.6.2 Passband Response	331
8.6.3 Stopband Response	332
8.6.4 Transition Band	333
8.6.5 The Q Values Required	333
8.6.6 Time Delay	335
8.6.7 Circuit Realization	338
Problems	339
9 FREQUENCY TRANSFORMATION	341
9.1 Lowpass-to-Highpass Transformation	343
9.2 Lowpass-to-Bandpass Transformation	352
9.3 Lowpass-to-Band-Elimination Transformation	370
9.4 Lowpass-to-Multiple Passband Transformation	381
9.5 The Foster Reactance Function	387
Problems	391
10 DELAY FILTERS	398
10.1 Time-Delay and Transfer Functions	398
10.2 Bessel-Thomson Response	401

Oxford University Press

Oxford New York
Athens Auckland Bangkok Bogotá Buenos Aires Calcutta Cape Town
Chennai Dar es Salaam Delhi Florence Hong Kong Istanbul Karachi
Kuala Lumpur Madrid Melbourne Mexico City Mumbai Nairobi Paris
São Paulo Shanghai Singapore Taipei Tokyo Toronto Warsaw

and associated companies in
Berlin Ibadan

Copyright © 2001 by Oxford University Press, Inc.

Published by Oxford University Press, Inc.
198 Madison Avenue, New York, New York, 10016
http://www.oup-usa.org

Oxford is a registered trademark of Oxford University Press

All rights reserved. No part of this publication may be reproduced,
stored in a retrieval system, or transmitted, in any form or by any means,
electronic, mechanical, photocopying, recording, or otherwise,
without the prior permission of Oxford University Press.

Library of Congress Cataloging-in-Publication Data

Schaumann, Rolf, 1941–

Design of analog filters / Rolf Schaumann, Mac E. Van Valkenburg.

p. cm. — (The Oxford series in electrical and computer engineering)

Rev. ed. of: Analog filters design / M.E. Van Valkenburg. c1982.

Includes bibliographical references.

ISBN 0-19-511877-4 (cloth)

1. Electric filters. Active—Design and construction. 2. Analog electronic systems—Design and construction. 3. Linear integrated circuits—Design and construction. 4. Operational amplifiers.

I. Van Valkenburg, M. E. (Mac Elwyn), 1921– II. Van Valkenburg, M. E. (Mac Elwyn), 1921–

Analog filters design. III. Title. IV. Series.

TK787.Z55.S29 2001

621.3815324—dc21

99-035428

Printing (last digit): 9 8 7 6 5 4 3 2

Printed in the United States of America
on acid-free paper

Contents vii

vi CONTENTS

3.4 Active Realizations	84
3.4.1 Inverting Opamp Circuits	84
3.4.2 Noninverting Opamp Circuits	91
3.4.3 Differential Opamp Circuits Allpass Filters: Phase Shaping	95
3.5 The Effect of $A(s)$	99
3.6 Cascade Design	104
3.7 And Now Design	107
Problems	117
4 SECOND-ORDER LOWPASS AND BANDPASS FILTERS	125
4.1 Design Parameters: Q and ω_0	125
4.2 The Second-Order Circuit	129
4.3 Frequency Response of Lowpass and Bandpass Circuits	136
4.4 Integrators: The Effects of $A(s)$	147
4.4.1 Inverting Integrators	149
4.4.2 Noninverting Integrators	152
4.4.3 The Effects of $A(s)$ on the Biquad	155
4.5 Other Biquads	161
4.5.1 Sallen-Key Circuits	161
4.5.2 The Single-Amplifier Biquad (SAB)	170
4.5.3 The General Impedance Converter (GIC) Circuit	178
Problems	187
5 SECOND-ORDER FILTERS WITH ARBITRARY TRANSMISSION ZEROS	192
5.1 By Using Summing	193
5.1.1 Phase Response of the General Biquadratic Circuit	206
5.2 By Voltage Feedforward	209
5.3 Cascade Design Revisited	229
5.3.1 Pole-Zero Pairing	233
5.3.2 Section Ordering	235
5.3.3 Gain Assignment	237
Problems	246
6 LOWPASS FILTERS WITH MAXIMALLY FLAT MAGNITUDE	252
6.1 The Ideal Lowpass Filter	252
6.2 Butterworth Response	254
6.3 Butterworth Pole Locations	256

14.3	Realizing Simple Ladders	540
14.4	Gorski-Popiel's Embedding Technique	544
14.5	Bruton's FDNR Technique	549
14.6	Creating Negative Components	558
	Problems	564
15	OPERATIONAL SIMULATION OF LADDERS	568
15.1	Simulation of Lowpass Ladders	569
15.2	Design of General Ladders	580
15.3	All-Pole Bandpass Ladders	591
	Problems	599
16	TRANSCONDUCTANCE-C FILTERS	603
16.1	Transconductance Cells	605
16.1.1	A Model	610
16.2	Elementary Transconductor Building Blocks	613
16.2.1	Resistors	613
16.2.2	Integrators	616
16.2.3	Amplifiers	621
16.2.4	Summers	622
16.2.5	Gyrators	623
16.3	First- and Second-Order Filters	628
16.3.1	A First-Order Section	629
16.3.2	A Second-Order Section	630
16.4	High-Order Filters	638
16.4.1	Cascade Design	638
16.4.2	Ladder Design	638
16.5	Automatic Tuning	646
16.5.1	Frequency Tuning	648
16.5.2	Q -Tuning	650
16.5.3	On-Line-Off-Line Operation	653
	Problems	654
17	SWITCHED-CAPACITOR FILTERS	658
17.1	The MOS Switch	659
17.2	The Switched Capacitor	662
17.3	First-Order Building Blocks	664
17.4	Second-Order Sections	672
17.5	Sampled-Data Operation	676
17.5.1	The z -Transform	679
17.5.2	The Spectrum of a Sampled Signal	681

10.3	Bessel Polynomials	406
10.4	Further Comparisons of Responses	409
10.5	Design of Bessel-Thomson Filters	411
10.6	Equal-Ripple Delay Response	415
10.7	Approximating an Ideal Delay Function	422
10.8	Improving High-Frequency Attenuation Generating Gain Boosts	426
	Problems	430

11	DELAY EQUALIZATION	432
11.1	Equalization Procedures	433
11.2	Equalization with First-Order Modules	435
11.3	Equalization with Second-Order Modules	439
11.4	Strategies for Equalizer Design	444
	Problems	447

12	SENSITIVITY	451
12.1	Definition of Bode Sensitivity	453
12.2	Second-Order Sections	466
12.3	High-Order Filters	472
12.3.1	Cascade Design	474
12.3.2	LC Ladders	475
	Problems	477

13	LC LADDER FILTERS	482
13.1	Some Properties of Lossless Ladders	483
13.2	A Synthesis Strategy	487
13.3	Tables for Other Responses	497
13.4	General Ladder Design Methods	499
13.4.1	The Twoport Parameters	500
13.4.2	Immittance Synthesis	505
13.4.3	Ladder Development	511
13.5	Frequency Transformation	518
13.6	Design of Passive Equalizers	524
	Problems	529

14	LADDER SIMULATIONS BY ELEMENT REPLACEMENT	533
14.1	The General Impedance Converter	533
14.2	Optimal Design of the GIC	536

17.5.3	The Frequency Response for a z -Domain Transfer Function	684
17.6	Switched-Capacitor First- and Second-Order Sections	687
17.6.1	Bilinear Sections	689
17.6.2	Second-Order Sections	691
17.7	The Bilinear Transformation	697
17.8	Design of Switched-Capacitor Cascade Filters	700
17.9	Design of Switched-Capacitor Ladder Filters	705
17.9.1	The γ -Plane Circuit	712
17.9.2	The z -Domain Circuit	721
	Problems	731
	Index	735