


(1) بائیس DC مدار مقدار آبرابرات با:

$$I_C = 813 \mu A$$

$$r_{\pi} = 3.1 k\Omega, g_m = 32.5 mS$$

کہ نتیجہ میں شور

مدار معادل AC بہ صورت زیرات

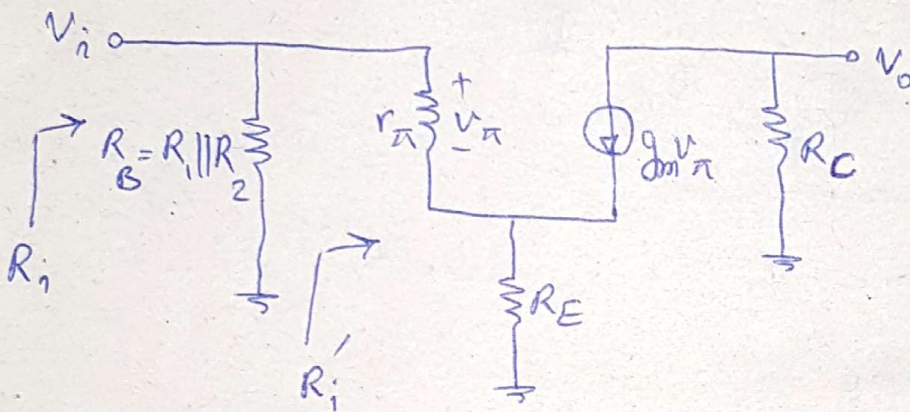

$$A_v = \frac{V_o}{V_i} = - \frac{R_C}{R_E + \frac{r_{\pi}}{\beta}} = -16.9$$

$$R'_i = r_{\pi} + \beta R_E \Rightarrow R_i = R_B \parallel R'_i = 3.6 k\Omega$$

$$r_o = 86.1 k\Omega$$

$V_A = 70V$ فواہم دات:

$$R'_o = r_o \left[1 + \frac{\beta R_E}{r_{\pi} + R_S + R_E} \right] \Rightarrow R_o = R'_o \parallel R_C = 3.9 k\Omega$$


(2) با تحلیل DC فواید حالت:

$$I_C = 2 \text{ mA} \Rightarrow r_{\pi} = 1.25 \text{ k}\Omega$$

$$g_m = 80 \text{ mS}$$

$$r_o = 75 \text{ k}\Omega$$

سار معادل AC به صورت زیر است:

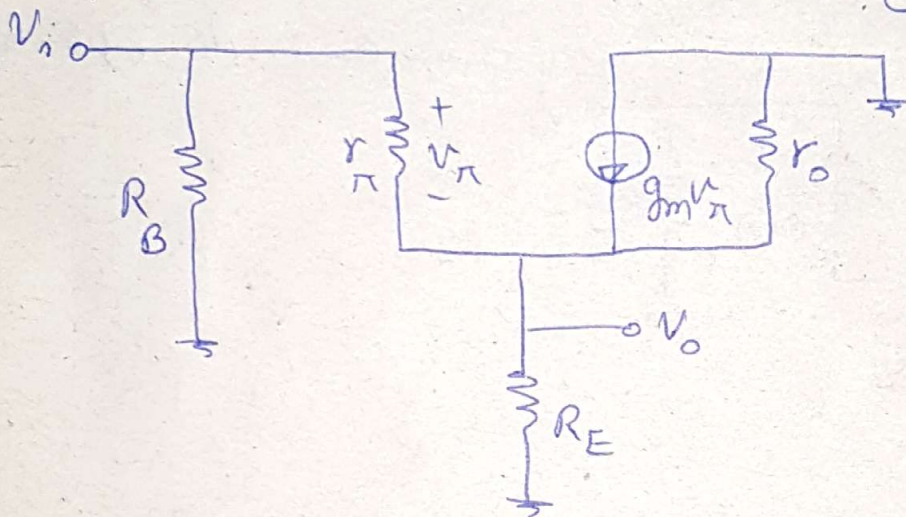

$$A_v = \frac{R_E}{R_E + \frac{r_{\pi}}{\beta}} = 0.994$$

$$R'_i = r_{\pi} + \beta R_E = 223 \text{ k}\Omega \Rightarrow R_i = R'_i \parallel R_B = 133 \text{ k}\Omega$$

$$R_o = R_E \parallel \frac{r_{\pi}}{\beta} \parallel r_o \approx R_E \parallel \frac{r_{\pi}}{\beta} = 12.4 \Omega$$

$$R_{oB} = r_o \parallel \left(r_e + \frac{R'_s}{\beta} \right), \quad R'_s = R_s \parallel R_B$$

با فرض دادن R_s فواید حالت:

$$R_o = R_{oB} \parallel R_E \approx 32 \Omega$$

(3) بائیں DC بہت سے اور ہم:

$$I_C = 1.06 \text{ mA}$$

$$g_m = 42.4 \text{ mS}$$

$$r_e = \frac{r_\pi}{\beta} = 23.6 \Omega$$

$$r_o = 189 \text{ k}\Omega$$

دائیں AC خواہم ثابت:

$$R_i \approx r_e = 23.6 \Omega$$

$$V_e = \frac{R_i}{R_i + R_s} V_s = 0.7 V_s$$

$$\frac{V_o}{V_e} = g_m R'_C, \quad R'_C = R_C \parallel R_L$$

$$\Rightarrow \frac{V_o}{V_s} = 0.7 \cdot \frac{V_o}{V_e} = \frac{V_e}{V_s} \cdot \frac{V_o}{V_e} = 0.7 \times 283 = \boxed{198}$$

$$I_C = 0.78 \text{ mA}, \quad r_e = \frac{r_\pi}{\beta} = 32 \Omega$$

(4) DC کیس


$$R_i = 6.8 \text{ k} \parallel r_e \approx 32 \Omega$$

AC کیس

$$R_o = 4.7 \text{ k}\Omega$$

$$A_v = \frac{R_C}{r_e} = 147, \quad \frac{V_i}{6.8 \text{ k}} = \frac{r_e i_e}{6.8 \text{ k}} = 5 \times 10^{-3} i_e$$
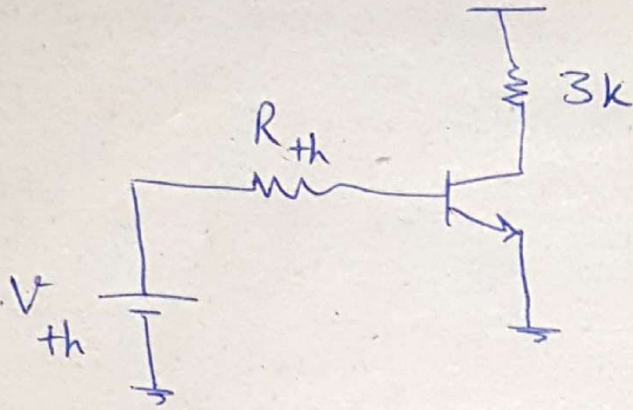
$$\Rightarrow A_i = \frac{\alpha i_e}{i_e} \approx \boxed{1}$$



$$R_{th} = 34 \parallel 16 = 10.88 k\Omega$$

$$V_{th} = \frac{16}{16+34} \times 2.5 = 0.8v$$

$$I_C = \beta \left(\frac{0.8 - V_{BE}}{10.88k} \right), \quad V_{BE} = V_T \ln \frac{I_C}{I_S}$$


$$I_C = 0.92mA, \quad V_{BE} = 0.734v$$

بافتراض $V_{BE} = 0.7v$ داریم:

$$I_C = 0.67mA, \quad V_{BE} = 0.726v$$

باروش تکراریدیت من آوریم:

$$I_B = 6.7\mu A, \quad V_{CE} = 0.49v$$

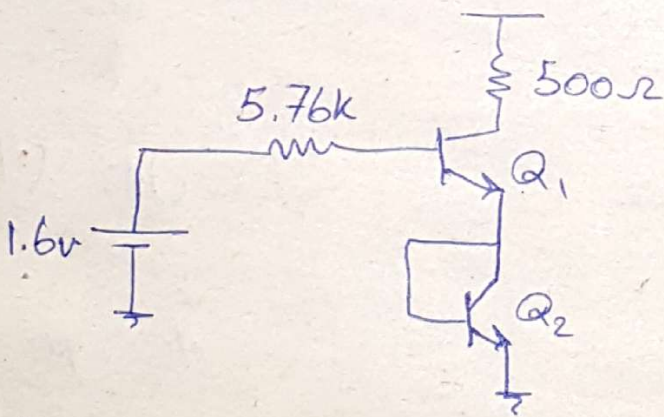

$$I_{C2} = \beta \left(\frac{1.6 - V_{BE1} - V_{BE2}}{5.76k} \right)$$

$$V_{BE} = V_{BE1} = V_{BE2} = V_T \ln \left(\frac{I_C}{I_S} \right)$$


فرض:

$$V_{BE1} = V_{BE2} = 0.7v \Rightarrow I_C = 3.47mA \Rightarrow V_{BE} = 0.769v$$

$$I_{C1} = I_{C2} = 1.74mA, \quad I_{B1} = I_{B2} = 17.4\mu A$$

باروش تکراریدیت من آوریم
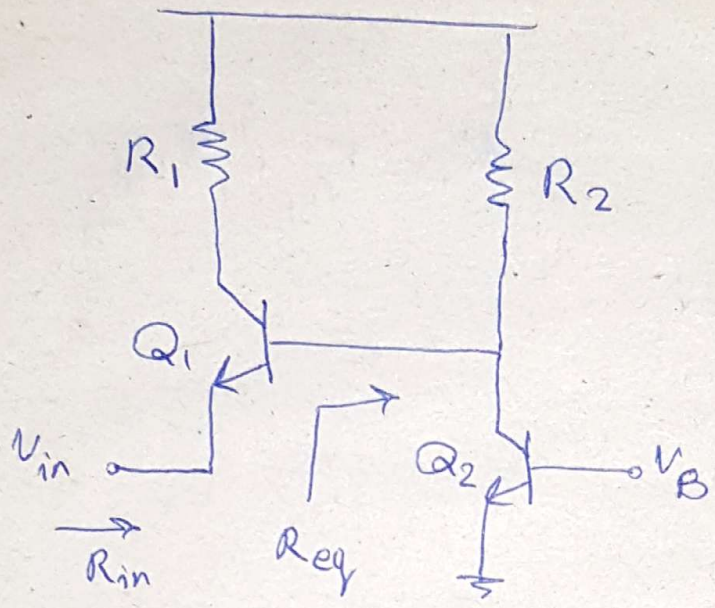
$$V_{BE1} = V_{BE2} = 0.75v, \quad V_{CE1} = 0.88v, \quad V_{CE2} = 0.75v$$




$$R_{eq} = R_2 \parallel \infty = R_2$$

$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} + \frac{R_2}{\beta_1 + 1}$$

$$R_{in} = \frac{1}{g_{m1}} + \frac{R_2}{\beta_1}$$

باتوجه به اینکه β معمولاً خیلی بزرگ است:

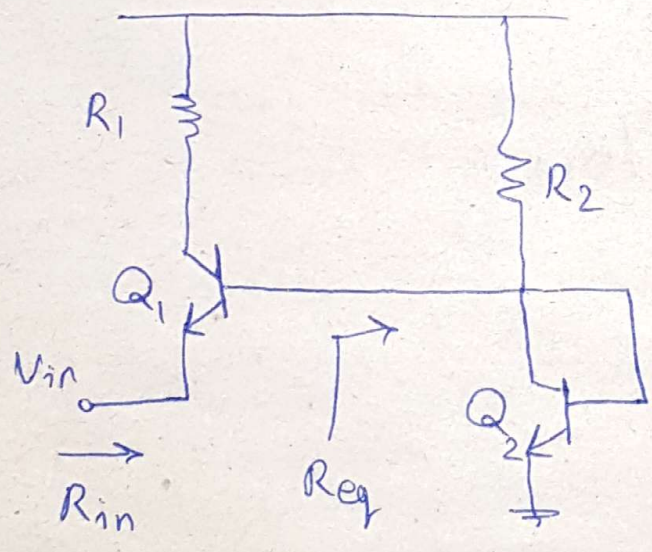


$$R_{eq} = R_2 \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}$$


$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} + \frac{R_{eq}}{\beta + 1}$$

باتوجه به بزرگ بودن β داریم
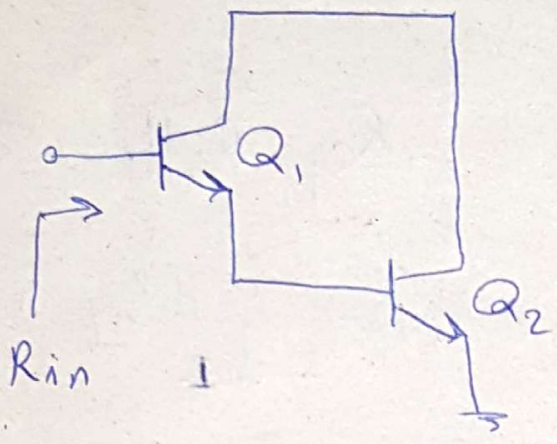
$$R_{in} = \frac{1}{g_{m1}} + \frac{R_{eq}}{\beta}$$



$$R_{in} = r_{\pi 1} + \beta r_{\pi 2}$$

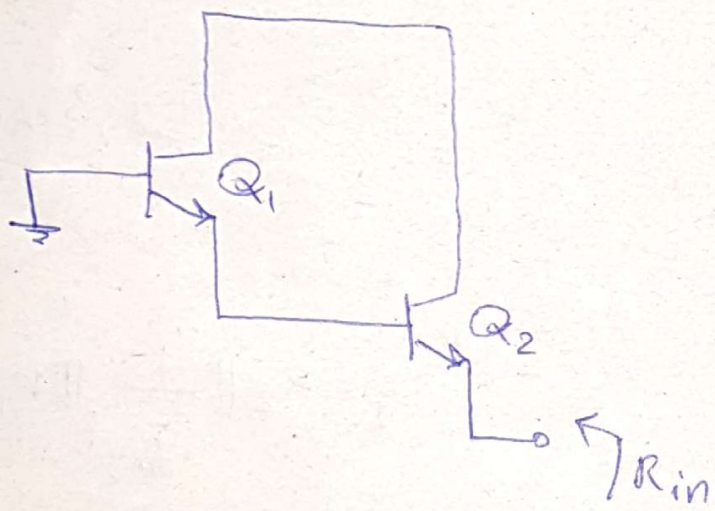

$$R_{in} = \frac{1}{g_{m2}} + \frac{\frac{1}{g_{m1}}}{\beta}$$