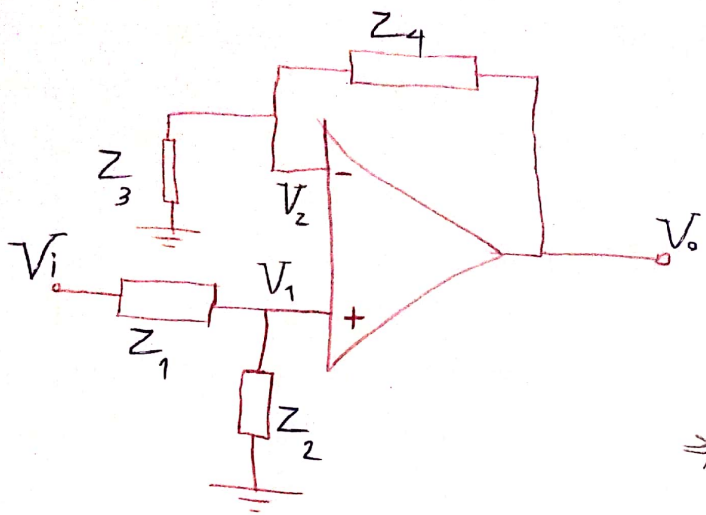


1



$$V_1 = V_2 = \frac{Z_2}{Z_2 + Z_1} V_i \quad (A)$$

$$KCL @ V_2: \frac{0 - V_2}{Z_3} = \frac{V_2 - V_o}{Z_4} \quad (B)$$

$$\Rightarrow V_o = \left(1 + \frac{Z_4}{Z_3}\right) V_2$$

$$(A), (B) \Rightarrow V_o = \left(1 + \frac{Z_4}{Z_3}\right) \left(\frac{Z_2}{Z_2 + Z_1}\right) V_i \rightarrow \left(\frac{V_o}{V_i}\right) = \frac{1 + \frac{Z_4}{Z_3}}{1 + \frac{Z_1}{Z_2}}$$

برای بالا نگه داشتن باند عبور باید مقادیر زیر را با جای امپدانس ها جایگزین کنیم:

$$Z_1 = \frac{1}{C_1 s}, Z_2 = R_2, Z_3 = R_3, Z_4 = R_4$$

$$\rightarrow \frac{V_o}{V_i} = \frac{R_2 C_1 (1 + \frac{R_4}{R_3}) s}{1 + R_2 C_1 s}$$


$$\text{فرکانس قطع: } f_c = \frac{1}{2\pi R_2 C_1}$$

$$25000 = \frac{1}{2\pi R_2 C_1} \rightarrow R_2 C_1 = 6.4 \times 10^{-6} \rightarrow \begin{cases} C_1 = 1 \text{ nF} \\ R_2 = 6.4 \text{ k}\Omega \end{cases}$$

f_c می خواهد 25 kHz باشد:

$$\begin{cases} R_3 = 100 \Omega \\ R_4 = 10 \text{ M}\Omega \end{cases}$$

2

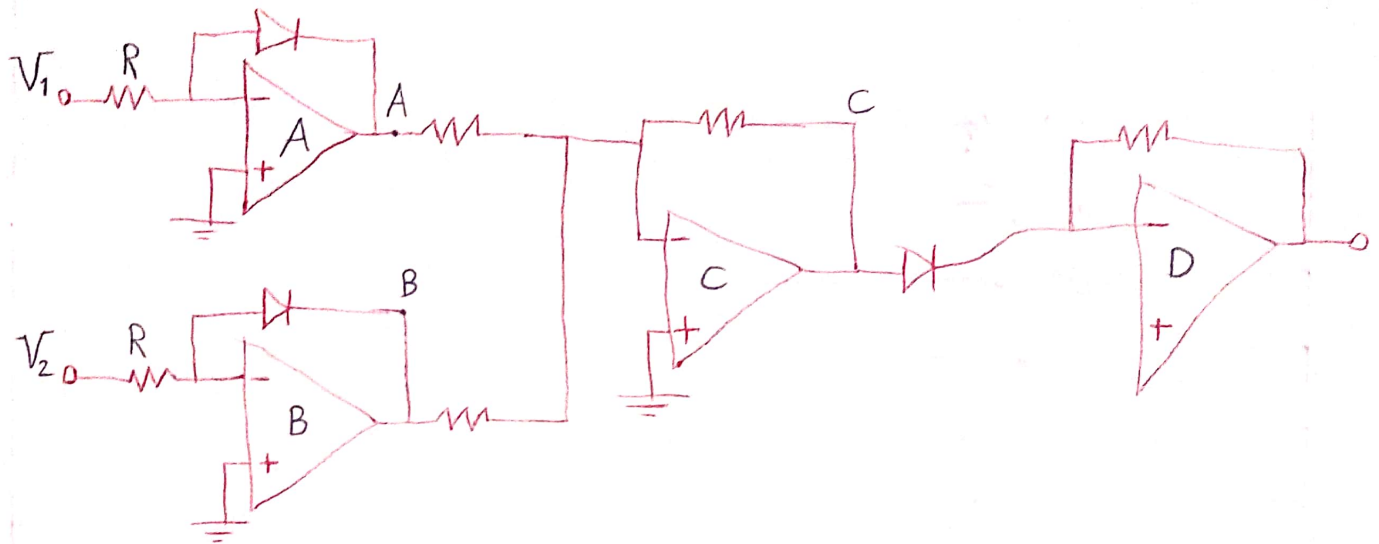

op-Amp A, kcl @ $V_- = \frac{V_1 - 0}{R} = I_s e^{\frac{0 - V_a}{V_T}} \rightarrow \frac{V_1}{RI_s} = e^{\frac{-V_a}{V_T}} \rightarrow V_a = -V_T \ln \frac{V_1}{RI_s}$

به همین ترتیب داریم: $V_b = -V_T \ln \frac{V_2}{RI_s}$

$V_c = -R \left[\frac{V_a}{R} + \frac{V_b}{R} \right] = -V_a - V_b$

Op Amp C جمع کننده است:

$\rightarrow V_c = V_T \left(\ln \frac{V_1}{RI_s} + \ln \frac{V_2}{RI_s} \right) = V_T \ln \frac{V_1 V_2}{R^2 I_s^2}$


Op-Amp D exponential گیر است:

kcl @ $V_- = I_s e^{\frac{V_c - 0}{V_T}} = \frac{0 - V_o}{R}$

$\rightarrow V_o = -RI_s e^{\frac{V_c}{V_T}} = -RI_s e^{\frac{V_T \ln \frac{V_1 V_2}{R^2 I_s^2}}{V_T}} = -RI_s \times \left(\frac{V_1 V_2}{R^2 I_s^2} \right)$

$\rightarrow V_o = -\frac{V_1 V_2}{RI_s}$

3

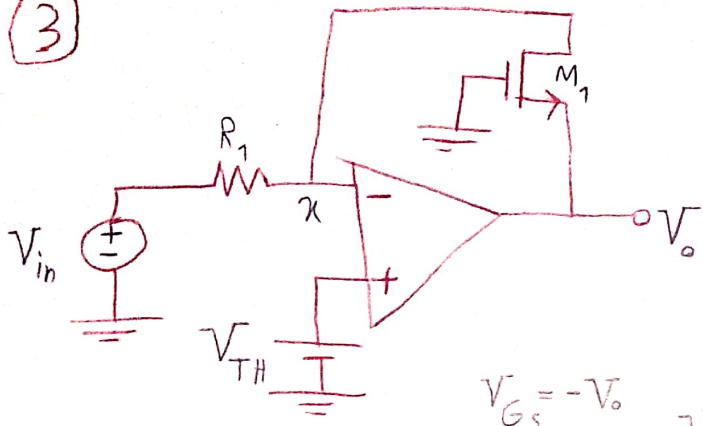

$k \ll \beta @ \mu$

$$\Rightarrow \frac{V_{in} - V_{TH}}{R_1} = \frac{1}{2} k (V_{GS} - V_{TH})^2$$

$$V_{GS} = -V_o \rightarrow \frac{V_{in} - V_{TH}}{R_1} = \frac{1}{2} k (-V_o - V_{TH})^2$$

$$\rightarrow (V_o + V_{TH})^2 = \frac{2(V_{in} - V_{TH})}{k R_1} \rightarrow V_o + V_{TH} = \sqrt{\frac{2(V_{in} - V_{TH})}{k R_1}}$$

$$\rightarrow V_o = \sqrt{\frac{2(V_{in} - V_{TH})}{k R_1}} - V_{TH}$$

مبار داده شده در واقع نوع مدار square root
گیر است.

$$4) \quad V_{b2} = \frac{R_4}{R_4 + R_3} V_o \quad V_{b2} = V_Z + V_{BE2} \quad V_Z = V_i - R_2 (I_Z - I_{E2}) \quad \textcircled{C}$$

$$I_{E2} = \frac{V_i - (V_o + V_{BE1})}{R_1} \quad V_Z = V_{ZK} + r_Z I_Z \rightarrow I_Z = \frac{V_Z - V_{ZK}}{r_Z} \quad \textcircled{B}$$

$$\textcircled{A} \textcircled{B} \textcircled{C} \rightarrow V_Z = V_i - R_2 \left[\frac{V_Z - V_{ZK}}{r_Z} - \frac{V_i}{R_1} + \frac{V_o + V_{BE1}}{R_1} \right]$$

$$\rightarrow \left(1 + \frac{R_2}{r_Z}\right) V_Z = \left(1 + \frac{R_2}{R_1}\right) V_i - \frac{R_2}{R_1} V_o + \frac{R_2}{r_Z} V_{ZK} - \frac{R_2}{R_1} V_{BE1}$$

$$\rightarrow V_Z = \frac{r_Z (R_1 + R_2)}{(r_Z + R_2) R_1} V_i - \frac{R_2 r_Z}{(r_Z + R_2) R_1} V_o + \frac{r_Z R_2}{(r_Z + R_2) R_1} V_{ZK} - \frac{r_Z R_2}{(r_Z + R_2) R_1} V_{BE1} \quad \textcircled{D}$$

$\textcircled{D} \textcircled{e} \textcircled{f} \rightarrow$

$$V_o = \frac{(R_3 + R_4) r_Z (R_1 + R_2)}{R_4 (r_Z + R_2) R_1} V_i - \frac{(R_3 + R_4) R_2 r_Z}{R_4 (r_Z + R_2) R_1} V_o + \frac{(R_3 + R_4) R_2}{R_4 (r_Z + R_2)} V_{ZK} + \frac{(R_3 + R_4) r_Z R_2}{R_4 (r_Z + R_2) R_1} V_{BE1} + \frac{(R_3 + R_4)}{R_4} V_{BE2}$$

$$S_V = \frac{\Delta V_o}{\Delta V_i} = \frac{(R_3 + R_4) r_Z (R_1 + R_2)}{R_4 (r_Z + R_2) R_1}$$

$$S_T = \frac{\Delta V_o}{\Delta T} = \frac{(R_3 + R_4) R_2}{R_4 (r_Z + R_2) R_1} \frac{\Delta V_{ZK}}{\Delta T} + \frac{(R_3 + R_4) r_Z R_2}{R_4 (r_Z + R_2) R_1} \frac{\Delta V_{BE1}}{\Delta T} + \frac{(R_3 + R_4)}{R_4} \frac{\Delta V_{BE2}}{\Delta T}$$