


-۲ روش‌های متعددی برای اثبات این دو رابطه وجود دارد.

$$(a \oplus b \oplus c)' = (a \odot b \odot c)' = (a \odot p)' = a \oplus p = a \oplus (b \odot c) = a \oplus (b \oplus c)'$$

$$a \oplus b \oplus ab = (a \oplus b)'ab + (a \oplus b)(ab)' = (ab + a'b')ab + (ab' + a'b)(a' + b') =$$



$$ab + ab' + a'b = a + a'b = a + b \Rightarrow$$
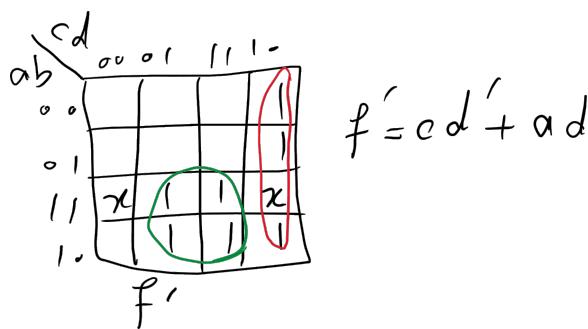
$$a \oplus c \oplus ac = a + c \rightarrow (a \oplus b \oplus ab)(a \oplus c \oplus ac) = (a + b)(a + c) = a + bc$$









$$\begin{aligned} d &= D \odot L \\ a &= D \odot R \\ d' &= D \odot \overline{L} \\ a' &= D \odot \overline{R} \end{aligned}$$

| ab | cd | w | x | y | z |
|------|------|-----|-----|-----|-----|
| 0000 | 00 | 0 | 0 | 1 | 1 |
| 0001 | 01 | 0 | 1 | 0 | 0 |
| 0011 | 11 | 0 | 1 | 0 | 1 |
| 0010 | 10 | 0 | 1 | 1 | 0 |
| 0110 | 00 | 0 | 1 | 1 | 1 |
| 0111 | 10 | 1 | 0 | 0 | 0 |
| 0101 | 01 | 1 | 0 | 0 | 1 |
| 0100 | 11 | 1 | 0 | 1 | 0 |
| 1100 | 10 | 1 | 0 | 1 | 1 |
| 1101 | 01 | 1 | 1 | 0 | 0 |

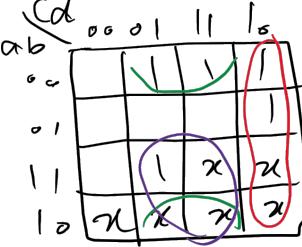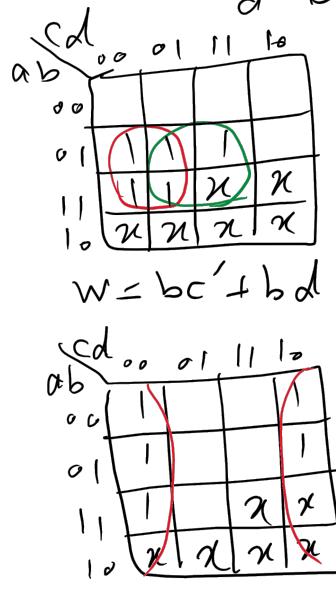
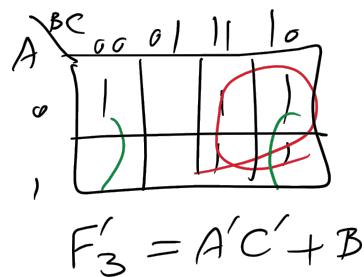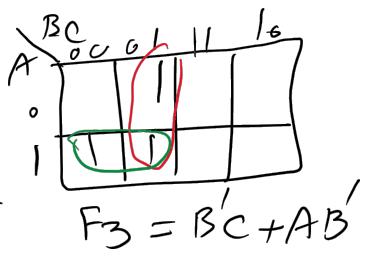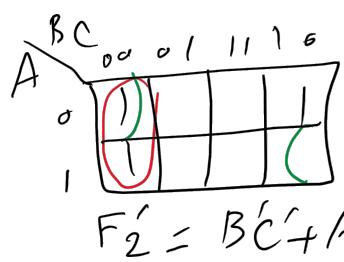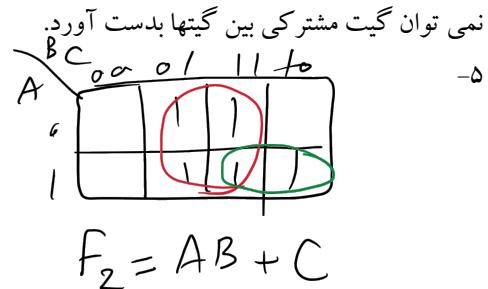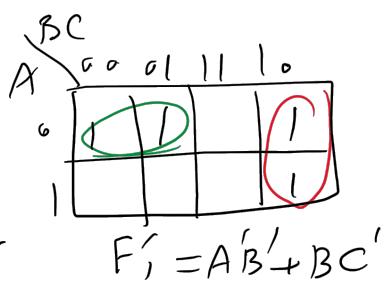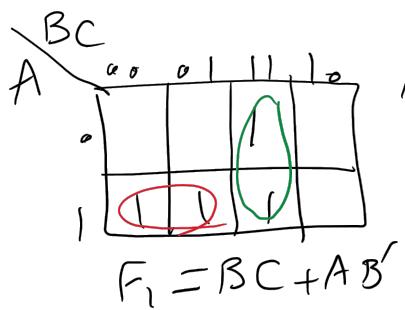
$$\begin{aligned} x &= cd' + ad + b'd \\ y &= d' \\ z &= b'cd + b'c'd' + ad' \\ &\quad + bcd' + a'b'cd \end{aligned}$$



| <u>A</u> | <u>B</u> | <u>C</u> | <u>F_1</u> | <u>F_2</u> | <u>F_3</u> |
|----------|----------|----------|-------------------------|-------------------------|-------------------------|
| - | 1 | 1 | 1 | - | - |
| 1 | 0 | - | 1 | - | 1 |
| - | 0 | 1 | - | - | 1 |
| - | 0 | 0 | - | - | - |
| 0 | - | 0 | - | - | 1 |
| | | | T | C | T |


| <u>a</u> | <u>b</u> | <u>c</u> | <u>d</u> | <u>w</u> | <u>x</u> | <u>y</u> | <u>z</u> |
|----------|----------|----------|----------|----------|----------|----------|----------|
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |

$$w = \sum(4, 5) + d(10, 11, 12, 13, 14, 15)$$

$$x = \sum(0, 1, 2, 3, 7, 8, 9) + \sim$$

$$y = \sum(2, 3, 6, 9) + \sim$$

$$z = \sum(1, 3, 5, 6, 8) + \sim$$

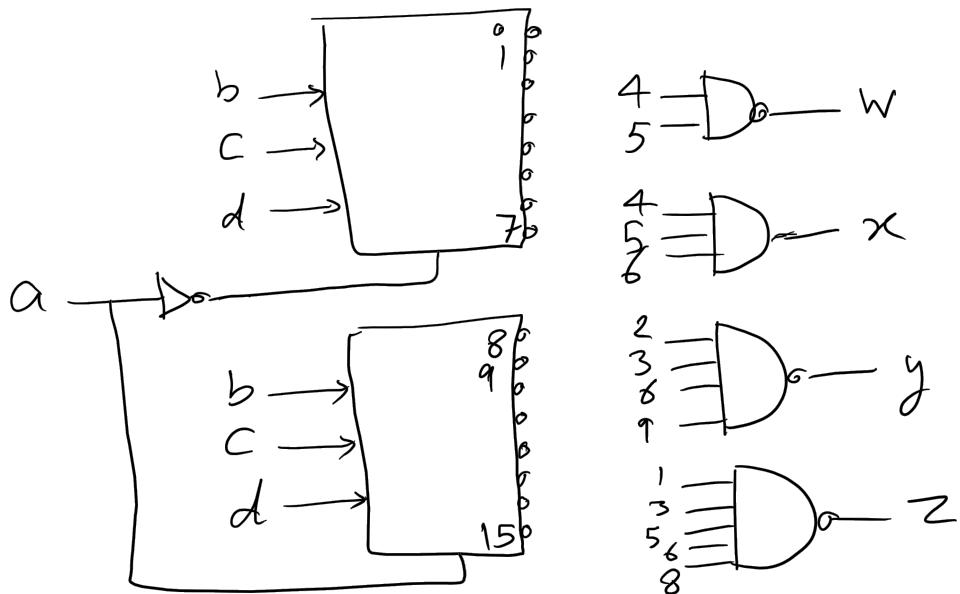

| | I ₀ | I ₁ | I ₂ | I ₃ |
|------|----------------|----------------|----------------|----------------|
| a'b' | 0 | 1 | 2 | 3 |
| a'b | 4 | 5 | 6 | 7 |
| ab | 12 | 13 | 14 | 15 |
| ab' | 8 | 9 | 10 | 11 |
| w | b | b | 0 | 0 |

| | I ₀ | I ₁ | I ₂ | I ₃ |
|------|----------------|----------------|----------------|----------------|
| a'b' | 0 | 1 | 2 | 3 |
| a'b | 4 | 5 | 6 | 7 |
| ab | 12 | 13 | 14 | 15 |
| ab' | 8 | 9 | 10 | 11 |
| x | b' | b' | b' | a' |

| | I ₀ | I ₁ | I ₂ | I ₃ |
|------|----------------|----------------|----------------|----------------|
| a'b' | 0 | 1 | 2 | 3 |
| a'b | 4 | 5 | 6 | 7 |
| ab | 12 | 13 | 14 | 15 |
| ab' | 8 | 9 | 10 | 11 |
| y | 0 | a | a' | b' |

| | I ₀ | I ₁ | I ₂ | I ₃ |
|------|----------------|----------------|----------------|----------------|
| a'b' | 0 | 1 | 2 | 3 |
| a'b | 4 | 5 | 6 | 7 |
| ab | 12 | 13 | 14 | 15 |
| ab' | 8 | 9 | 10 | 11 |
| | a | a' | b | b' |

چون هیچیک از خروجی ها برابر ورودیها یا هیچیک از خروجیها صفر و یا یک نیستند، اندازه ROM برابر 16×4 است.