
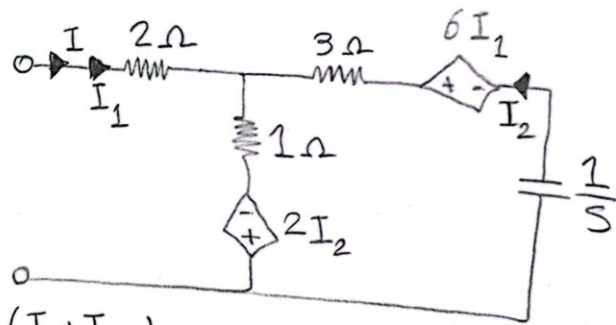


پاسخ نامه تکلیف سری ۳  
مدار الکتریکی ترم ۴۰۲۲

-۱

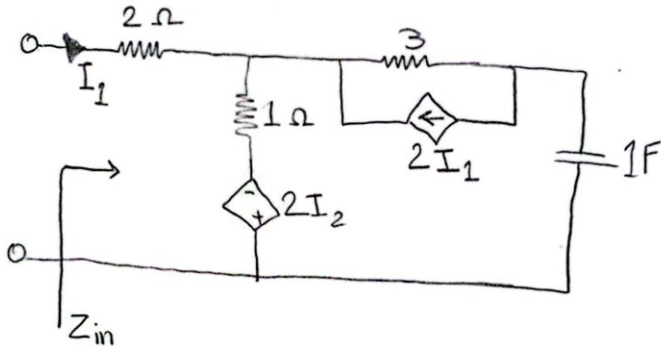


KVL در حلقه راست:  $\frac{1}{S} I_2 - 6I + 3I_2 + 1 \times (I + I_2) - 2I_2 = 0$

$$I_2 = \frac{5S}{2S+1} I$$


KVL در حلقه چپ:  $V = 2I + 1 \times (I + I_2) - 2I_2 \rightarrow V = 3I - I_2$
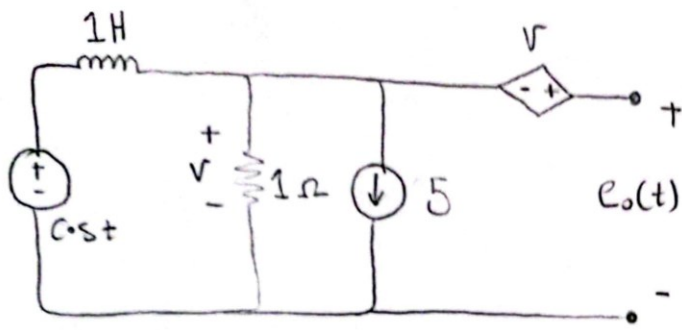
$$V = \left(3 - \frac{5S}{2S+1}\right) I \rightarrow \frac{V}{I} = \frac{S+3}{2S+1}$$



با توجه به تفاوت فرکانس ما از جمع آثار استادی لینیم


$$V=0, e_1=0$$

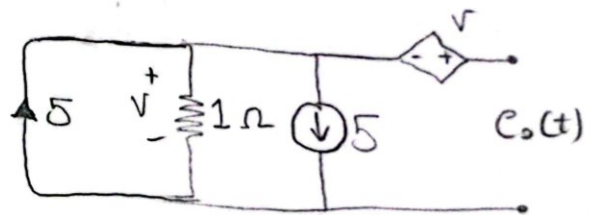


$$V=i \rightarrow i = \frac{1 \angle 0}{1+j} = \frac{1}{\sqrt{2}} \angle -45$$

$$V = \frac{1}{\sqrt{2}} \angle -45$$

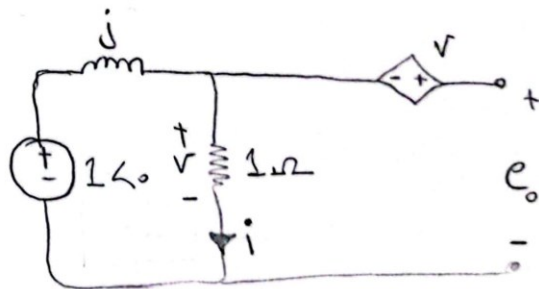
$$e_2 = 2V \rightarrow \frac{2}{\sqrt{2}} \angle -45$$


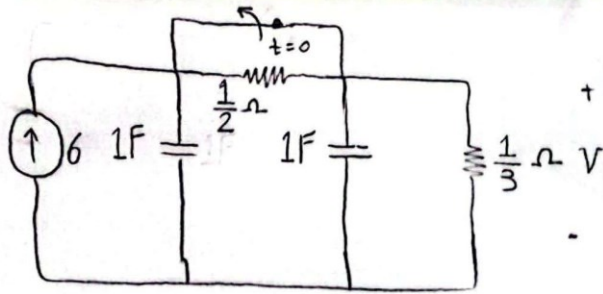
$$e_o = e_1 + e_2 \Rightarrow 0 + \frac{2}{\sqrt{2}} \angle -45 \Rightarrow e_o(t) = \frac{2}{\sqrt{2}} \cos(t - 45)$$



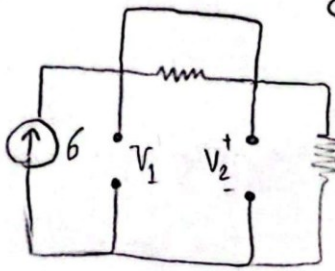ابتدا شرایط اولیه را در  $t=0$  محاسبه کنیم در این حالت خازن مدار باز است



$$V_1(0) = V_2(0) = \frac{1}{3} \times 6 = 2$$


سپس با اعمال شرایط اولیه مدار را به حوزه لاپلاس ببریم

$$Kcl(1): s(V_1 - \frac{2}{s}) + 2(V_1 - V_2) = \frac{6}{s}$$

$$(s^2 + 2s)V_1 - 2sV_2 = 2s + 6 \quad \text{I}$$


$$Kcl(2): 2(V_2 - V_1) + s(V_2 - \frac{2}{s}) + 3(V_2 - 0) = 0$$

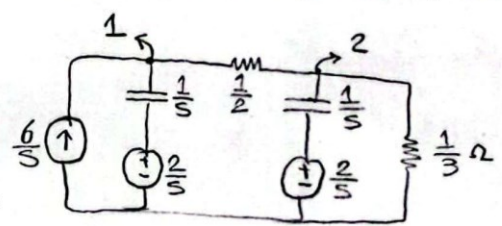
$$-2V_1 + (s + 5)V_2 = 2 \quad \text{II}$$




$$\text{I, II} \rightarrow V_2 = \frac{2(s^2 + 2s) + 2(2s + 6)}{(s^2 + 2s)(s + 5) - 4s} = \frac{2s^2 + 8s + 12}{s(s + 1)(s + 2)}$$
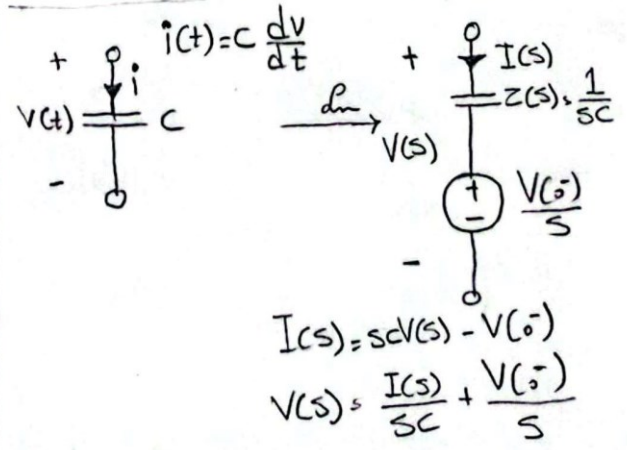
$$V_2 = \frac{2}{s} - \frac{1.2}{s + 1} + \frac{1.2}{s + 2} \rightarrow V_2(t) = (2 - 1.2e^{-t} + 1.2e^{-2t})u(t)$$



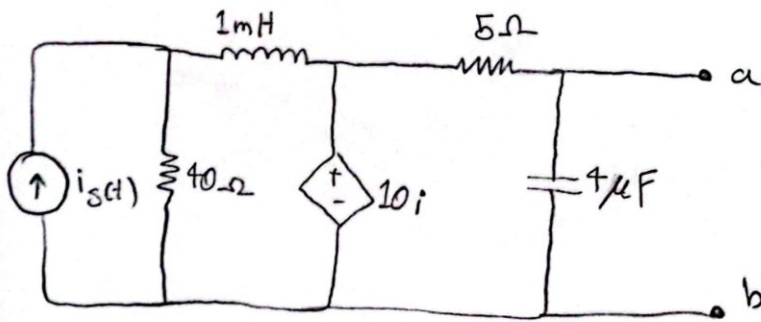
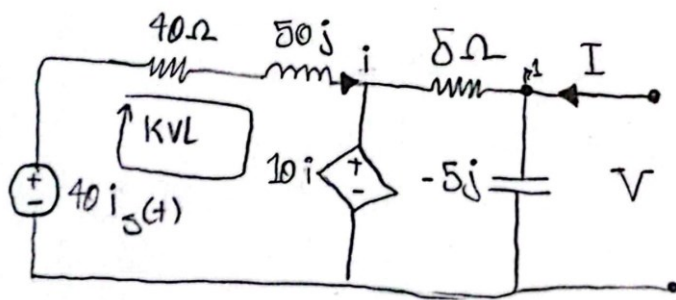
$$i_s(t) = 5 \text{ C} \cdot s(5 \times 10^4 t)$$





$$\text{KVL: } -40 i_s + (40 + 50j)i + 10i = 0 \rightarrow i = \frac{40 i_s(t)}{50 + 50j}$$

$$i = \frac{40 \times 5}{50 + 50j} = 2 - 2j$$

$$\text{Kcl(1): } \frac{V - 10i}{5} + \frac{V - 0}{-5j} - I = 0 \xrightarrow{\times 5} V - 10i - Vj = 5I \rightarrow$$

$$V - 10(2 - 2j) - Vj = 5I \rightarrow (1 + j)V = 5I + 10(2 - 2j)$$
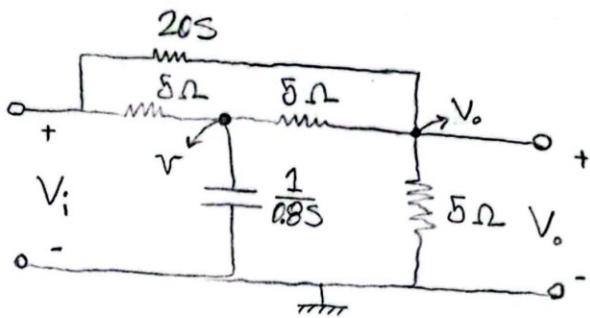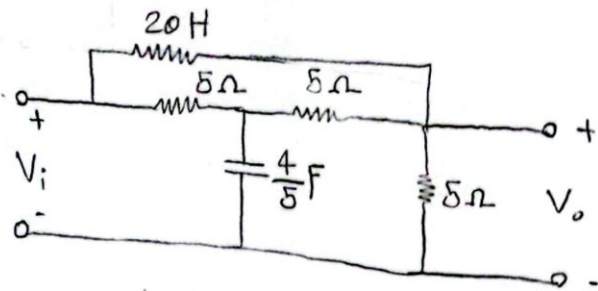
$$V = \left(\frac{5}{2} - \frac{5}{2}j\right)I - 20j$$



Kcl: 
$$\frac{V-V_o}{5} + \frac{V-V_i}{5} + \frac{V}{0.8S} = 0 \rightarrow V = \frac{V_o + V_i}{2+4s} \quad \text{①}$$

Kcl 
$$\frac{V_o - V_i}{20S} + \frac{V_o - V}{5} + \frac{V_o - 0}{5} = 0 \xrightarrow{\times 20S} V_o - V_i + 4sV_o - 4sV + 4sV_o = 0$$

$$(1+8s)V_o - V_i + 4sV_o = 0 \xrightarrow{\text{①}} (1+8s)V_o - V_i + 4s\left(\frac{V_o + V_i}{2+4s}\right) = 0$$

$$(32s^2 + 16s + 2)V_o = (8s + 2)V_i$$

$$\frac{V_o}{V_i} = \frac{8s+2}{32s^2+16s+2} = \frac{4s+1}{16s^2+8s+1} = \frac{4s+1}{(4s+1)^2} = \frac{1}{4s+1}$$

$$h(t) = -\delta(t) + 2e^{-2t} u(t)$$

$$e(t) = 1 + c \cdot s 2t + \sin 4t$$

$$H(s) = -1 + \frac{2}{s+2} \Rightarrow \frac{-s}{s+2}$$

$$1 \rightarrow H(0) = 0$$

$$c \cdot s 2t \rightarrow H(2j) = \frac{-2j}{2+2j} = \frac{-1}{2} - \frac{1}{2}j \Rightarrow \frac{\sqrt{2}}{2} c \cdot s (2t - \frac{3\pi}{4})$$

$$\sin 4t \rightarrow H(4j) = \frac{-4j}{2+4j} = \frac{16}{20} - \frac{8}{20}j \Rightarrow \frac{2\sqrt{5}}{5} \sin(4t - 26.56)$$