

$$\begin{cases} v' - (i_s - i) - v + (i_s - Cv') = 0 \\ (i_s - Cv') + (i_s - Cv' - i) - v = 0 \end{cases} \rightarrow \begin{cases} v' - Cv' = -i + v \\ v_i - i - v = Cv' \end{cases} \rightarrow v' = \frac{1}{\gamma C}(v_i - i - v),$$

$$i' - C \frac{1}{\gamma C}(v_i - i - v) = -i + v \rightarrow i' = i_s - 1/\delta i + 1/\delta v \rightarrow \begin{bmatrix} v' \\ i' \end{bmatrix} = \begin{bmatrix} -1/\gamma C & -1/\gamma C \\ 1/\delta & -1/\delta \end{bmatrix} \begin{bmatrix} v \\ i \end{bmatrix} + \begin{bmatrix} 1/C \\ 1 \end{bmatrix} i_s$$

$$y = v_L = (i_s - 1/\delta i + 1/\delta v) \rightarrow y = v_L = [1/\delta \quad -1/\delta] \begin{bmatrix} v \\ i \end{bmatrix} + i_s$$

$$A = \begin{bmatrix} -1/\gamma C & -1/\gamma C \\ 1/\delta & -1/\delta \end{bmatrix}, |sI - A| = \begin{vmatrix} s + 1/\gamma C & 1/\gamma C \\ -1/\delta & s + 1/\delta \end{vmatrix} = (s + 1/\gamma C)(s + 1/\delta) + 1/\gamma \delta = s^2 + (1/\delta + 1/\gamma C)s + 1/C = 0$$

$$s = -1 \rightarrow 1 - (1/\delta + 1/\gamma C) + 1/C = 0 \rightarrow -1/\delta = -1/\gamma \delta \rightarrow C = \gamma$$

$$Y(s) = C(sI - A)^{-1} BU(s) + DU(s) = [1/\delta \quad -1/\delta] \begin{bmatrix} s + 1/\delta & 1/\delta \\ -1/\delta & s + 1/\delta \end{bmatrix}^{-1} \begin{bmatrix} 1 \\ 1 \end{bmatrix} + 1 \rightarrow$$

$$Y(s) = [1/\delta \quad -1/\delta] \frac{1}{(s+1)^2} \begin{bmatrix} s + 1/\delta & 1/\delta \\ -1/\delta & s + 1/\delta \end{bmatrix} \begin{bmatrix} 1 \\ 1 \end{bmatrix} + 1 = [1/\delta \quad -1/\delta] \frac{1}{(s+1)^2} \begin{bmatrix} s+1 \\ s+1 \end{bmatrix} + 1 \rightarrow$$

$$Y(s) = \frac{s}{s+1} = 1 - \frac{1}{s+1} \rightarrow y(t) = \delta(t) - e^{-t} u(t)$$

$$Y(s) = C(sI - A)^{-1} BU(s) + C(sI - A)^{-1} x(\cdot) + DU(s)$$

$$Y(s) = [1/\delta \quad -1/\delta] \begin{bmatrix} s + 1/\delta & 1/\delta \\ -1/\delta & s + 1/\delta \end{bmatrix}^{-1} \begin{bmatrix} 1 \\ 1 \end{bmatrix} s + [1/\delta \quad -1/\delta] \begin{bmatrix} s + 1/\delta & 1/\delta \\ -1/\delta & s + 1/\delta \end{bmatrix}^{-1} \begin{bmatrix} x_1(\cdot) \\ x_2(\cdot) \end{bmatrix} + \frac{1}{s}$$

$$Y(s) = [1/\delta \quad -1/\delta] \frac{1}{(s+1)^2} \begin{bmatrix} s + 1/\delta & 1/\delta \\ -1/\delta & s + 1/\delta \end{bmatrix} \begin{bmatrix} 1 \\ 1 \end{bmatrix} s + [1/\delta \quad -1/\delta] \frac{1}{(s+1)^2} \begin{bmatrix} s + 1/\delta & 1/\delta \\ -1/\delta & s + 1/\delta \end{bmatrix} \begin{bmatrix} x_1(\cdot) \\ x_2(\cdot) \end{bmatrix} + \frac{1}{s}$$

$$Y(s) = [1/\delta \quad -1/\delta] \frac{1}{(s+1)^2} \begin{bmatrix} s+1 \\ s+1 \end{bmatrix} s + \frac{1}{(s+1)^2} [1/\delta s \quad -1/\delta s - 1] \begin{bmatrix} x_1(\cdot) \\ x_2(\cdot) \end{bmatrix} + \frac{1}{s}$$

$$Y(s) = \frac{-1}{s(s+1)} + \frac{1/\delta s x_1(\cdot) - (1/\delta s + 1)x_2(\cdot)}{(s+1)^2} + \frac{1}{s} = \frac{-s - 1 + 1/\delta s x_1(\cdot) - s(1/\delta s + 1)x_2(\cdot) + (s+1)^2}{s(s+1)^2}$$

برای اینکه پاسخ شامل هیچ بخش گذرا نباشد، بایستی ریشه صورت هم ۱- با مرتبه ۲ باشد. پس :


$$[-s - 1 + \frac{1}{5s} x_1(0) - s(\frac{1}{5s} + 1)x_r(0) + (s+1)^2]_{s=-1} = 0 \rightarrow \frac{1}{5}x_1(0) - \frac{1}{5}x_r(0) = 0 \rightarrow x_1(0) = x_r(0) \quad \boxed{1}$$

$$[-s - 1 + \frac{1}{5s} x_1(0) - s(\frac{1}{5s} + 1)x_r(0) + (s+1)^2]_{s=-1}' = 0 \rightarrow [-1 + sx_1(0) - (3s+1)x_r(0) + 2(s+1)]_{s=-1}' = 0$$

$$\rightarrow -1 - x_1(0) + 2x_r(0) = 0 \rightarrow x_1(0) = x_r(0) = 1 \rightarrow v_C(0) = i_L(0) = 1 \Rightarrow$$

$$Y(s) = \frac{-s - 1 + \frac{1}{5s} - s(\frac{1}{5s} + 1) + (s+1)^2}{s(s+1)^2} = \frac{\cdot}{s(s+1)^2} \rightarrow y(t) = \cdot$$

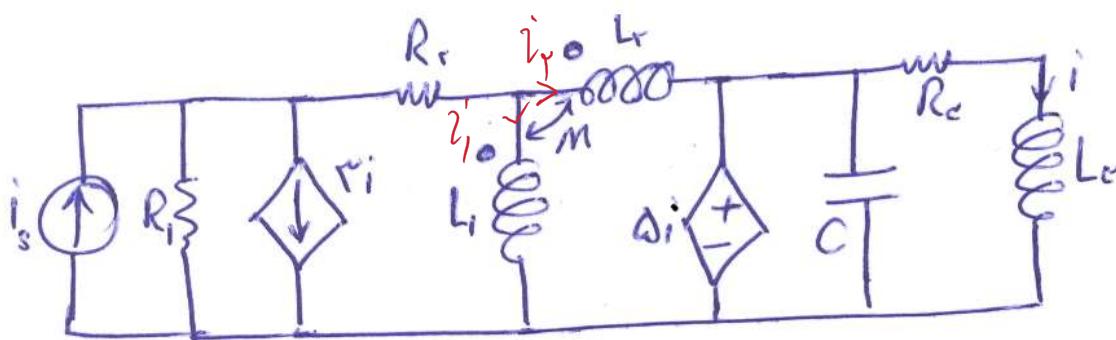نواتهای سلیمانی و حلقه خازنی نداریم. از طرفی نمی توان ولتاژ خازن را متغیر حالت گرفت. چون $N = (3+1) - 0 - 0 - 1 = 3 - 3$ این ولتاژ برابر ۵ است که در آن متغیر حالت (جریان سلف سوم است).



$$\begin{cases} R_r i + L_r i' - \delta i = 0 \\ R_r(i_s - \tau i - i_1 - i_r) = R_r(i_1 + i_r) + L_r i' + M i_r' \rightarrow \\ L_r i' + M i_r' = L_r i'_r + M i'_r + \delta i \end{cases}$$

$$\begin{bmatrix} L_r & \cdot & \cdot \\ \cdot & L_r & M \\ \cdot & L_r - M & -L_r + M \end{bmatrix} \begin{bmatrix} i \\ i_1 \\ i_r \end{bmatrix}' = \begin{bmatrix} -R_r + \delta & \cdot & \cdot \\ -\tau R_r & -(R_r + R_r) & -(R_r + R_r) \\ \delta & \cdot & \cdot \end{bmatrix} \begin{bmatrix} i \\ i_1 \\ i_r \end{bmatrix} + \begin{bmatrix} \cdot \\ R_r \\ \cdot \end{bmatrix} i_s \rightarrow$$

$$\begin{bmatrix} i \\ i_1 \\ i_r \end{bmatrix}' = \begin{bmatrix} L_r & \cdot & \cdot \\ \cdot & L_r & M \\ \cdot & L_r - M & -L_r + M \end{bmatrix}^{-1} \begin{bmatrix} -R_r + \delta & \cdot & \cdot \\ -\tau R_r & -(R_r + R_r) & -(R_r + R_r) \\ \delta & \cdot & \cdot \end{bmatrix} \begin{bmatrix} i \\ i_1 \\ i_r \end{bmatrix} +$$

$$\begin{bmatrix} L_r & \cdot & \cdot \\ \cdot & L_r & M \\ \cdot & L_r - M & -L_r + M \end{bmatrix}^{-1} \begin{bmatrix} \cdot \\ R_r \\ \cdot \end{bmatrix} i_s$$