
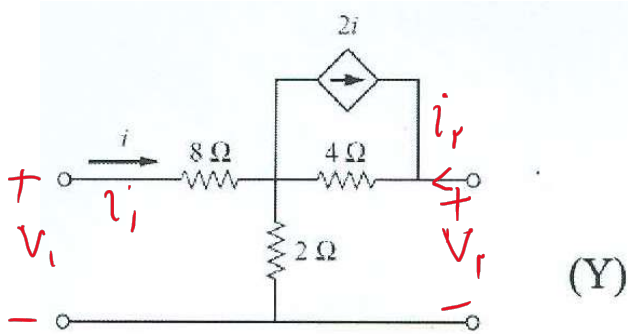


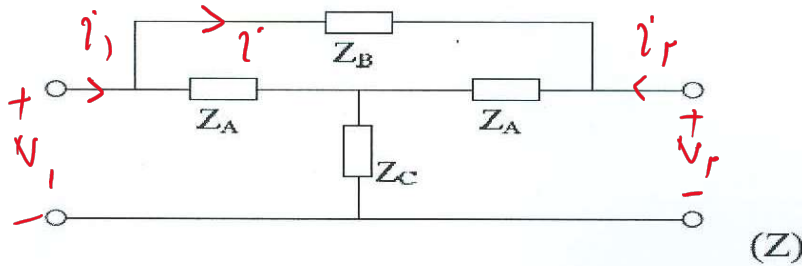


$$\begin{cases} V_i = 8I_i + 2(I_i + I_r) \\ V_r = 4(I_i + I_r) + 2(I_i + I_r) \end{cases} \rightarrow \begin{bmatrix} V_i \\ V_r \end{bmatrix} = \begin{bmatrix} 10 & 2 \\ 10 & 6 \end{bmatrix} \begin{bmatrix} I_i \\ I_r \end{bmatrix} \rightarrow \begin{bmatrix} I_i \\ I_r \end{bmatrix} = \begin{bmatrix} 10 & 2 \\ 10 & 6 \end{bmatrix}^{-1} \begin{bmatrix} V_i \\ V_r \end{bmatrix} = \frac{1}{40} \begin{bmatrix} 6 & -2 \\ -10 & 10 \end{bmatrix} \begin{bmatrix} V_i \\ V_r \end{bmatrix}$$



$$\begin{cases} V_i = Z_A(I_i - I) + Z_C(I_i - I + I_r + I) \\ V_r = Z_A(I_r + I) + Z_C(I_i - I + I_r + I) \end{cases} \rightarrow \begin{cases} V_i = Z_A(I_i - I) + Z_C(I_i + I_r) \\ V_r = Z_A(I_r + I) + Z_C(I_i + I_r) \end{cases} \quad \text{[۱]}$$

$$Z_B I = Z_A(I_i - I) - Z_A(I_r + I) \rightarrow (Z_B + 2Z_A)I = Z_A(I_i - I_r) \rightarrow I = \frac{Z_A(I_i - I_r)}{Z_B + 2Z_A} \quad \text{[۲]}$$

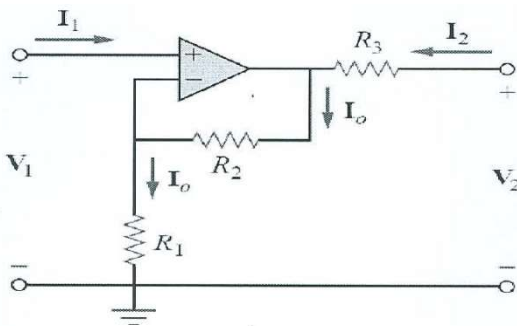
$$\text{[۱]} \rightarrow \begin{cases} V_i = (Z_A + Z_C)I_i - Z_A \frac{Z_A(I_i - I_r)}{Z_B + 2Z_A} + Z_C I_r \\ V_r = Z_C I_i + (Z_A + Z_C)I_r + Z_A \frac{Z_A(I_i - I_r)}{Z_B + 2Z_A} \end{cases} \rightarrow Z = \begin{bmatrix} Z_A + Z_C - \frac{Z_A^2}{Z_B + 2Z_A} & Z_C + \frac{Z_A^2}{Z_B + 2Z_A} \\ Z_C + \frac{Z_A^2}{Z_B + 2Z_A} & Z_A + Z_C - \frac{Z_A^2}{Z_B + 2Z_A} \end{bmatrix}$$



$$R_r I_r + (R_l + R_r) I_o = V_r, \quad R_l I_o = V_l \rightarrow R_r I_r + (R_l + R_r) \frac{V_l}{R_l} = V_r \rightarrow I_r = -\frac{R_l + R_r}{R_l R_r} V_l + \frac{1}{R_r} V_r \rightarrow$$

$$\begin{bmatrix} I_l \\ I_r \end{bmatrix} = \begin{bmatrix} \cdot & \cdot \\ -\frac{R_l + R_r}{R_l R_r} & \frac{1}{R_r} \end{bmatrix} \begin{bmatrix} V_l \\ V_r \end{bmatrix} \rightarrow Y = \begin{bmatrix} \cdot & \cdot \\ -\frac{R_l + R_r}{R_l R_r} & \frac{1}{R_r} \end{bmatrix} \rightarrow |Y| = \cdot$$

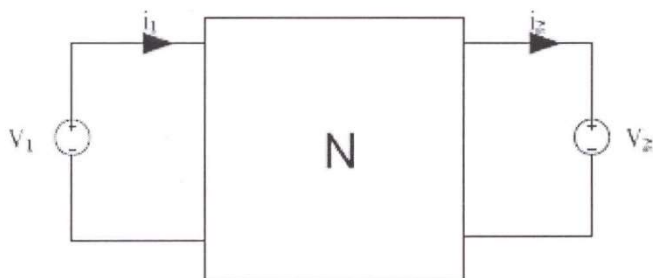۳- شبکه پسیو است. پس خاصیت هم پاسخی برقرار است.



$$V_l(t) = 2 \cdot t, \quad V_r(t) = \cdot, \quad i_l(t) = 4t, \quad i_r(t) = t$$

$$V_r(t) = 5 \cdot t + 1 \cdot, \quad V_l(t) = 2 \cdot t + 4 \cdot$$

$$V_\alpha \hat{J}_\alpha + V_\beta \hat{J}_\beta = \hat{V}_\alpha J_\alpha + \hat{V}_\beta J_\beta \rightarrow \frac{2 \cdot}{s_r} \hat{J}_\alpha + \cdot = \left(\frac{5 \cdot}{s_r} + \frac{1 \cdot}{s} \right) \left(-\frac{4}{s_r} \right) + \left(\frac{2 \cdot}{s_r} + \frac{4 \cdot}{s} \right) \left(\frac{1}{s_r} \right) \rightarrow \hat{J}_\alpha = -\frac{9}{s_r} \rightarrow I_l = \frac{9}{s_r} \rightarrow$$

$$i_l = 9t$$