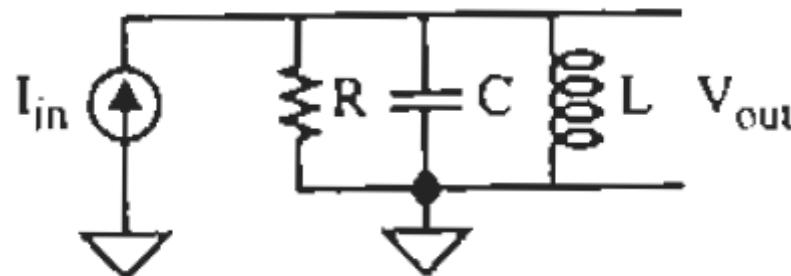


Passive RLC Networks

Parallel RLC Tank



$$Y = G + j\omega C + \frac{1}{j\omega L} = G + j\left(\omega C - \frac{1}{\omega L}\right)$$

Resonant Frequency: $\left(\omega_0 C - \frac{1}{\omega_0 L}\right) = 0 \implies \omega_0 = \frac{1}{\sqrt{LC}}$.

$L=1 \text{ nH}, C=1 \text{ pF} \rightarrow f=5 \text{ GHz}$

Q (Quality Factor)

$$Q \equiv \omega \frac{\text{energy stored}}{\text{average power dissipated}}.$$

$$E_{\text{tot}} = \frac{1}{2} C (I_{\text{pk}} R)^2$$

$$P_{\text{avg}} = \frac{1}{2} I_{\text{pk}}^2 R$$

$$Q = \omega_0 \frac{E_{\text{tot}}}{P_{\text{avg}}} = \frac{1}{\sqrt{LC}} \frac{\frac{1}{2} C (I_{\text{pk}} R)^2}{\frac{1}{2} I_{\text{pk}}^2 R} = \frac{R}{\sqrt{L/C}}$$


The quantity $\sqrt{L/C}$ has the dimensions of resistance and is sometimes called the *characteristic impedance* of the network.

It is Proven that: $Q = \frac{\omega_o}{\text{BW}}$

Series RLC Network

$$Q = \frac{\sqrt{L/C}}{R}$$

Q of the Capacitor and Inductor

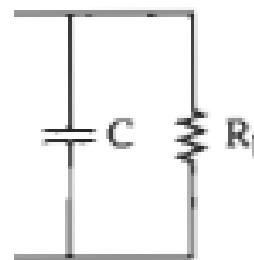

A circuit diagram showing a vertical loop with a capacitor labeled C in the top-left position and an inductor labeled R_p in the top-right position.

\longrightarrow

$$Q = R_p C \omega_o$$





A circuit diagram showing a vertical loop with an inductor labeled L_s in the top-left position and a resistor labeled R_s in the bottom-right position.

\longrightarrow

$$Q = \frac{L \omega_o}{R_s}$$

Equivalent Series and Parallel Circuits

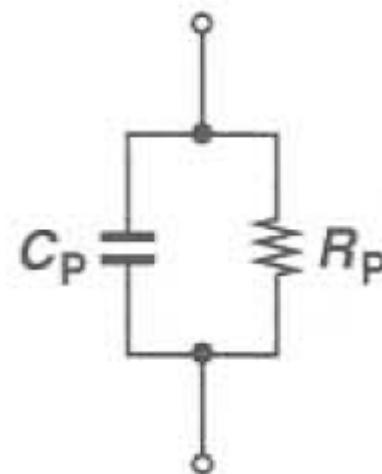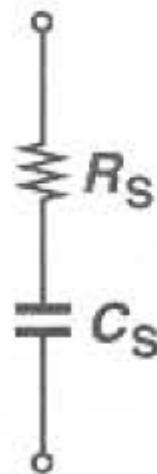

$$\frac{R_P}{R_P C_{PS} + 1} = \frac{R_S C_{SS} + 1}{C_{SS}}$$

$$[1 - R_s C_s R_p C_p \omega^2] + j\omega [R_s C_s + R_p C_p - R_p C_s] = 0$$

$$[1 - R_s C_s R_p C_p \omega^2] = 0 \implies Q_s = Q_p = Q = \frac{1}{R_s C_s \omega} = R_p C_p \omega$$



$$j\omega \left[\frac{1}{Q \omega} + \frac{Q}{\omega} - R_p C_s \right] = 0$$

$$R_p = \frac{1}{C_s \omega} \left[\frac{1+Q^2}{Q} \right]$$

↗

$$R_p = R_s (1 + Q^2)$$


Equivalent Series and Parallel Circuits

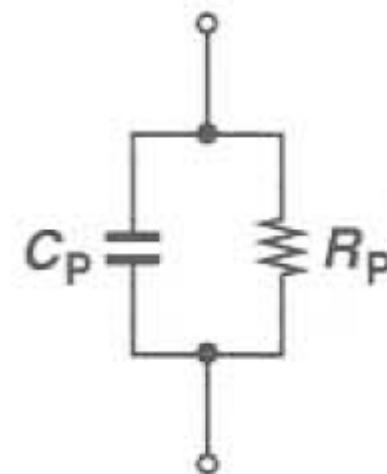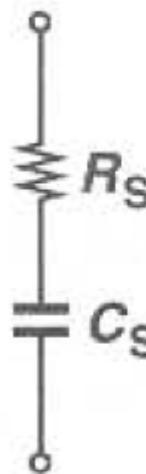

$$\frac{R_P}{R_P C_{PS} + 1} = \frac{R_S C_{SS} + 1}{C_{SS}}$$



$$R_p = \frac{1}{C_s \omega} \left[\frac{1 + Q^2}{Q} \right]$$
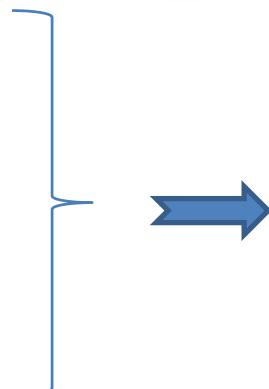
$$Q = R_p C_p \omega = \frac{1}{C_s \omega} \left[\frac{1 + Q^2}{Q} \right] C_p \omega$$



$$C_p = \left[\frac{Q^2}{1 + Q^2} \right] C_s$$

Equivalent Series and Parallel Circuits

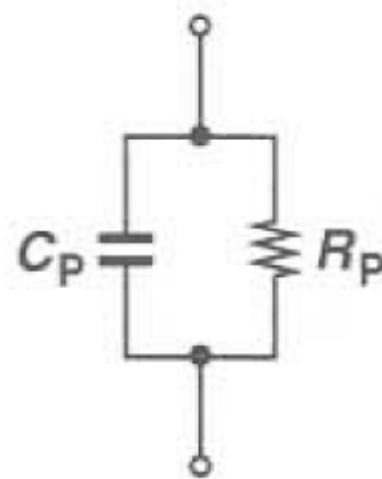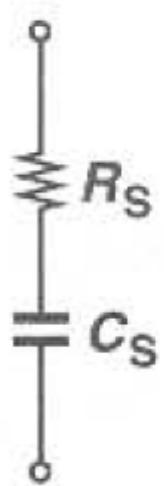


$$\frac{R_P}{R_P C_{PS} + 1} = \frac{R_S C_{SS} + 1}{C_{SS}}$$

If $Q^2 \gg 1$



$$R_p \cong R_s Q^2$$
$$C_p \cong C_s$$

Equivalent Series and Parallel Circuits

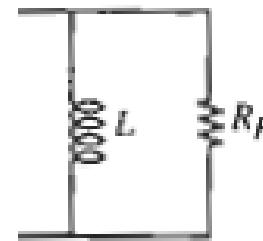

$$R_P = R_S(1 + Q^2)$$


$$L_P = L_S \left(\frac{1 + Q^2}{Q^2} \right)$$

If: $Q^2 \gg 1$


$$R_P \approx R_S Q^2 = \frac{L_S^2 \omega^2}{R_S}$$

$$L_P \approx L_S$$

The L-Match

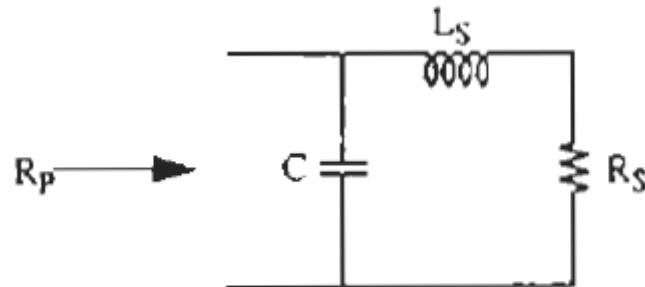



Upward Impedance Transformer

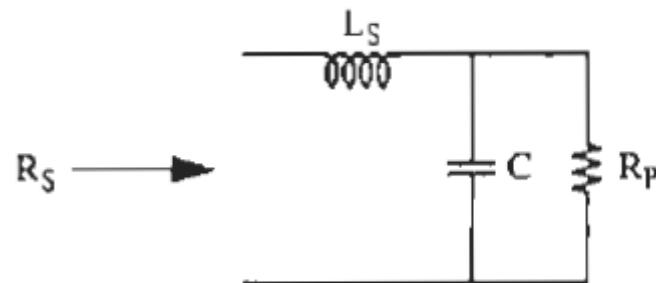

Downward Impedance Transformer


there are only two degrees of freedom (one can choose only L and C).

The π -Match

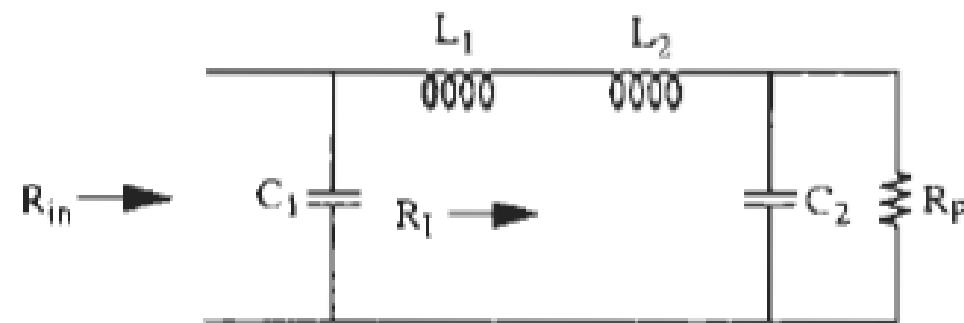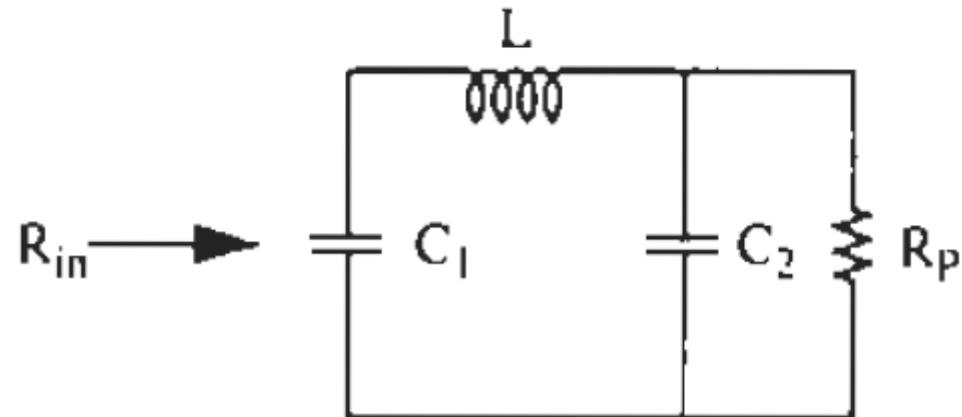


Π -match as cascade of L-matches

The T-Match

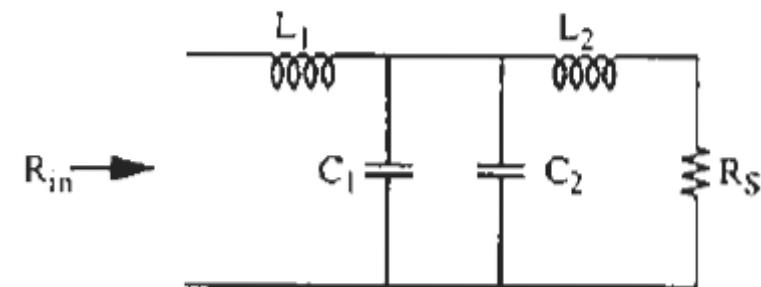

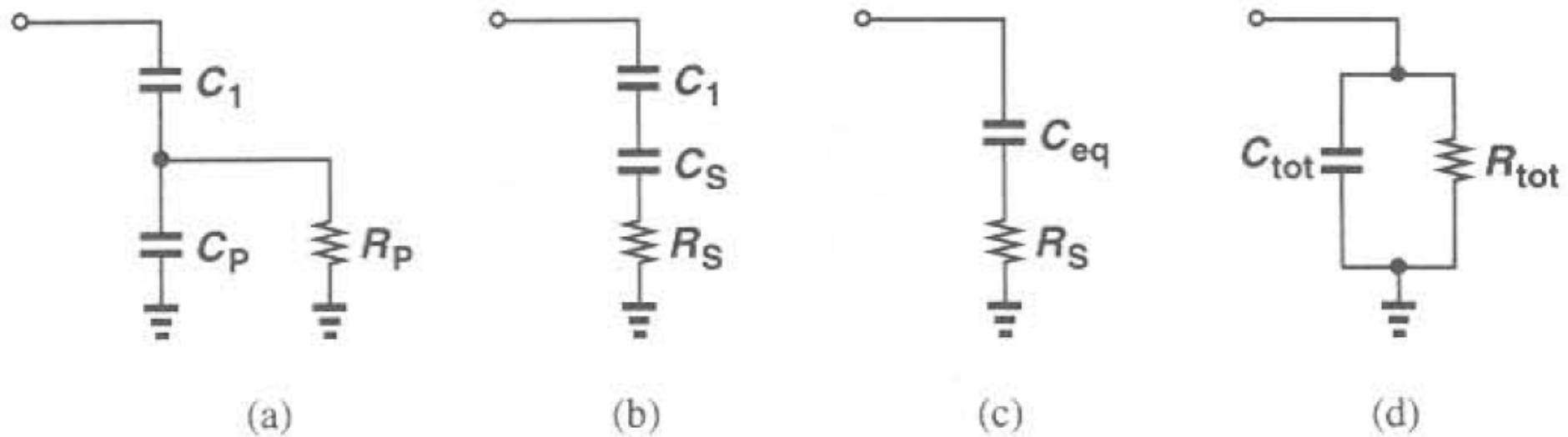
Impedance Transformation by Means of a Capacitor Divider




$$C_{tot} \approx C_1 C_P / (C_1 + C_P)$$

$$R_{tot} \approx 1/[R_S(C_{eq}\omega)^2] = (1+C_P/C_1)^2 R_P$$

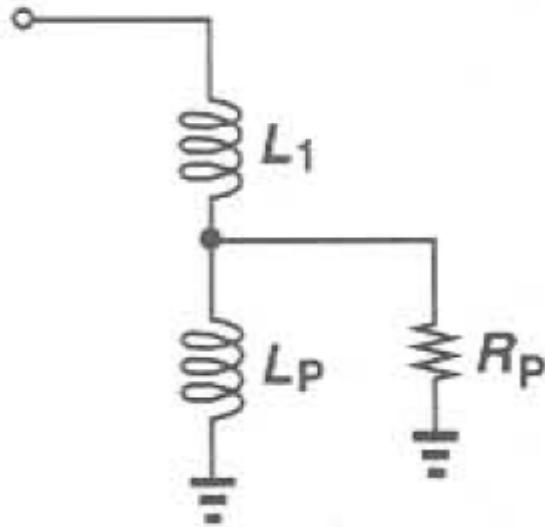Impedance Transformation by Means of an Inductor Divider



(a)

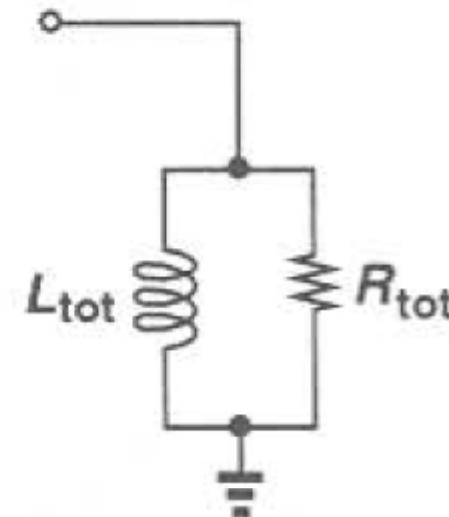


(b)

$$L_{\text{tot}} \approx L_1 + L_P$$


$$R_{\text{tot}} \approx (1 + L_1/L_P)^2 R_P$$

Tapped Capacitor Match

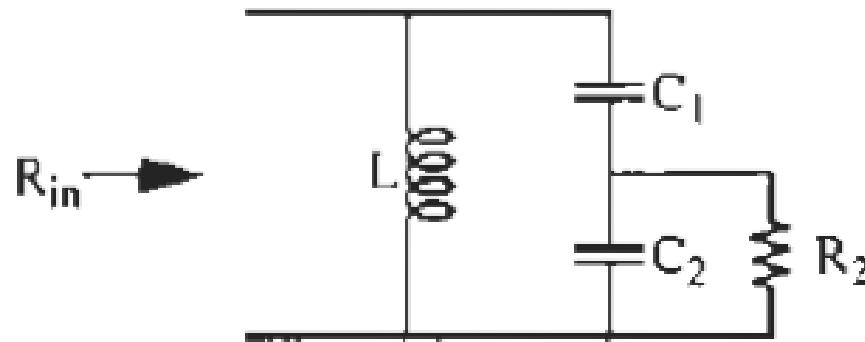


Tap: an intermediate point in an electric circuit where a connection may be made.

Tapped Inductor Match


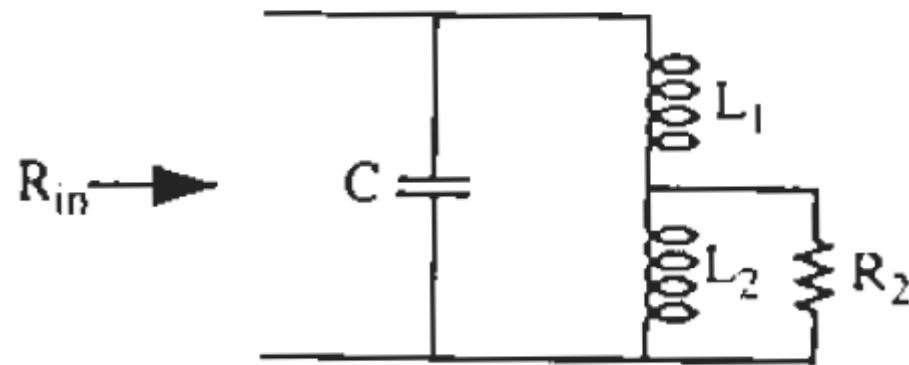


Double-Tapped Match

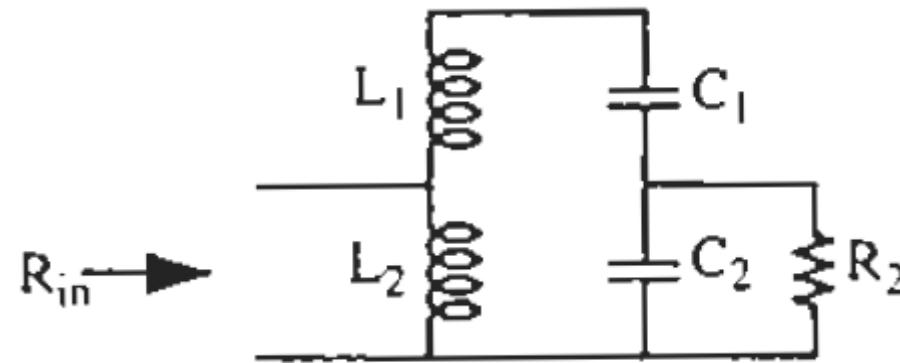

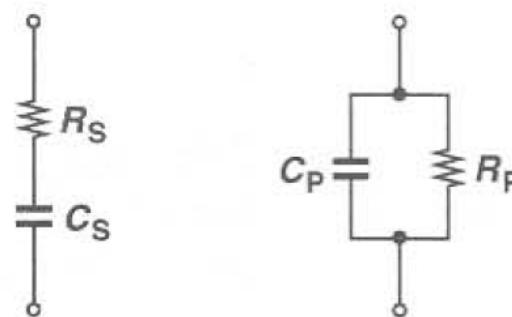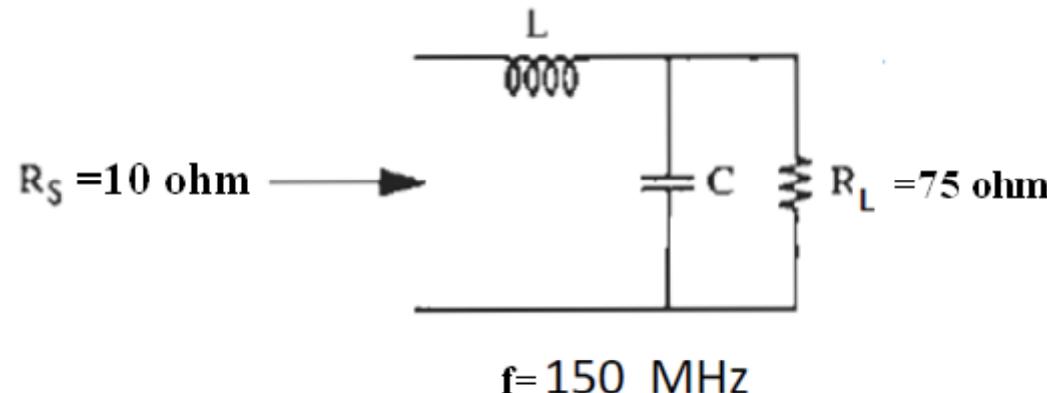Example#1

Determine L, C in order to have good matching between R_L and R_s . BW=?



$$R_p = R_s(1 + Q^2)$$

$$C_p \cong C_s$$

$$\frac{R_L}{R_s} = 1 + Q_1^2 \quad \xrightarrow{yields} \quad 7.5 = 1 + Q_1^2 \quad \xrightarrow{yields} Q_1 = 2.55$$

$$Q_1 = R_L C W$$

$$2.55 = 75 \times C \times 2 \times \pi \times 150 \times (10^6) \quad \xrightarrow{yields} C = 36.075 \text{ PF}$$

$$LC\omega^2 = 1$$



$$L \times 36 \text{ p} \times (2\pi \times 150 \text{ MHz})^2 = 1$$

$$L = 31nH$$

$$Q_1 = \frac{W}{BW} \quad \xrightarrow{yields} \quad 2.55 = \frac{150 \text{ MHz}}{BW} \quad \xrightarrow{yields} \quad BW = 58.8 \text{ MHz}$$

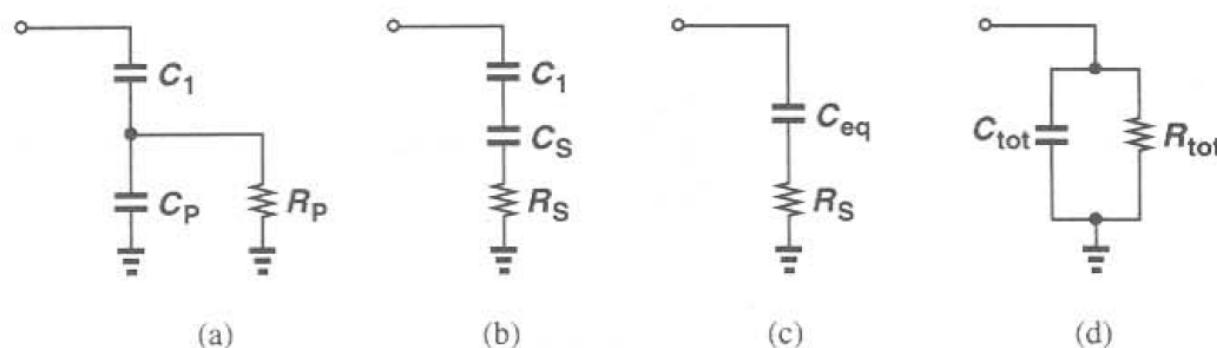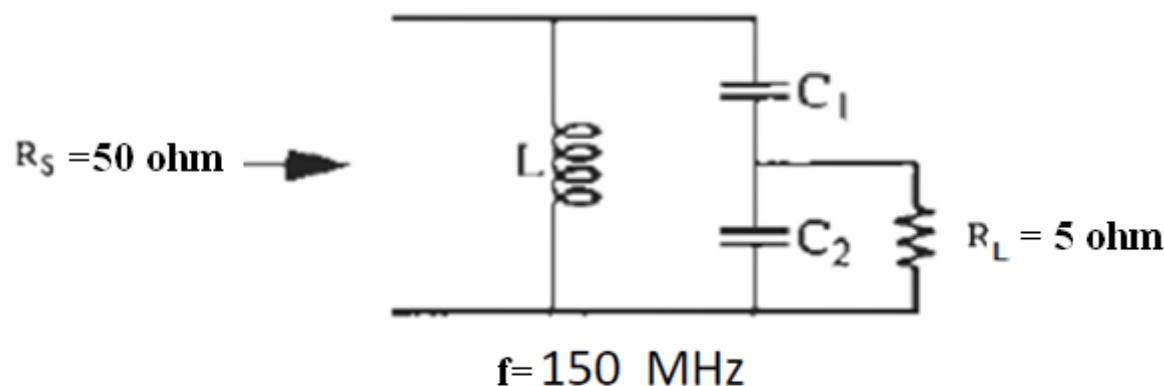Example#2

Determine L, C1, C2 in order to have good matching between R_L and R_s over the 15 MHz bandwidth.



$$C_{tot} \approx C_1 C_P / (C_1 + C_P)$$

$$R_{tot} \approx 1/[R_S(C_{eq}\omega)^2] = (1 + C_P/C_1)^2 R_P$$

$$Q = \frac{\omega}{BW} = \frac{2\pi \times 150MHz}{2\pi \times 15MHz} = 10$$

Parallel RLC : $Q = \frac{Rs}{\sqrt{\frac{L}{C_{tot}}}}$ $10 = \frac{50}{\sqrt{\frac{L}{C_{tot}}}}$

$$\rightarrow \sqrt{\frac{L}{C_{tot}}} = 5$$

$LC_{tot}\omega^2 = 1$

$\omega = 2\pi \times 150MHz$

$L = 5.3 \text{ nH}$ $C_{tot} = 212 \text{ pF}$

$$R_{tot} = \left(1 + \frac{C_2}{C_1}\right)^2 \times R_L \longrightarrow 10 = \left(1 + \frac{C_2}{C_1}\right)^2 \xrightarrow{\text{yields}} \frac{C_2}{C_1} = 2.16$$

$$C_{tot} \approx C_1 \times \frac{C_2}{C_1 + C_2} = 212PF \xrightarrow{\text{yields}} 212PF = \frac{C_2}{1 + \frac{C_2}{C_1}} \xrightarrow{\text{yields}} C_2 = 670PF$$

$$C_1 = 310PF$$