



Voltage and Current References

Bandgap References

The objective of reference generation is to establish a dc voltage or current with following characteristics:


- Independent of the supply and process.
- Having a well-defined behavior with temperature.
 - Temperature independent.

Supply-Independent Biasing

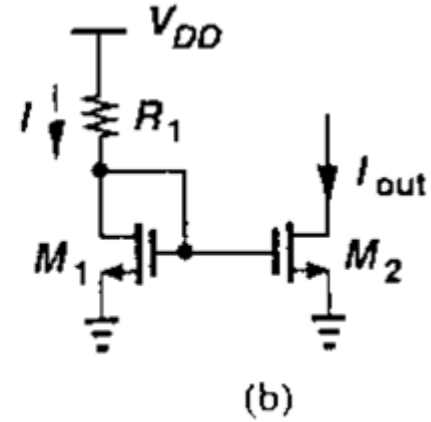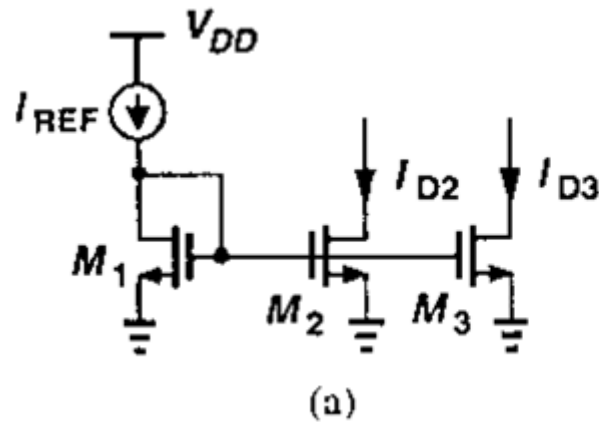

- ❖ In the design of current sources, we need to a **golden current source**, I_{REF} . (Figure (a))
- ❖ If instead of I_{REF} we use a resistor, the generated current sources will be supply-dependent. (Figure (b))

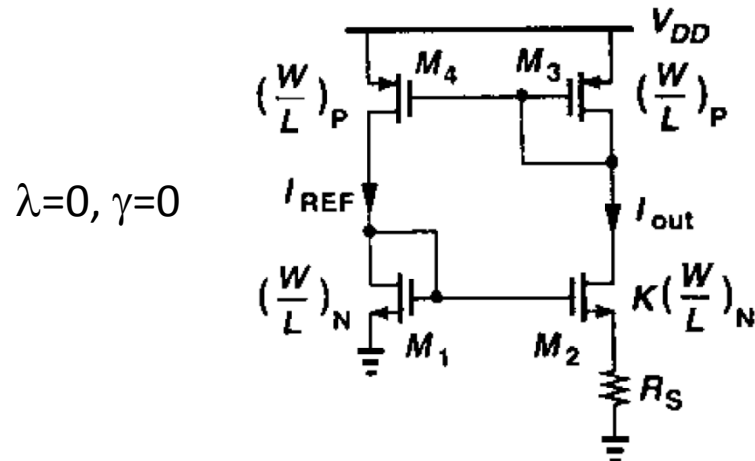A Simple Circuit to Establish Supply-Independent Current Supply-Independent Biasing




$$\sqrt{\frac{2I_{out}}{\mu_n C_{ox}(W/L)_N}} + V_{TH1} = \sqrt{\frac{2I_{out}}{\mu_n C_{ox}K(W/L)_N}} + V_{TH2} + I_{out}R_S$$

$$\sqrt{\frac{2I_{out}}{\mu_n C_{ox}(W/L)_N}} \left(1 - \frac{1}{\sqrt{K}}\right) = I_{out}R_S$$

$$I_{out} = \frac{2}{\mu_n C_{ox}(W/L)_N} \cdot \frac{1}{R_S^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

The current is independent of the supply voltage but it is still a function of process and temperature.


Start-up Problem

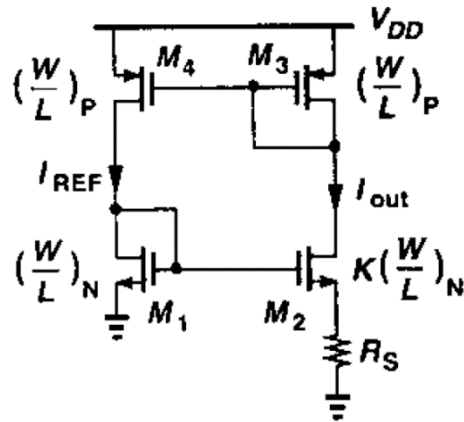

$I_{out}=0$ is another operating point of the above circuit because it satisfies the following equation. We call this problem as the start-up problem.

$$\sqrt{\frac{2I_{out}}{\mu_n C_{ox} (W/L)_N}} + V_{TH1} = \sqrt{\frac{2I_{out}}{\mu_n C_{ox} K(W/L)_N}} + V_{TH2} + I_{out} R_S$$

Addition of the Start-up devices

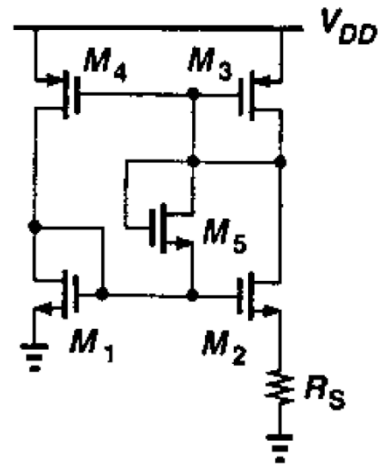

this technique is practical only if $V_{TH1} + V_{TH5} + |V_{TH3}| < V_{DD}$
and $V_{GS1} + V_{TH5} + |V_{GS3}| > V_{DD}$

Temperature-Independent References

if two quantities having opposite temperature coefficients (TCs) are added with proper weighting, the result displays a zero TC. For example.

$$V_{REF} = \alpha_1 V_1 + \alpha_2 V_2,$$

$$\alpha_1 \partial V_1 / \partial T + \alpha_2 \partial V_2 / \partial T = 0$$

Negative-TC Voltage

The base-emitter voltage of bipolar transistors or, more generally, the forward voltage of a *pn*-junction diode exhibits a negative TC.

$$I_C = I_S \exp(V_{BE}/V_T)$$
$$V_T = kT/q$$
$$I_S = bT^{4+m} \exp \frac{-E_g}{kT}$$
$$m \approx -3/2$$

b is a proportionality factor.

We assume that I_C is held constant.

$$V_{BE} = V_T \ln(I_C/I_S)$$
$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} - \frac{V_T}{I_S} \frac{\partial I_S}{\partial T}$$
$$\frac{\partial I_S}{\partial T} = b(4+m)T^{3+m} \exp \frac{-E_g}{kT} + bT^{4+m} \left(\exp \frac{-E_g}{kT} \right) \left(\frac{E_g}{kT^2} \right)$$
$$\frac{V_T}{I_S} \frac{\partial I_S}{\partial T} = (4+m) \frac{V_T}{T} + \frac{E_g}{kT^2} V_T$$


Continued

$$\begin{aligned}\frac{\partial V_{BE}}{\partial T} &= \frac{V_T}{T} \ln \frac{I_C}{I_S} - (4 + m) \frac{V_T}{T} - \frac{E_g}{kT^2} V_T \\ &= \frac{V_{BE} - (4 + m)V_T - E_g/q}{T}.\end{aligned}$$

With $V_{BE} \approx 750 \text{ mV}$ and $T = 300^\circ\text{K}$, $\partial V_{BE}/\partial T \approx -1.5 \text{ mV}/^\circ\text{K}$.

Positive-TC Voltage

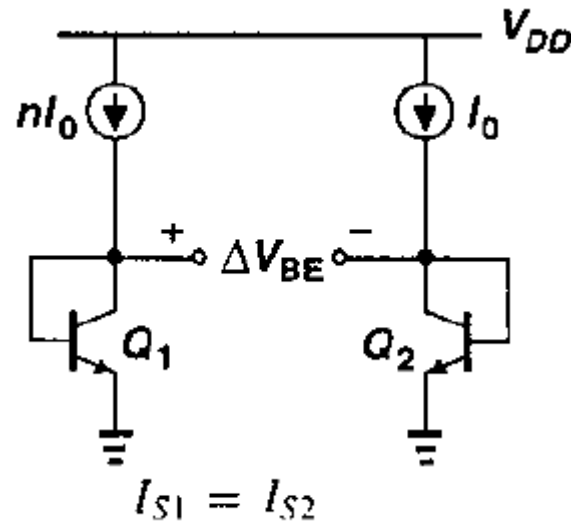
if two bipolar transistors operate at unequal current densities, then the *difference* between their base-emitter voltages is directly proportional to the absolute temperature.



Generation of PTAT voltage.

$$\begin{aligned}\Delta V_{BE} &= V_{BE1} - V_{BE2} \\ &= V_T \ln \frac{nI_0}{I_{S1}} - V_T \ln \frac{I_0}{I_{S2}} \quad \longrightarrow \quad \frac{\partial \Delta V_{BE}}{\partial T} = \frac{k}{q} \ln n. \\ &= V_T \ln n.\end{aligned}$$


Continued

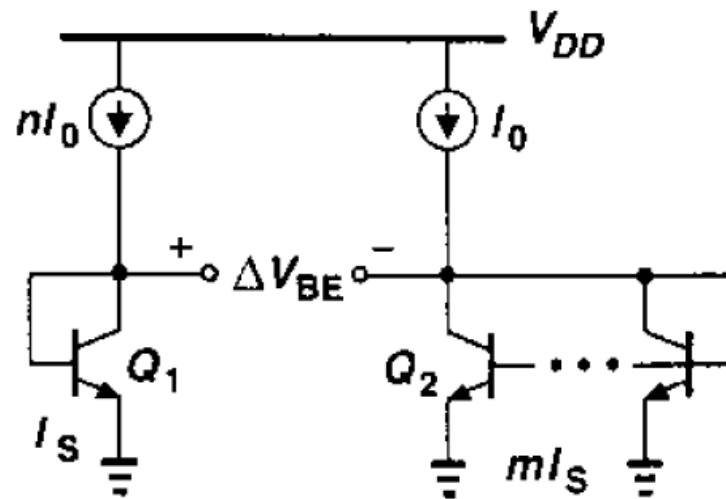

$$\begin{aligned}\Delta V_{BE} &= V_{BE1} - V_{BE2} \\ &= V_T \ln \frac{nl_0}{I_S} - V_T \ln \frac{I_0}{mI_S} \\ &= V_T \ln(nm).\end{aligned}$$

$$\frac{\partial \Delta V_{BE}}{\partial T} = (k/q) \ln(nm).$$

Bandgap References

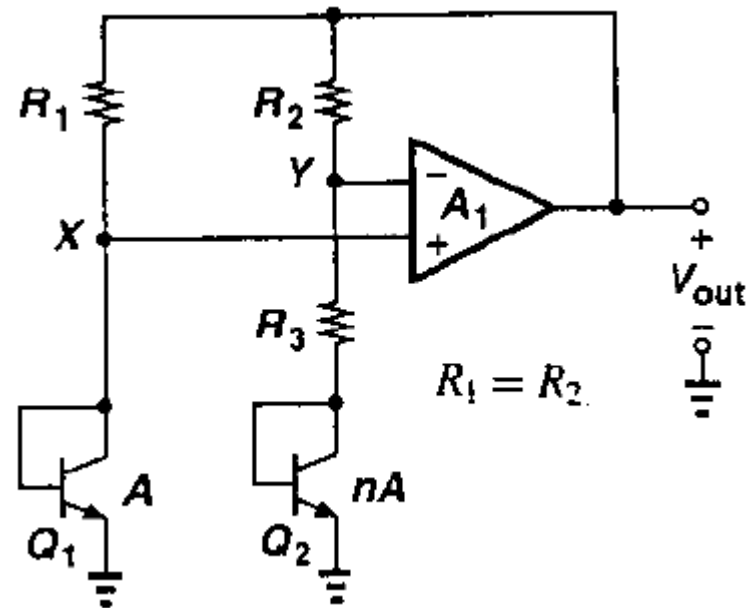


$$V_X \cong V_Y \Rightarrow \frac{V_{out} - V_X}{R_1} \cong \frac{V_{out} - V_Y}{R_2} \Rightarrow I_{C1} = I_{C2}$$



$$V_{BE1} - V_{BE2} = V_T \ln n$$


Continued

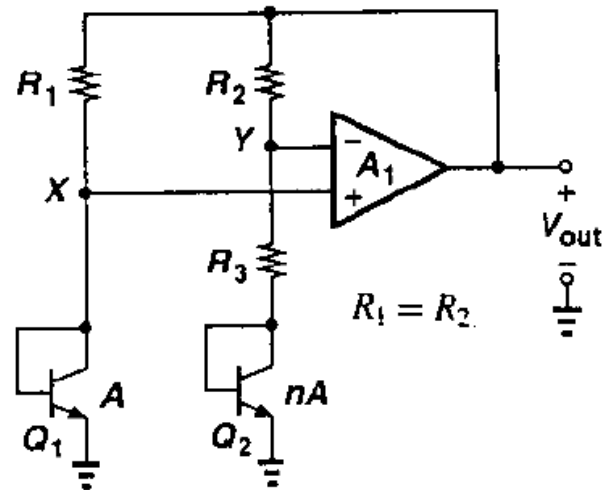

$$\left. \begin{aligned} V_{out} &= V_{BE1} + R_1 I_{C1} \\ V_{out} &= V_{BE2} + (R_2 + R_3) I_{C2} \\ I_{C1} &= I_{C2} \end{aligned} \right\} \Rightarrow \Delta V_{BE} = V_{BE1} - V_{BE2} = R_3 I_{C2} \Rightarrow I_{C2} = \frac{\Delta V_{BE}}{R_3}$$

$$V_{out} = (R_2 + R_3) I_{C2} + V_{BE2} = \left(1 + \frac{R_2}{R_3} \right) \Delta V_{BE} + V_{BE2}$$

Continued

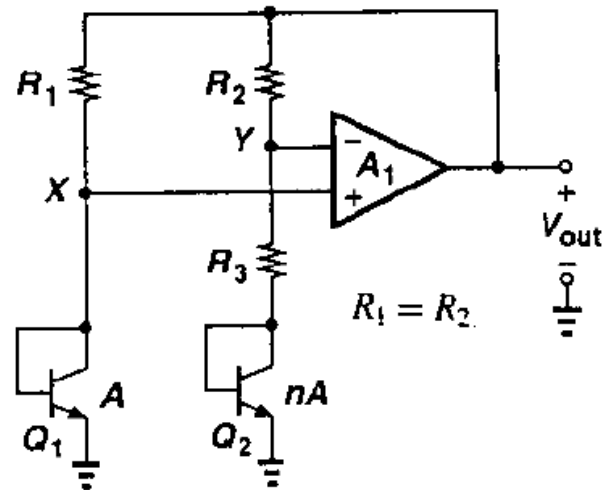


$$V_{out} = \left(1 + \frac{R_2}{R_3}\right) \Delta V_{BE} + V_{BE2} = \left(1 + \frac{R_2}{R_3}\right) V_T \ln(n) + V_{BE2}$$

$$\frac{\partial V_{out}}{\partial T} = 0 \Rightarrow \left(1 + \frac{R_2}{R_3}\right) \frac{k}{q} \ln(n) = -\frac{\partial V_{BE2}}{\partial T}$$



$$\left(1 + \frac{R_2}{R_3}\right) \frac{k}{q} \ln(n) = 1.5 \frac{mV}{^\circ K}$$


Continued

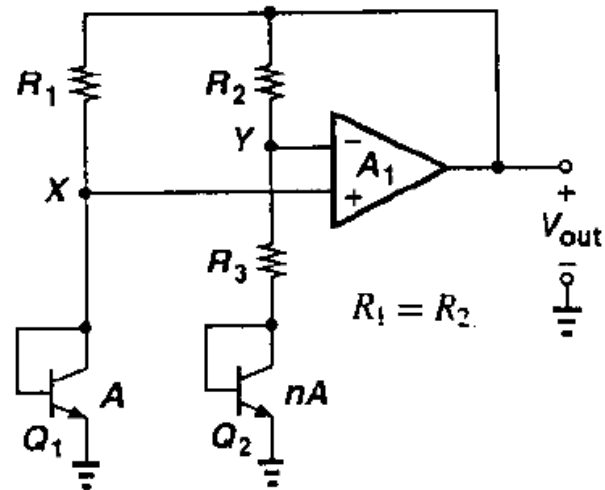

Assuming $V_{BE2}=750\text{mV}$, we have:

$$V_{out} = \left(1 + \frac{R_2}{R_3}\right) V_T \ln(n) + V_{BE2} = 1.5 \frac{\text{mV}}{\text{°K}} \times 300 + 750\text{mV} = 1.2\text{V}$$


Compatibility with CMOS Technology

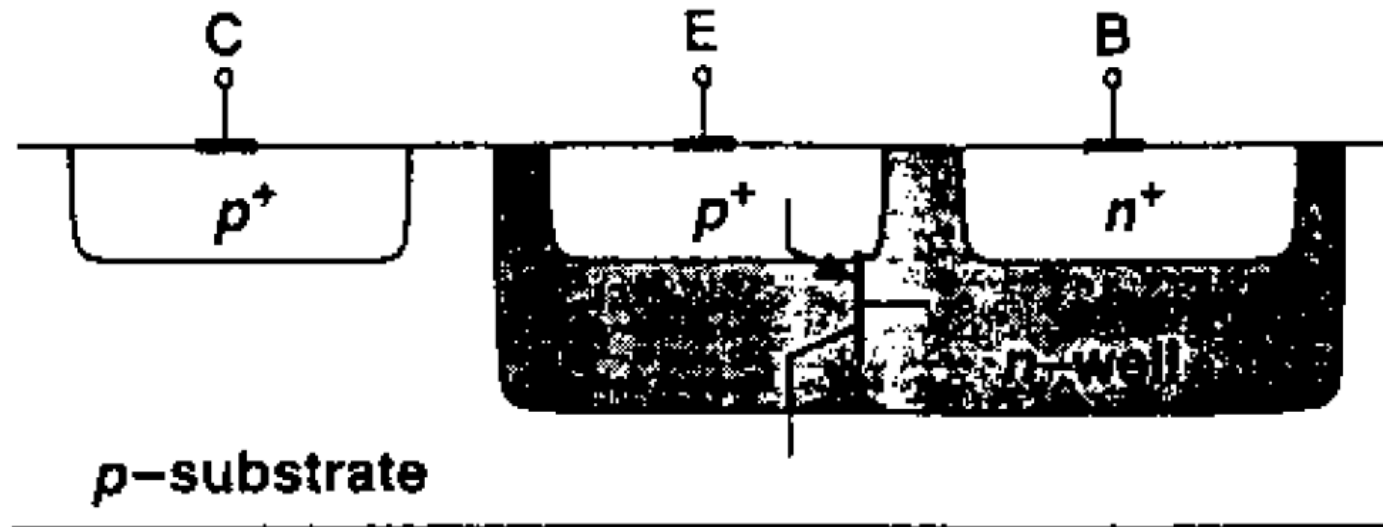


Realization of a *pnp* bipolar transistor in CMOS technology.

The *p*-type substrate acts as the collector and it is inevitably connected to the most negative supply (usually ground).

Modified Bandgap Circuit

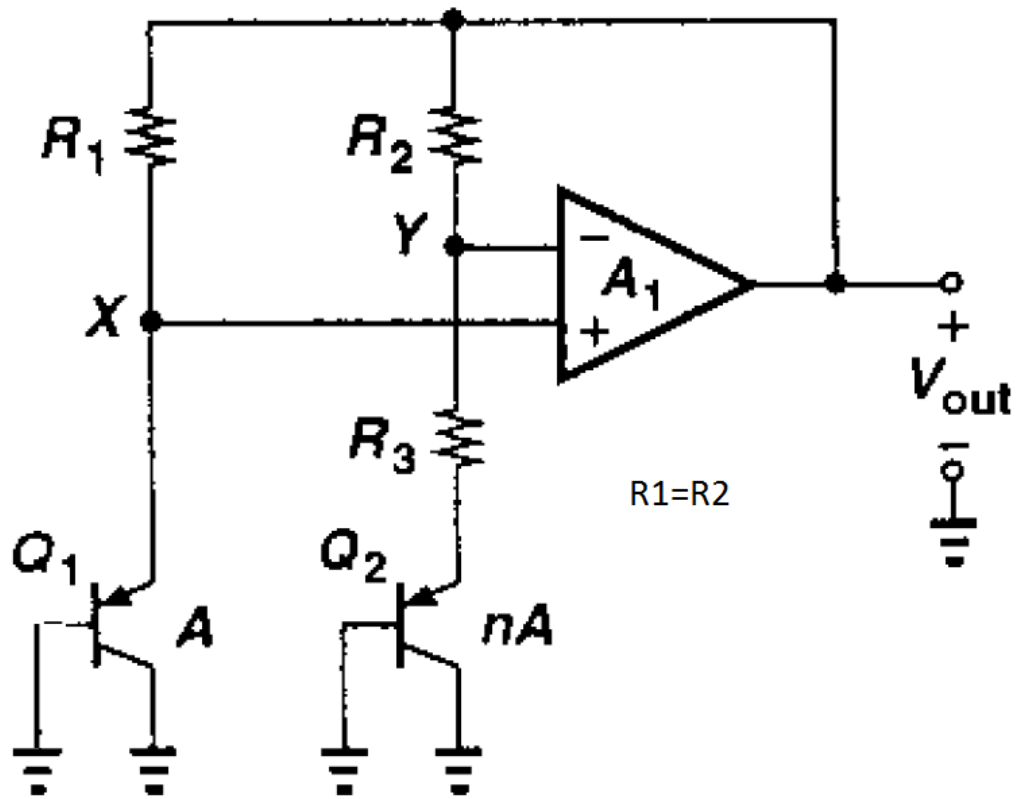


Bandgap Circuit ($V_{out}=2.5V$)

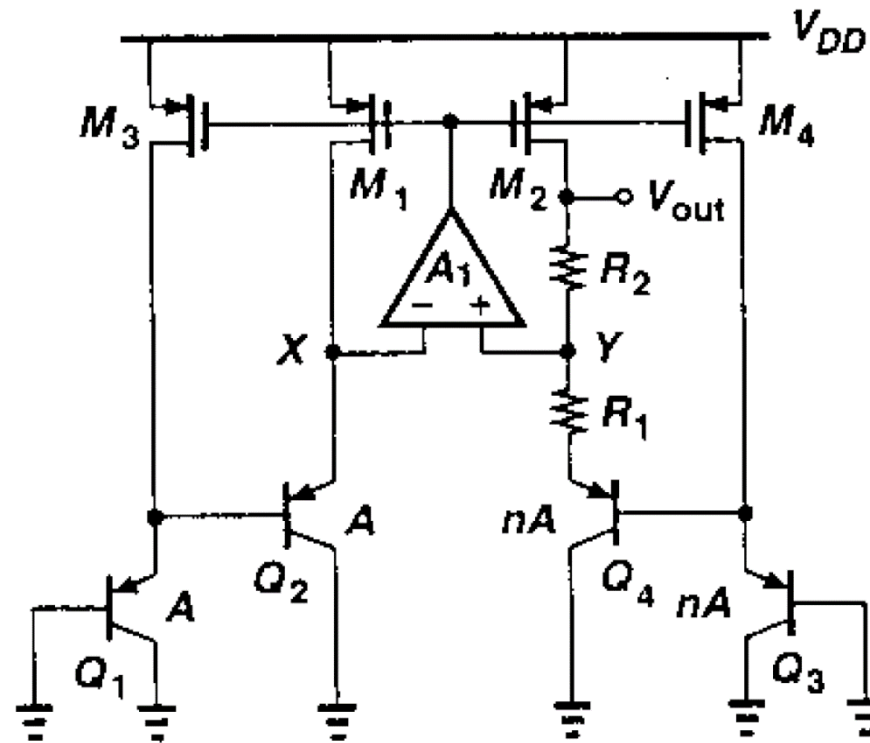

$$V_{out} = V_{EB3} + V_{EB4} + 2 \left(1 + \frac{R_2}{R_1} \right) V_T \ln(n)$$

The drawback of the above circuit is that $V_{DS1} \neq V_{DS2}$. Therefore I_{D1} is not accurately identical to I_{D2} .

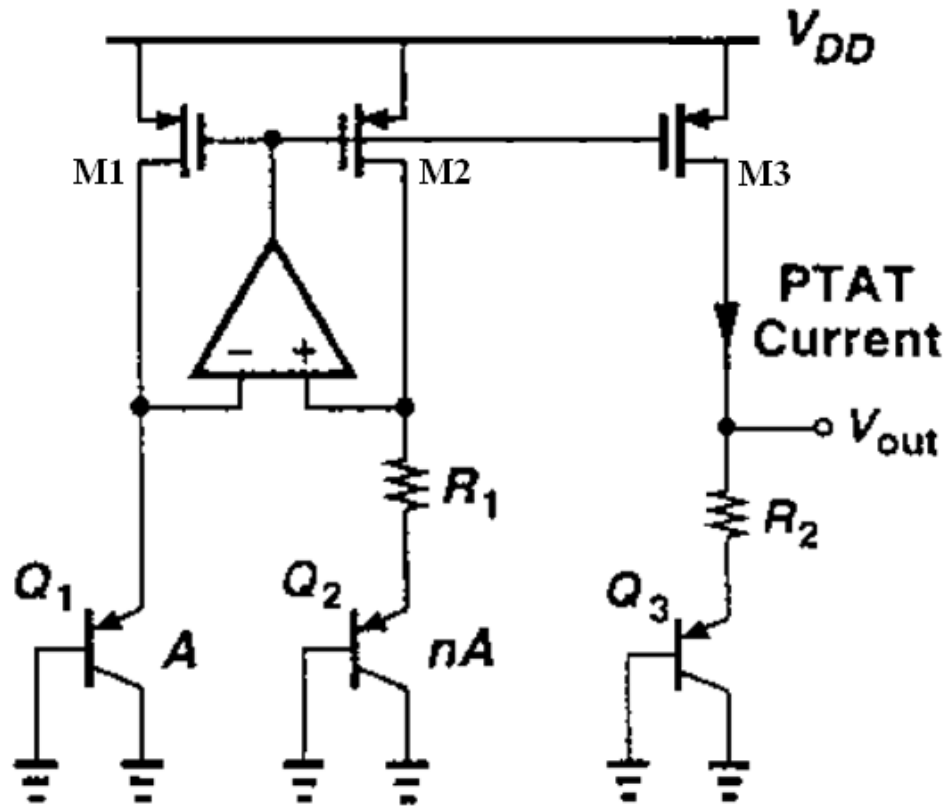
Employing PTAT to Generate Temperature-Independent Voltage




$$V_{out} = V_{EB3} + R_2 \frac{V_T \ln(n)}{R_1}$$

The advantage of the above circuit is that $V_{DS1} = V_{DS2}$. Therefore I_{D1} is accurately identical to I_{D2} .

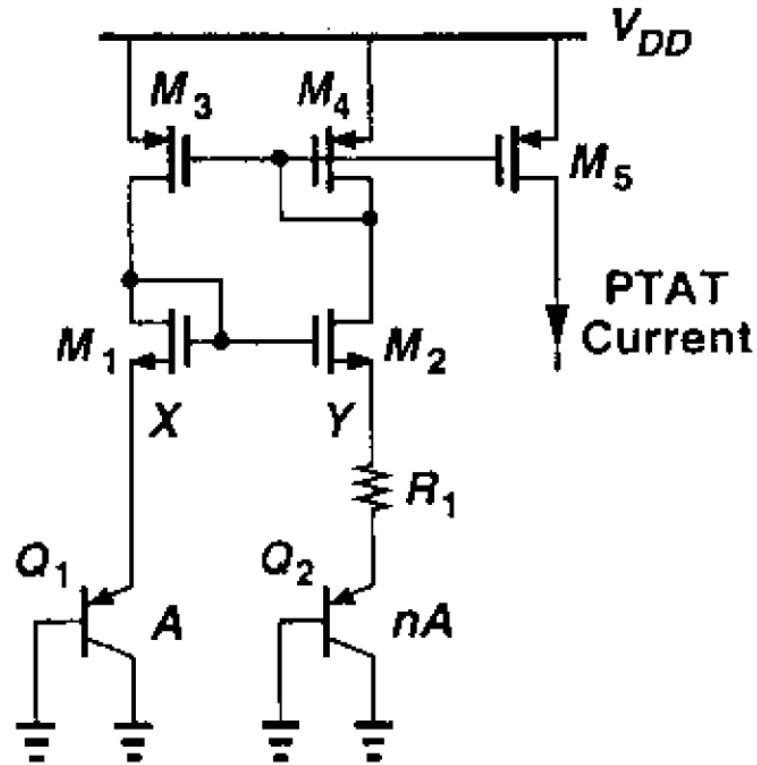
Generation of a PTAT Current Using a Simple Amplifier



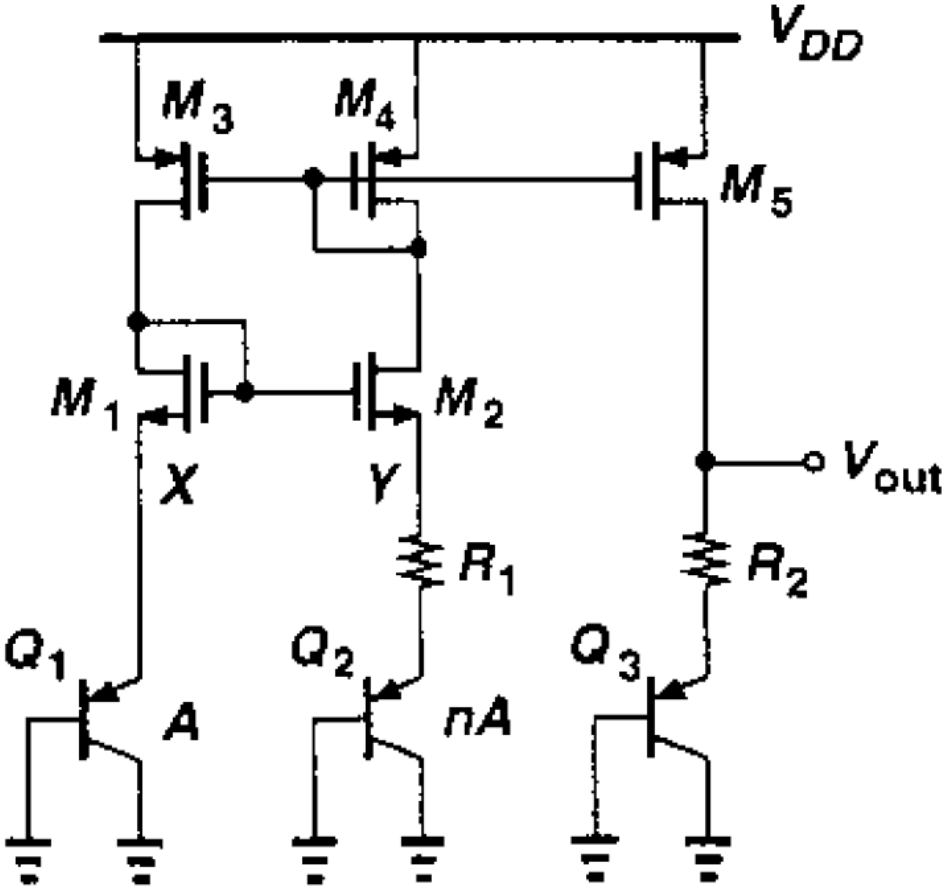Generation of a Temperature-Independent Voltage



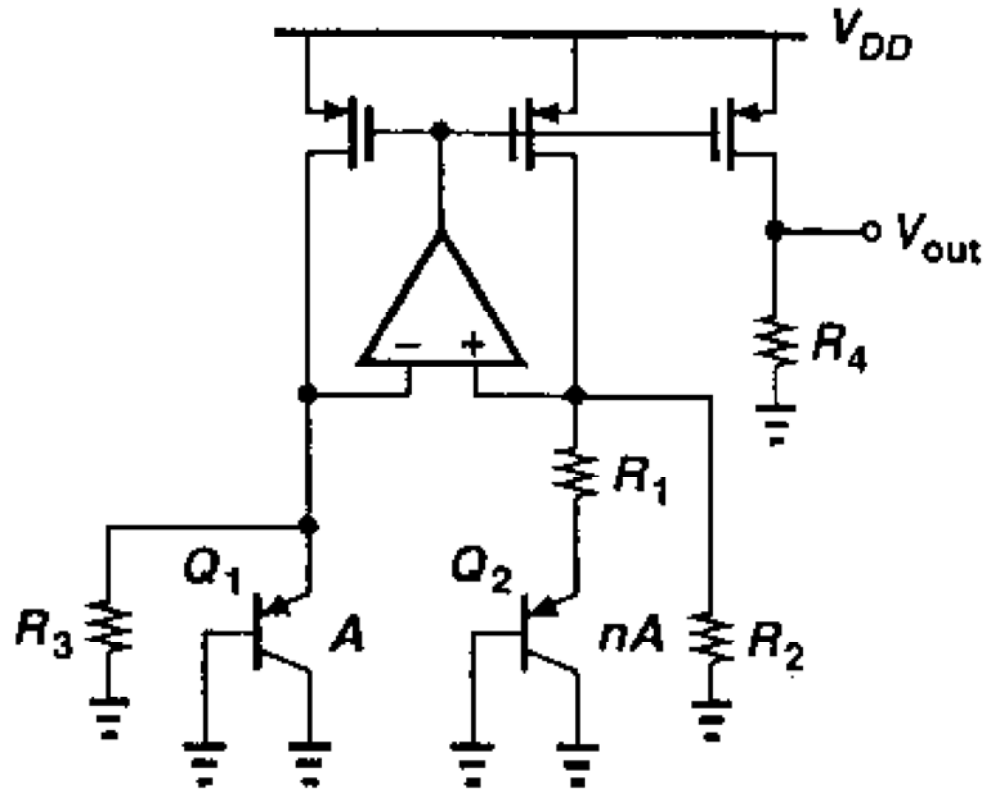
Generation of a Temperature-Independent Voltage



$$V_{out} = \frac{R_4}{R_2} V_{EB1} + \frac{R_4}{R_1} V_T \ln(n)$$

This circuit is useful to generate low reference voltages.

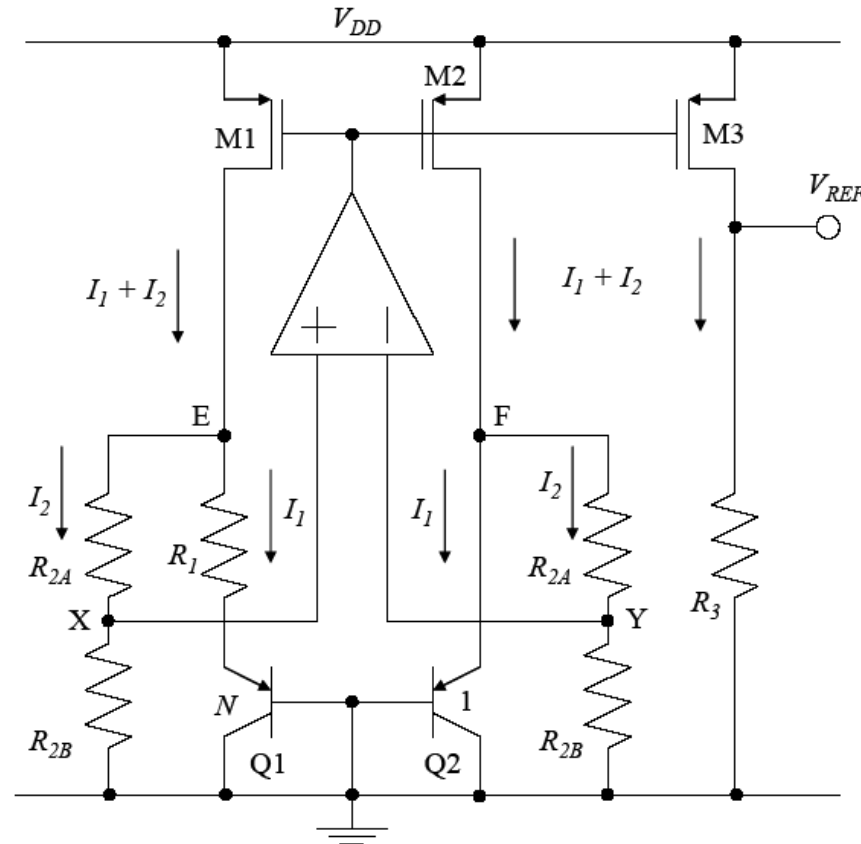
Generation of a Temperature-Independent Voltage




$$V_{REF} = \frac{R_3}{R_2} \left(V_{EB2} + \frac{R_2}{R_1} V_T \ln(N) \right)$$

This circuit is useful to generate low reference voltages.

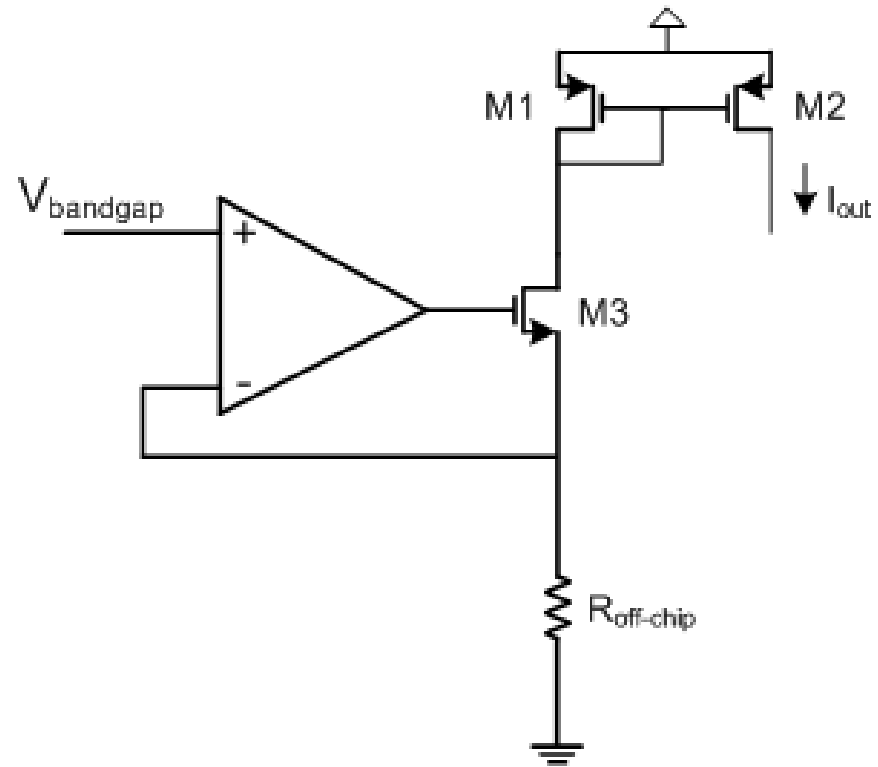Temperature-independent Current Generation



Constant-Gm Biasing

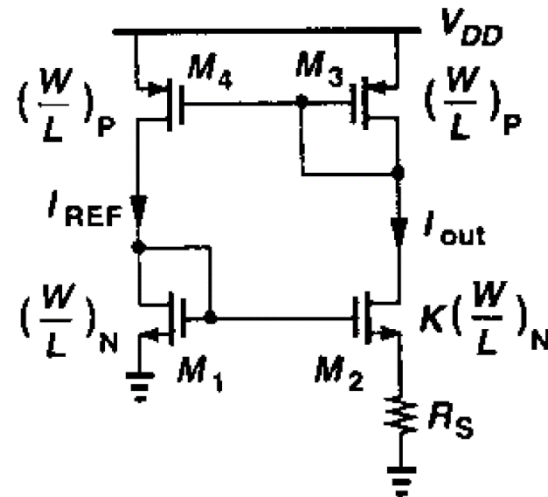


$$I_{out} = \frac{2}{\mu_n C_{ox} (W/L)_N R_S^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

$$\begin{aligned} g_{m1} &= \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_N I_{D1}} \\ &= \frac{2}{R_S} \left(1 - \frac{1}{\sqrt{K}}\right), \end{aligned}$$

The resistor R_S is an off-chip resistor.

Continued

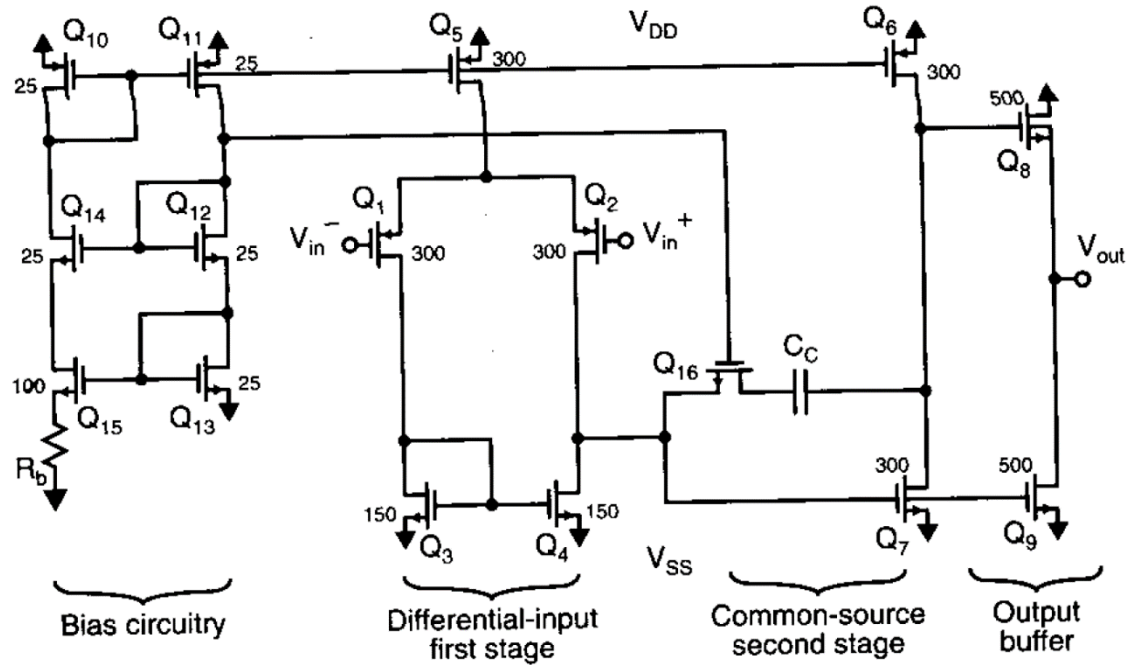

$$I_{D10} = \frac{2}{\mu_n C_{ox} \left(\frac{W}{L}\right)_{13}} \frac{1}{R_b^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2, \quad K = \frac{\left(\frac{W}{L}\right)_{15}}{\left(\frac{W}{L}\right)_{13}}$$

This opamp utilizes the constant-Gm biasing. R_b is an off-chip resistor.