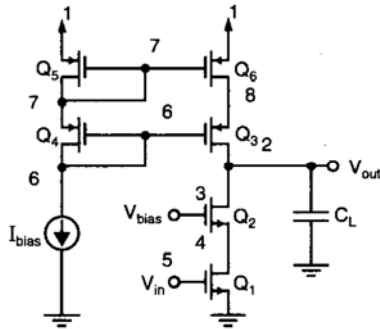


*In the Name of God*  
**K.N. Toosi University of Technology**  
 Electrical Faculty  
 Analog Electronics II  
 Spring 2017

**Project#1 (Cascode Amplifier Design)**

Making use of both ADS and 0.18 $\mu\text{m}$  CMOS technology, simulate the following circuit.



	W( $\mu\text{m}$ )	L( $\mu\text{m}$ )
M1, M2	4	0.18
M3, M6	45	0.18
M4, M5	30	0.18

$$V_{dd} = 1.8V, I_{bias} = 100 \mu A, V_{bias} = 0.9V, C_L = 5 pF$$

- In order to set the dc voltage of the output of the amplifier to 0.9 V, find a proper dc voltage for the input signal.
  - Why is  $V_{out}(dc)$  too much sensitive to  $V_{in}(dc)$ ?
  - Making use of "DC Simulation", report the following parameters for each transistor.  
 $I_D, g_m, V_{DS}, V_{GS}, V_{DSat}, V_{th}, r_{ds}, C_{gs}, C_{gd}, C_{db}, C_{sb}$
  - Making use of "Transient Simulation", find the amplitude of the input sinusoidal signal so that  $V_o(ac) = 0.1 \sin(2\pi f_{in} t), f_{in} = 10 \text{ kHz}$ .
  - What is the voltage gain of the amplifier at  $f_{in} = 10 \text{ kHz}$ ?
  - Making use of "AC Simulation", plot the amplitude frequency response of the amplifier and determine the following parameters.
    - $A_0$  (dc voltage gain of the amplifier)
    - $A(f = 10 \text{ kHz})$  (voltage gain of the amplifier at  $f_{in} = 10 \text{ kHz}$ )
    - $f_{p1}$  (-3 dB cut-off frequency)
    - $f_T$  (unity gain frequency)
  - Is the following relation is correct?
- $$f_T = A_0 \times f_{p1}$$
- Conclude about the capabilities of "DC Simulation", "Transient Simulation", and "AC Simulation".