
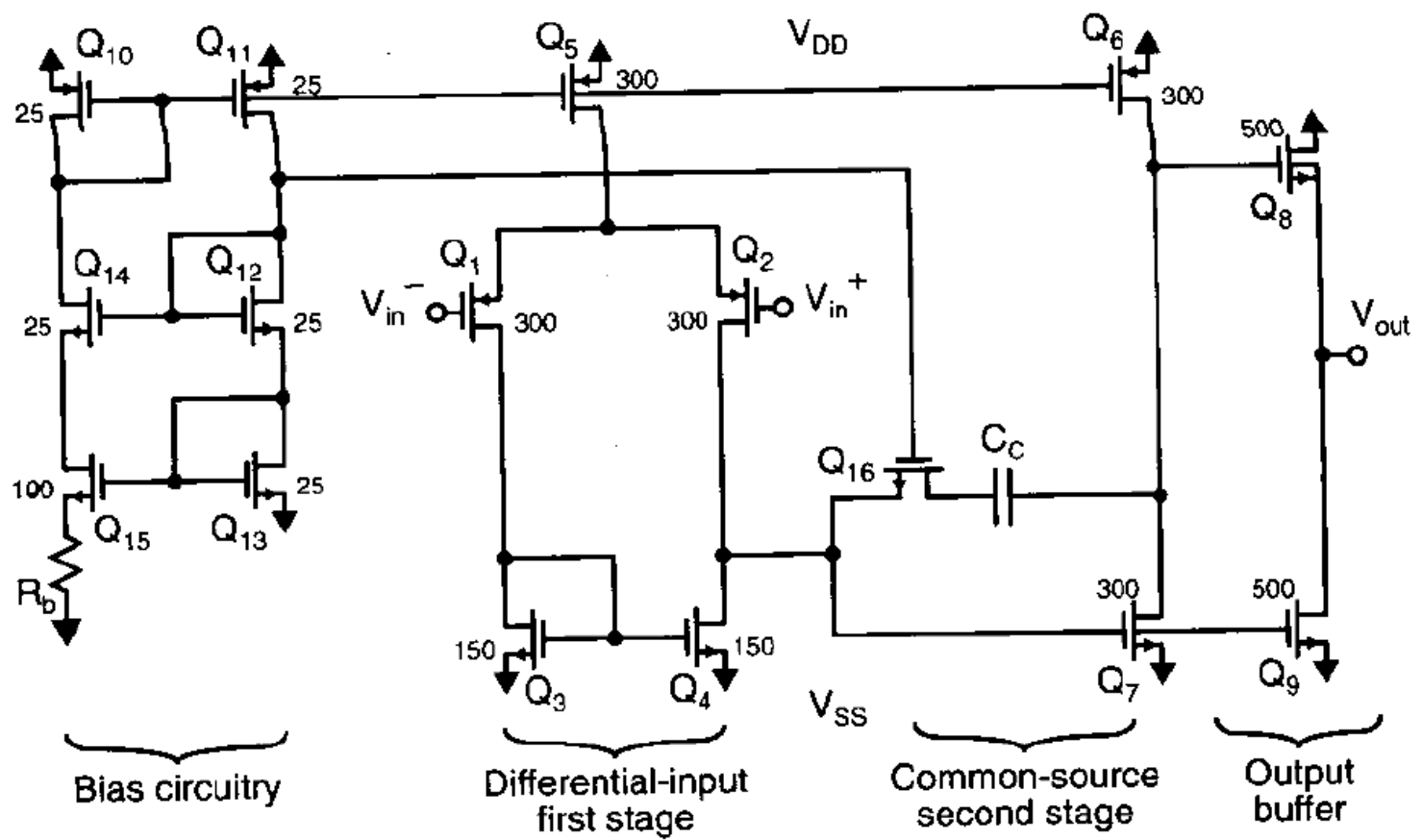


Basic Opamp Design and Compensation

Hossein Shamsi

Two-Stage opamp

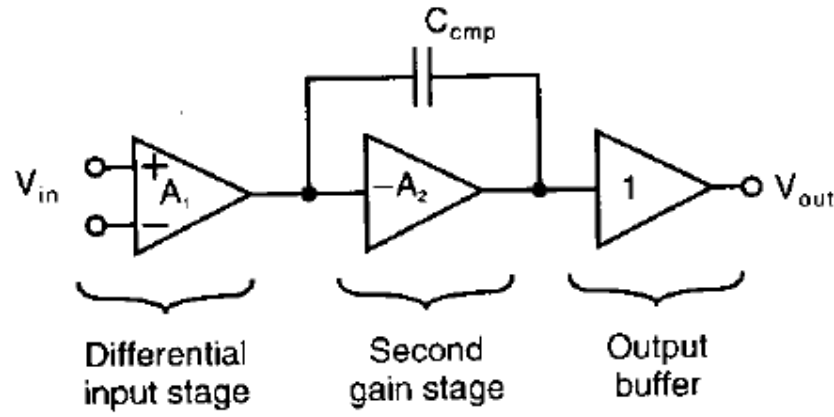

opamp Gain

$$A_{V1} = -g_{m1} (r_{ds2} \parallel r_{ds4})$$


$$A_{V2} = -g_{m7} (r_{ds6} \parallel r_{ds7})$$

$$A_{V3} \equiv \frac{g_{m8}}{G_L + g_{m8} + g_{ds8} + g_{ds9}}$$

$$A_0 = A_{V1} \times A_{V2} \times A_{V3}$$

Slew Rate

$$SR = \left| \frac{dV_o}{dt} \right|_{\max} = \frac{I_{D5}}{C_C}$$

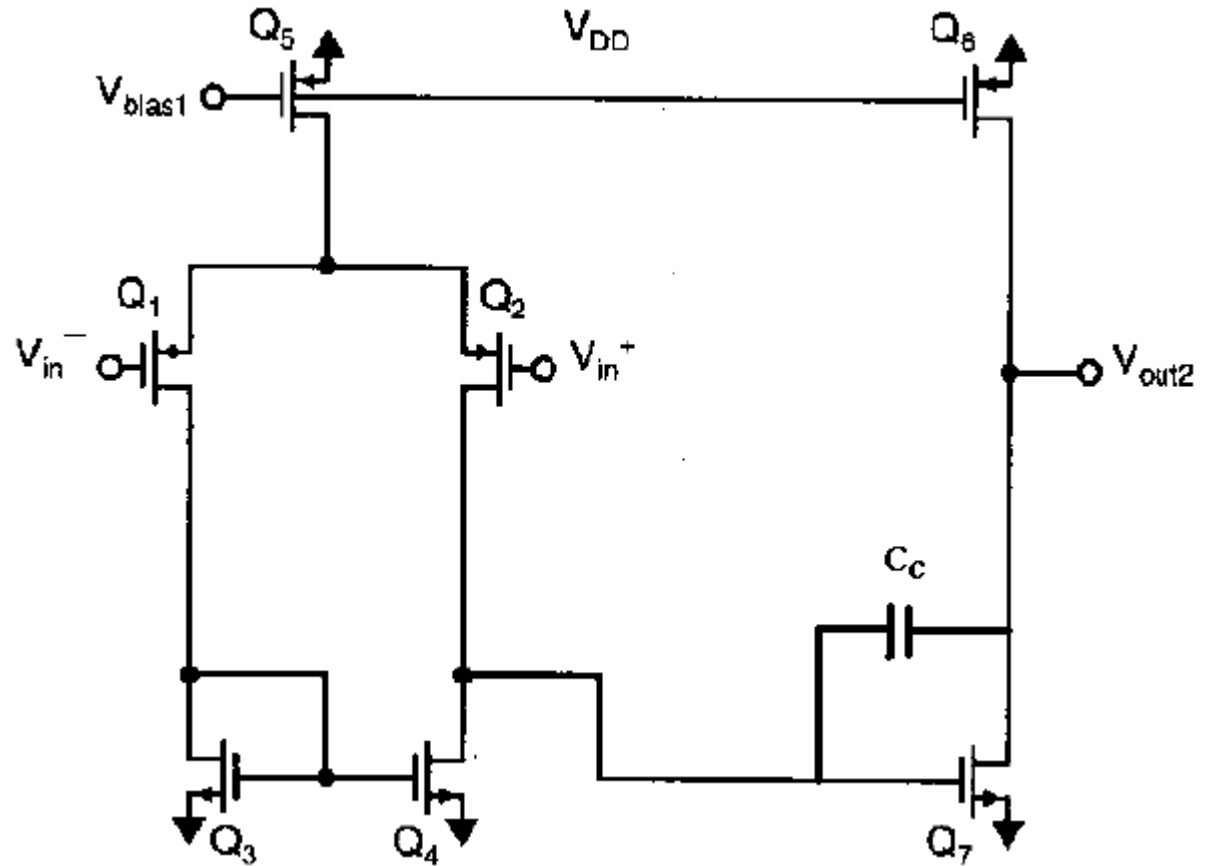


Guidelines for Biasing of the Two-Stage opamp

1. $100 \text{ mV} < V_{DS(SAT)} < 200 \text{ mV}$
2. $V_{DS} > 2V_{DS(SAT)}$
3. (both M_i and M_j are npmos or pmos)

$$\frac{I_{D_i}}{I_{D_j}} = \frac{\left(\frac{W}{L}\right)_i}{\left(\frac{W}{L}\right)_j}$$

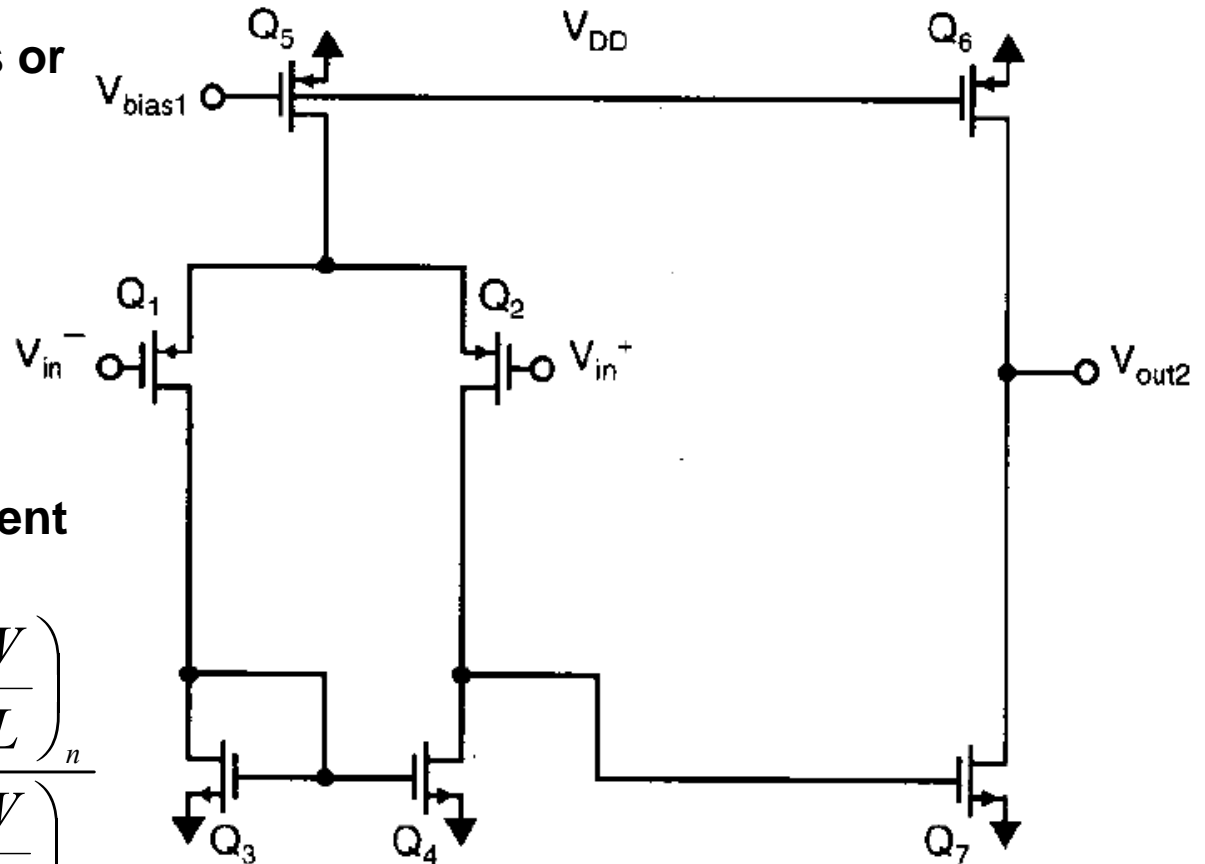4. (Transistors are from different types)

$$\frac{I_{D_n}}{I_{D_p}} = \frac{\mu_n}{\mu_p} \frac{\left(\frac{W}{L}\right)_n}{\left(\frac{W}{L}\right)_p} \cong 3 \frac{\left(\frac{W}{L}\right)_n}{\left(\frac{W}{L}\right)_p}$$



Frequency Response (first-order model)

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_{p1}}}$$

$$\omega_{p1} \cong \frac{1}{(r_{ds2} \parallel r_{ds4}) C_C (1 + A_2)}$$


$$\cong \frac{1}{(r_{ds2} \parallel r_{ds4}) C_C A_2}$$

$$A_0 = g_{m1} (r_{ds2} \parallel r_{ds4}) A_2$$


It is proven that:

$$UGBW = \omega_{ta} = A_0 \omega_{p1} = \frac{g_{m1}}{C_C}$$

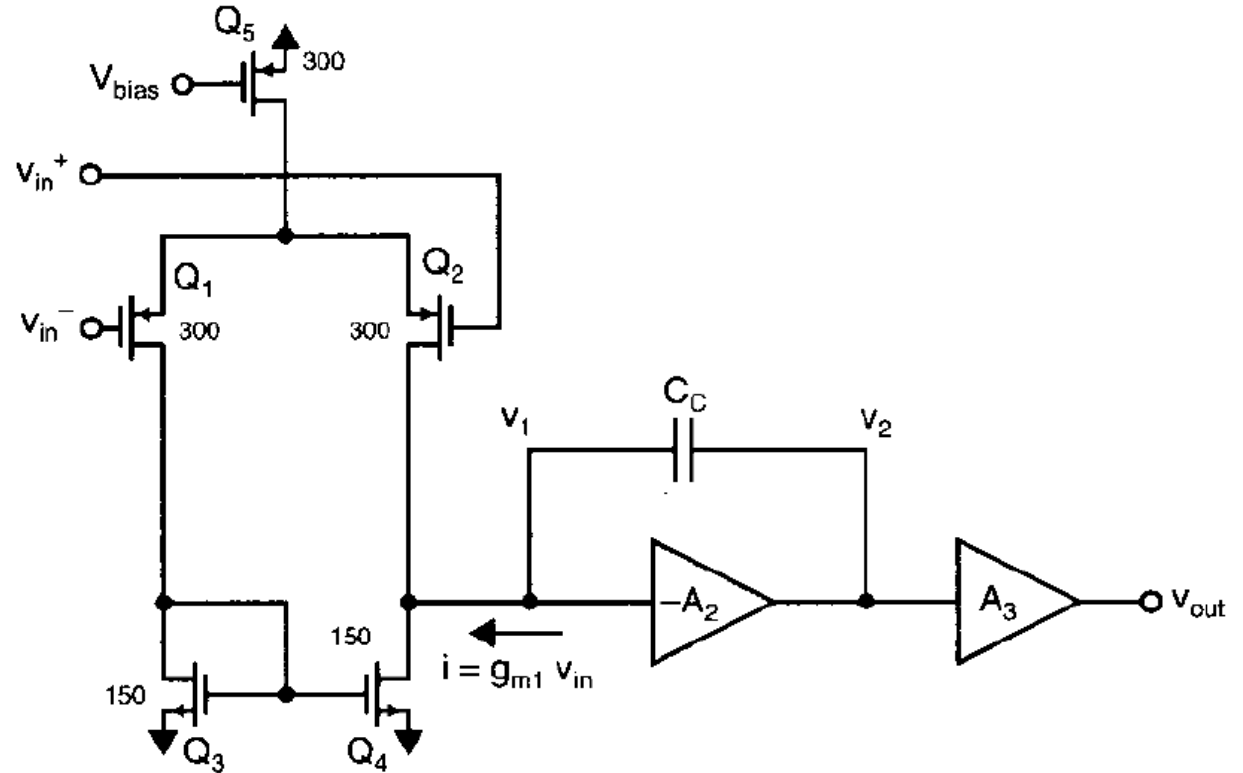Since a first order transfer function is assumed for the Opamp, therefore it does not have stability problem.




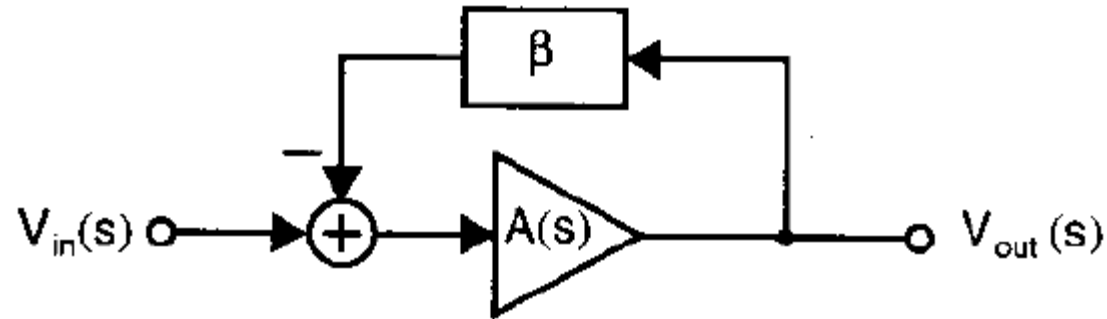Using opamp in closed-loop configurations



$$A(s) = \frac{A_0}{(1 + s/\omega_{p1})}$$
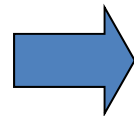
$$A_{CL}(s) = \frac{A(s)}{1 + \beta A(s)}$$




$$A_{CL}(s) \approx \frac{\omega_{ta}}{\beta\omega_{ta} + s} = \frac{1}{\beta} \frac{1}{(1 + s/\beta\omega_{ta})}$$

Hence for the closed-loop amplifier, we have:

$$A_{CL}(0) = \frac{1}{\beta}$$

$$\omega_{-3dB} = \beta\omega_{ta}$$

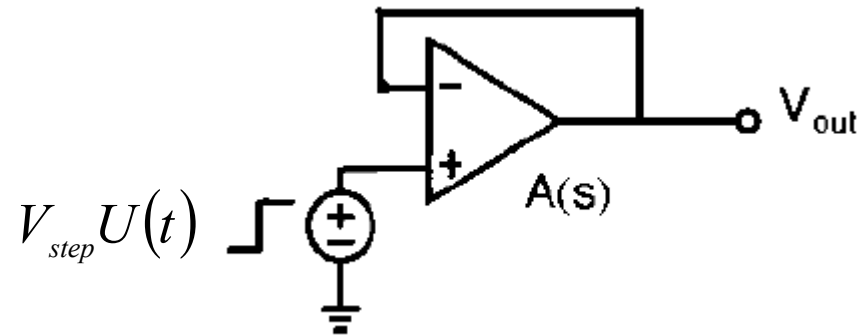Using opamp in closed-loop configurations (Example#1)




After performing an accurate analysis, we have:

$$V_o(s) = \frac{\frac{A_0}{1 + A_0}}{1 + \frac{s}{(1 + A_0)\omega_{p1}}} \times \frac{1}{s} \times V_{step} \cong \frac{1 - \frac{1}{A_0}}{1 + \frac{s}{\omega_{ta}}} \times \frac{1}{s} \times V_{step}$$

$$v_o(t) \cong \left(1 - \frac{1}{A_0}\right) V_{step} \left(1 - e^{-\frac{t}{\tau}}\right), \quad \tau = \frac{1}{\omega_{ta}}$$

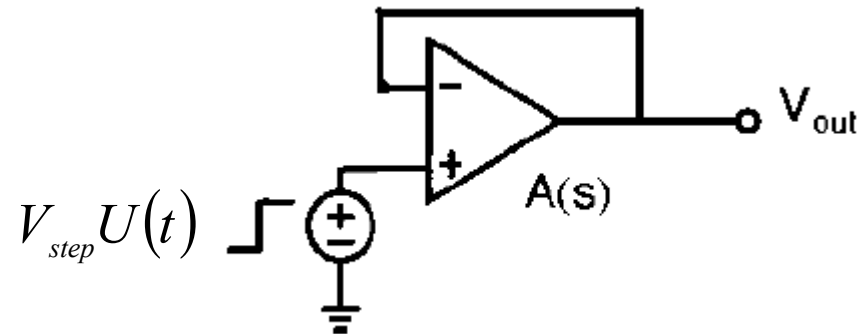Using opamp in closed-loop configurations (Example#1)



$$v_o(t) \cong \left(1 - \frac{1}{A_0}\right) V_{step} \left(1 - e^{-\frac{t}{\tau}}\right), \quad \tau = \frac{1}{\omega_{ta}}$$

$$\left(\frac{dv_o}{dt}\right)_{\max} = \left.\frac{dv_o}{dt}\right|_{t=0} = V_{step} \omega_{ta}$$


$$\text{if } V_{step} \omega_{ta} \leq SR \Rightarrow$$

The circuit has only the linear settling - time.




$$\text{if } V_{step} \omega_{ta} \geq SR \Rightarrow$$

The circuit has both the linear and non - linear settling - times.

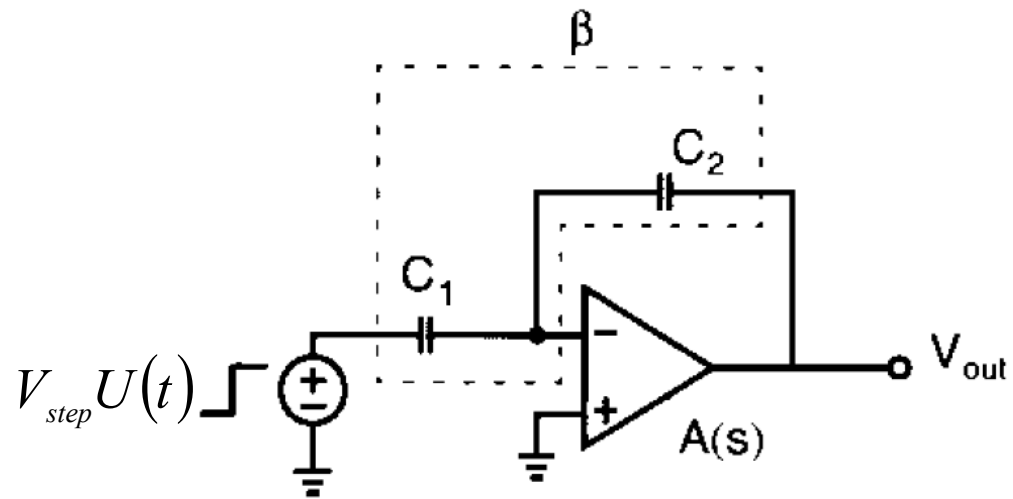Using opamp in closed-loop configurations (Example#2)



Frequency Response (second-order model)

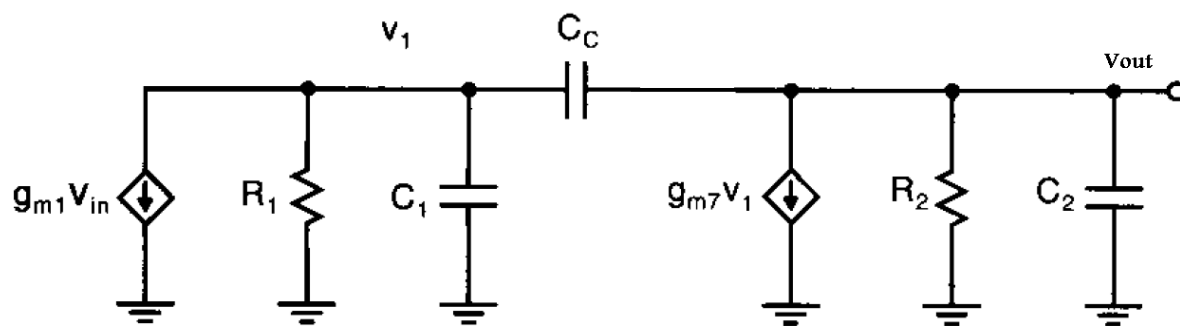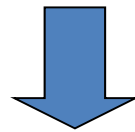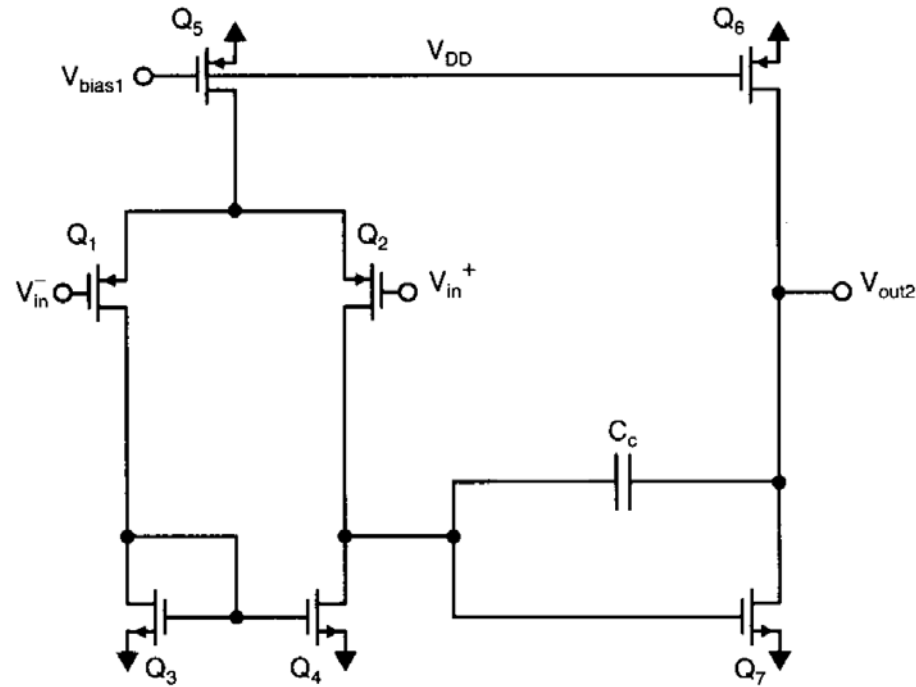


$$R_1 = r_{ds4} \parallel r_{ds2}$$

$$C_1 = C_{db2} + C_{db4} + C_{gs7}$$

$$R_2 = r_{ds6} \parallel r_{ds7}$$

$$C_2 = C_{db7} + C_{db6} + C_{L2}$$

Frequency Response (second-order model)

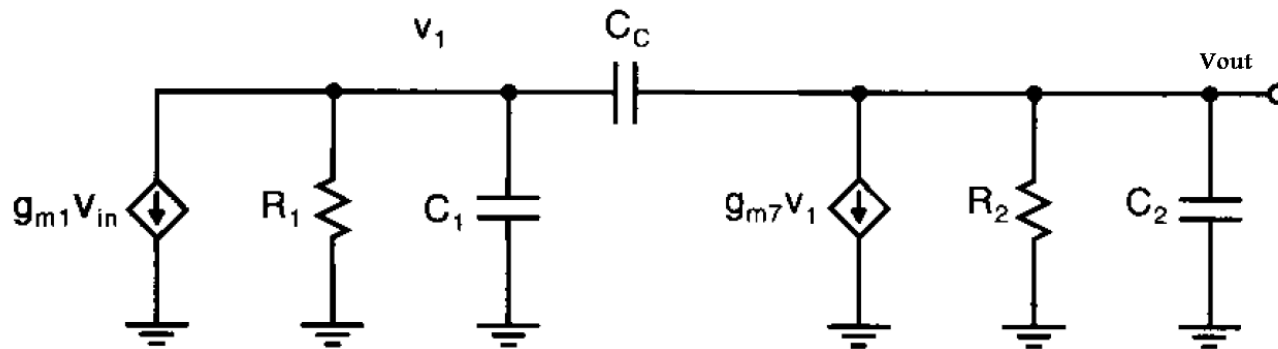

$$\frac{v_{out}}{v_{in}} = \frac{g_{m1} g_{m7} R_1 R_2 \left(1 - \frac{s C_C}{g_{m7}}\right)}{1 + s a + s^2 b}$$

$$a = (C_2 + C_C) R_2 + (C_1 + C_C) R_1 + g_{m7} R_1 R_2 C_C$$

$$b = R_1 R_2 (C_1 C_2 + C_1 C_C + C_2 C_C)$$

$$D(s) = \left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \cong 1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1} \omega_{p2}}$$

$$\omega_{p1} \cong \frac{1}{R_1 [C_1 + C_C (1 + g_{m7} R_2)] + R_2 (C_2 + C_C)}$$

$$\cong \frac{1}{R_1 C_C (1 + g_{m7} R_2)}$$


$$\cong \frac{1}{g_{m7} R_1 R_2 C_C}$$

$$\omega_{p2} \cong \frac{g_{m7} C_C}{C_1 C_2 + C_2 C_C + C_1 C_C}$$

$$\cong \frac{g_{m7}}{C_1 + C_2}$$

$$\omega_z = \frac{-g_{m7}}{C_C}$$

Frequency Response (second-order model)

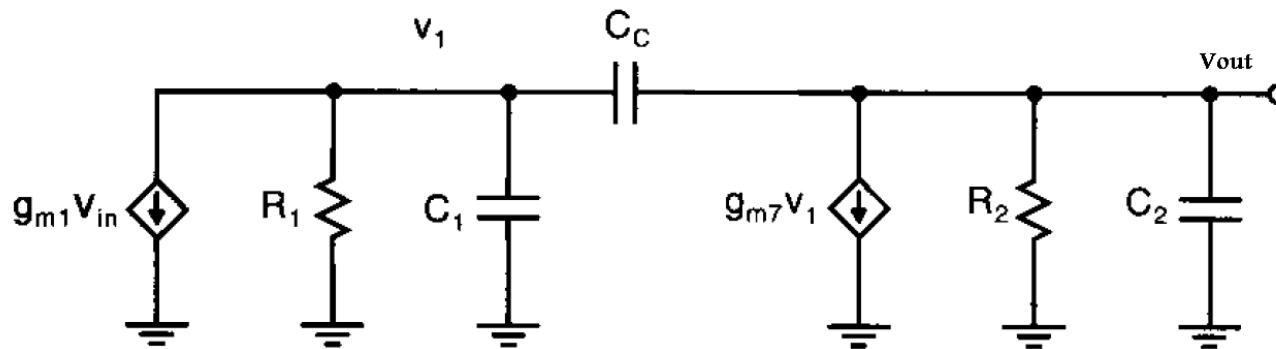

$$\omega_{p1} = \frac{1}{g_{m7} R_1 R_2 C_C}, \quad \omega_{p2} = \frac{g_{m7}}{C_1 + C_2}, \quad \omega_z = \frac{-g_{m7}}{C_C}$$

- As g_{m7} increases, the separation between the first and second poles increase.
- Increasing C_C moves the dominant pole to a lower frequency without affecting the second pole.
- Hence, the use of a Miller capacitance for compensation is often called “pole-splitting compensation”.
- The pole-splitting makes the opamp more stable.

Example1

Consider a two-stage opamp with the following characteristics:

$$g_{m1} = 1 \frac{\text{mA}}{\text{V}}, g_{m7} = 3 \frac{\text{mA}}{\text{V}}$$

$$R_1 = 10 \text{ k}, R_2 = 15 \text{ k}$$

$$C_1 = 0.1 \text{ pF}, C_2 = 0.3 \text{ pF}, C_c = 2 \text{ pF}$$

a) Calculate A_0 , ω_{p1} , ω_{p2} , ω_z , and $A(s)$.

$$A_0 = g_{m1} g_{m7} R_1 R_2 = 450 \rightarrow A_0 \Big|_{\text{dB}} = 53 \text{ dB}$$

$$\omega_{\text{ta}} = \frac{g_{m1}}{C_c} = \frac{1 \text{ m}}{2 \text{ p}} = 0.5 \text{ G} \frac{\text{Rad}}{\text{s}} = 2\pi \times 80 \text{ MHz}$$

$$\omega_{\text{ta}} = A_0 \times \omega_{p1} \rightarrow \omega_{p1} = 2\pi \times 177 \text{ kHz}$$


$$\omega_{p2} = \frac{g_{m7}}{C_1 + C_2} = 2\pi \times 1.19 \text{ GHz}$$

$$14 \quad \omega_z = -\frac{g_{m7}}{C_c} = -2\pi \times 239 \text{ MHz}$$


$$A(s) = 450 \frac{\left(1 - \frac{s}{1.5 \times 10^9}\right)}{\left(1 + \frac{s}{1.1 \times 10^6}\right) \left(1 + \frac{s}{7.5 \times 10^9}\right)}$$

b) Plot the Bode diagram of $A(s)$.

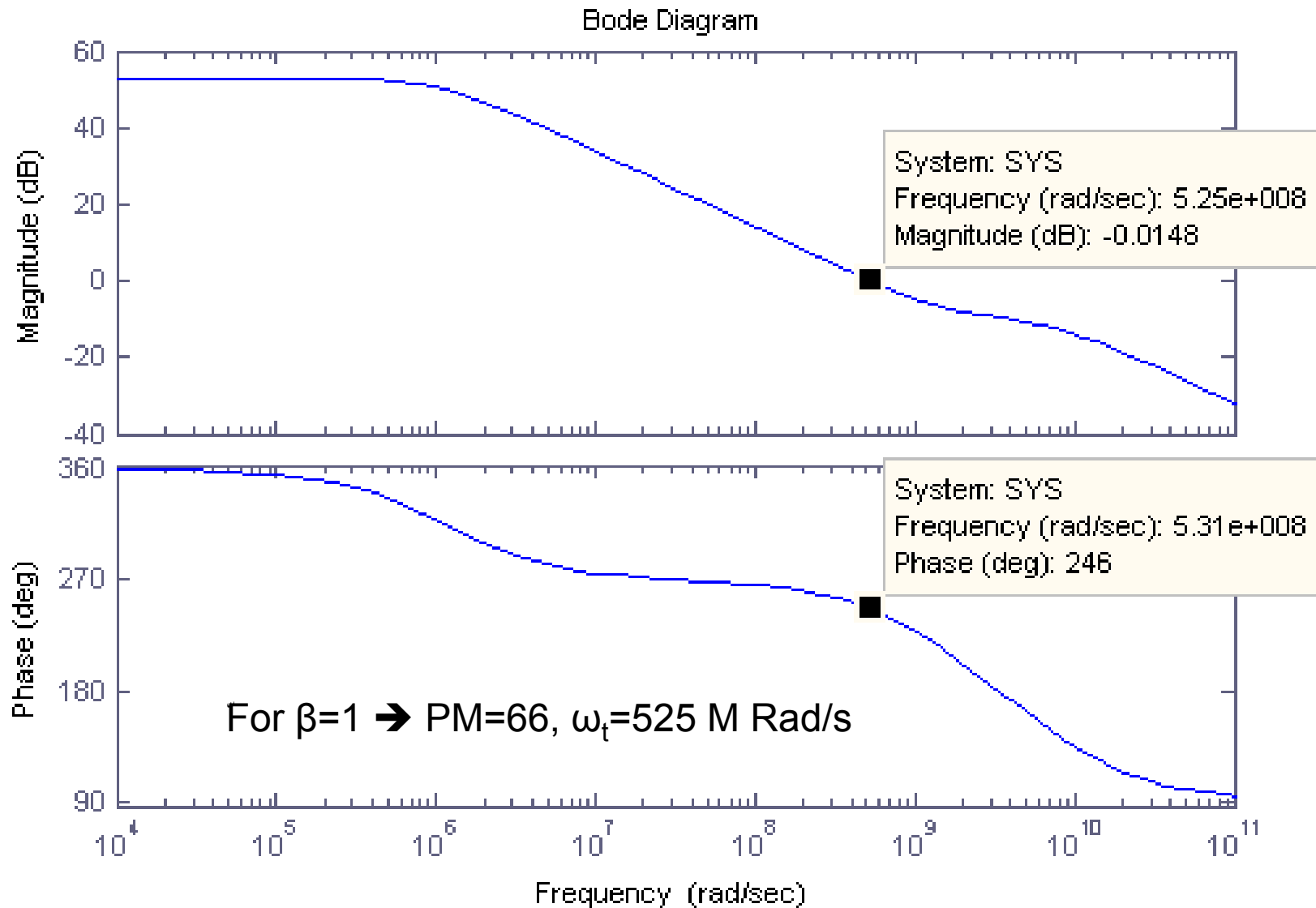c) What is the phase margin if we use the opamp in a closed-loop configuration with feedback coefficient of $\beta=1$?



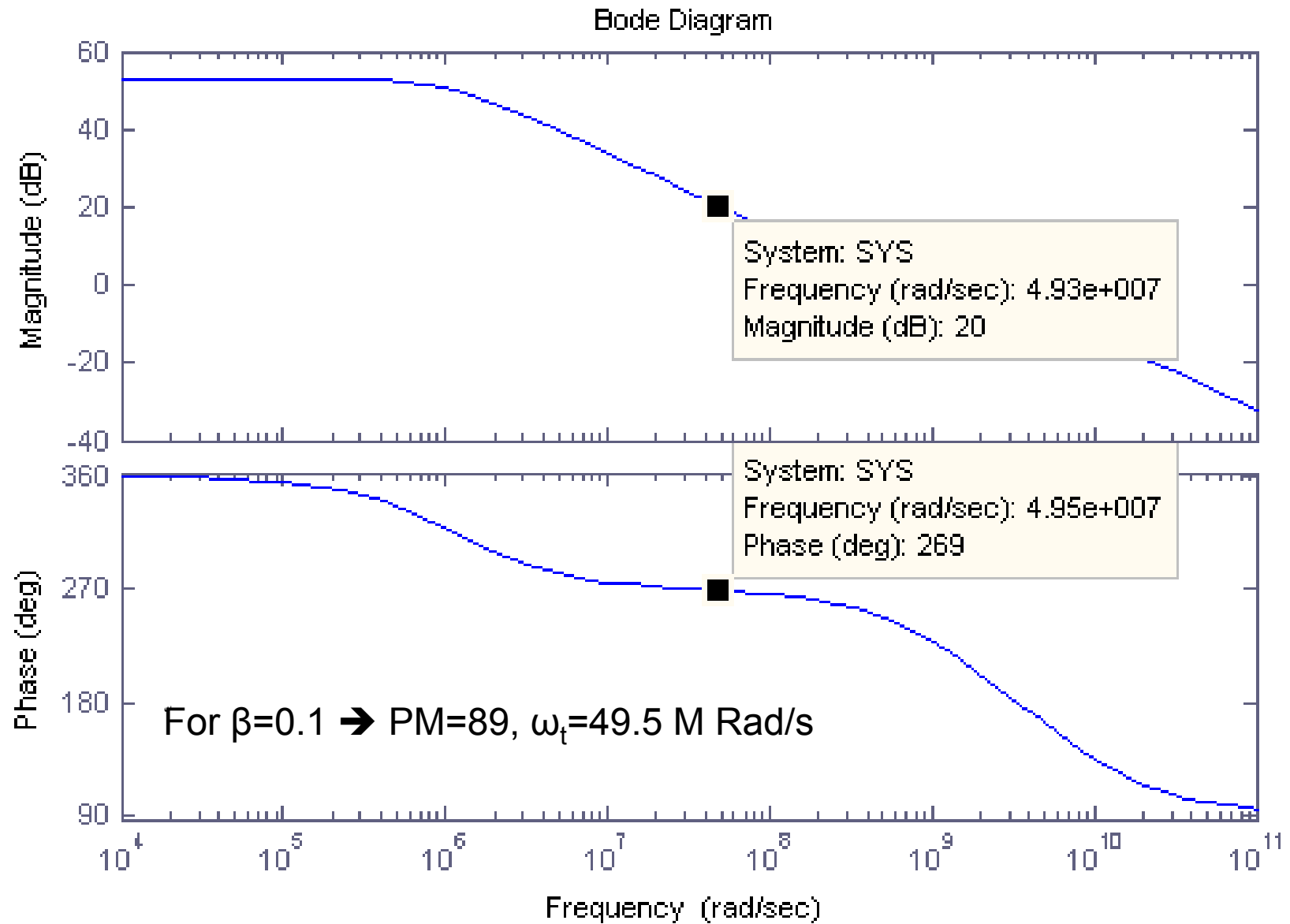d) What is the phase margin for $\beta=0.1$?



For $\beta=1 \rightarrow PM=66, \omega_t=525 \text{ M Rad/s}$

For $\beta=0.1 \rightarrow PM=89, \omega_t=49.5 \text{ M Rad/s}$

It is considered that for greater values of β , the stability of the closed-loop system decreases.

It is considered that for greater values of β , the bandwidth of the closed-loop system increases.

Example2

Consider a two-stage opamp with the following characteristics:

$$g_{m1} = 1 \frac{\text{mA}}{\text{V}}, g_{m7} = 3 \frac{\text{mA}}{\text{V}}$$

$$R_1 = 10 \text{ k}, R_2 = 15 \text{ k}$$

$$C_1 = 0.1 \text{ pF}, C_2 = 0.3 \text{ pF}, C_C = 1 \text{ pF}$$

a) Calculate A_0 , ω_{p1} , ω_{p2} , ω_z , and $A(s)$.

$$A_0 = g_{m1} g_{m7} R_1 R_2 = 450 \rightarrow A_0 \Big|_{\text{dB}} = 53 \text{ dB}$$

$$\omega_{\text{ta}} = \frac{g_{m1}}{C_C} = \frac{1 \text{ m}}{1 \text{ p}} = 1 \text{ G} \frac{\text{Rad}}{\text{s}} = 2\pi \times 160 \text{ MHz}$$

$$\omega_{\text{ta}} = A_0 \times \omega_{p1} \rightarrow \omega_{p1} = 2\pi \times 354 \text{ kHz}$$

$$\omega_{p2} = \frac{g_{m7}}{C_1 + C_2} = 2\pi \times 1.19 \text{ GHz}$$

$$\omega_z = -\frac{g_{m7}}{C_C} = -2\pi \times 478 \text{ MHz}$$

$$A(s) = 450 \frac{\left(1 - \frac{s}{3 \times 10^9}\right)}{\left(1 + \frac{s}{2.2 \times 10^6}\right) \left(1 + \frac{s}{7.5 \times 10^9}\right)}$$

- b) What is the phase margin for feedback coefficient of $\beta=1$?
c) What is the phase margin for feedback coefficient of $\beta=0.1$?

For $\beta=1 \rightarrow PM=63, \omega_t=1.04 \text{ G Rad/s}$

For $\beta=0.1 \rightarrow PM=89, \omega_t=99 \text{ M Rad/s}$

It is considered that if C_C is decreased, the bandwidth of the system is increased while the stability problem is worsened.

Comparison between the Example1 and Example2

Example1: ($C_C=2$ pF)

For $\beta=1 \rightarrow PM=66, \omega_t=525$ M Rad/s

For $\beta=0.1 \rightarrow PM=89, \omega_t=49.5$ M Rad/s


Example2: ($C_C=1$ pF)

For $\beta=1 \rightarrow PM=63, \omega_t=1.04$ G Rad/s

For $\beta=0.1 \rightarrow PM=89, \omega_t=99$ M Rad/s

The compensation of the opamp of Example2 is performed better than that of the Example1 because it leads to a higher bandwidth and enough phase margin.


Frequency Response (second-order model)

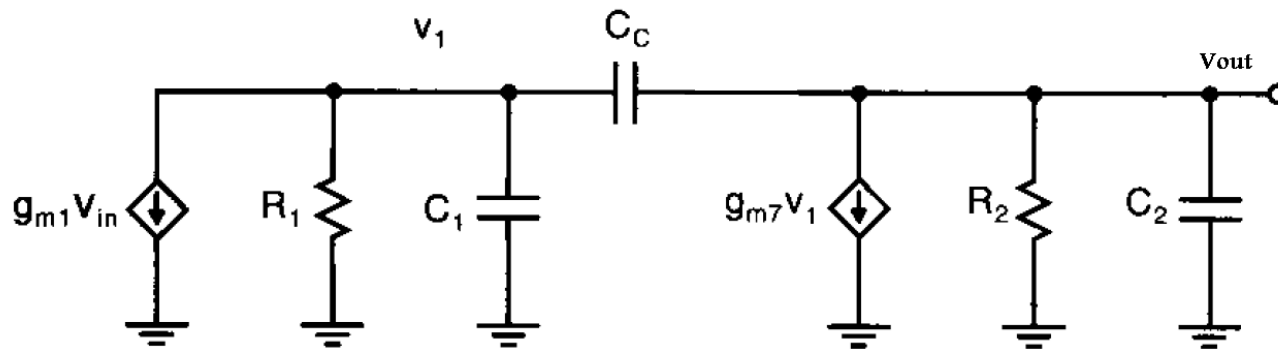

$$\omega_{p1} = \frac{1}{g_{m7} R_1 R_2 C_C}, \quad \omega_{p2} = \frac{g_{m7}}{C_1 + C_2}, \quad \omega_z = \frac{-g_{m7}}{C_C}$$

- A problem arises due to the right-half-plane zero, ω_z . It introduces negative phase shift (phase lag).
- The right-half-plane zero makes the stability more difficult.
- Fortunately by using the resistor, R_C , in series with C_C , this problem is mitigated.


Right-Half-Plane Zero Problem

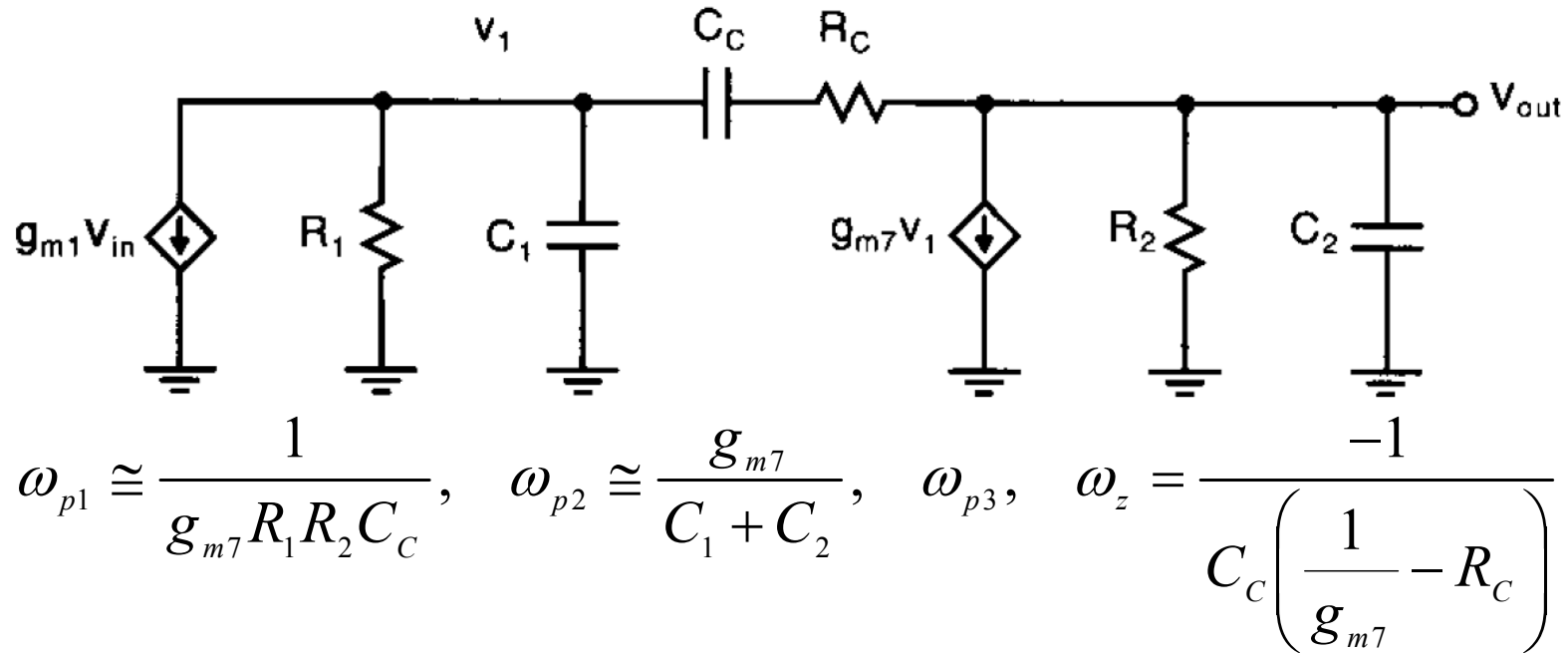

There are three approaches to solve the right-half-plane zero problem as follows:

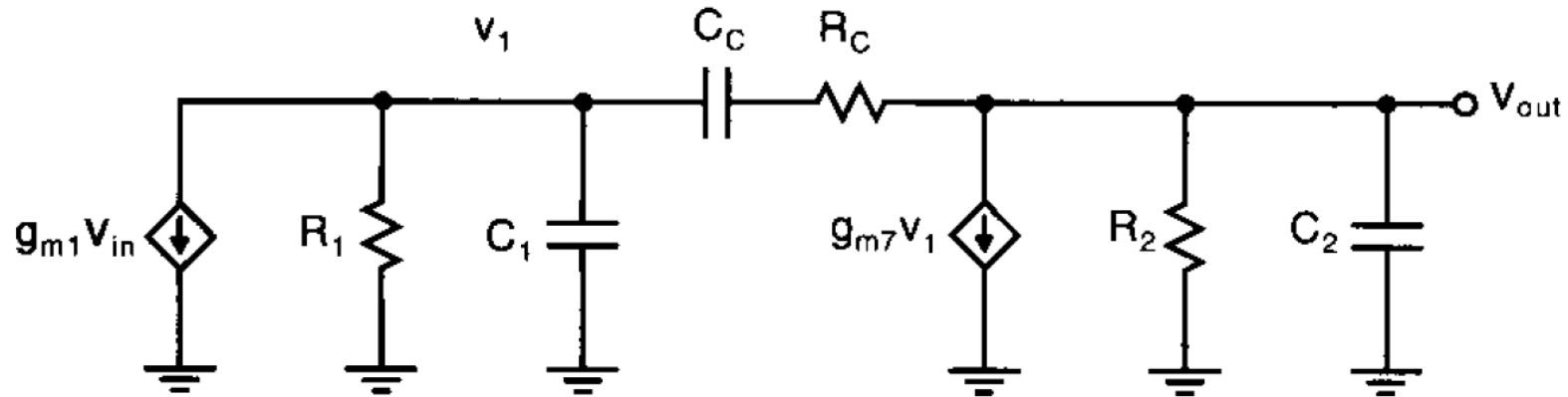1. zero cancellation
2. pole-zero cancellation
3. lead compensation

Zero cancellation, Pole-zero cancellation



$$\omega_{p1} \cong \frac{1}{g_{m7} R_1 R_2 C_C}, \quad \omega_{p2} \cong \frac{g_{m7}}{C_1 + C_2}, \quad \omega_{p3}, \quad \omega_z = \frac{-1}{C_C \left(\frac{1}{g_{m7}} - R_C \right)}$$

In order to eliminate the right-half plane zero, we should choose the value of R_C as follows:

$$R_C = 1/g_{m7}$$

Pole-zero cancellation is performed if $\omega_{p2} = \omega_z$. After a few manipulation, the condition for pole-zero cancellation is obtained as follows:

$$R_C = \frac{1}{g_{m7}} \left(1 + \frac{C_1 + C_2}{C_C} \right)$$

Lead compensation

$$\omega_{p1} \cong \frac{1}{g_{m7} R_1 R_2 C_C}, \quad \omega_{p2} \cong \frac{g_{m7}}{C_1 + C_2}, \quad \omega_{p3}, \quad \omega_z = \frac{-1}{C_C \left(\frac{1}{g_{m7}} - R_C \right)}$$

The pole-zero cancellation method is not reliable because C_2 is often not known a priori. David Johns recommends the lead compensation method as follows:

$$\omega_z = 1.7\omega_t$$

By using $\omega_t \cong \omega_{ta} = \frac{g_{m1}}{C_C}$ and $\omega_z = 1.7\omega_t$, the value of R_C is given as follows:

$$R_C = \frac{1}{1.7g_{m1}} + \frac{1}{g_{m7}} \cong \frac{1}{1.7g_{m1}}$$