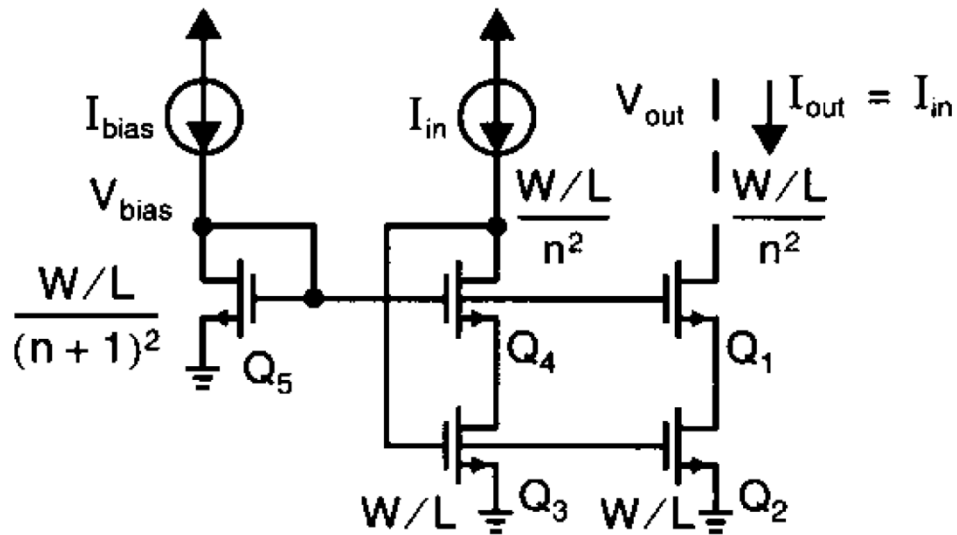


Advanced Current Mirrors and Opamps

Hossein Shamsi

Wide-Swing Current Mirrors




It is proven that if both of the following conditions are satisfied, then all transistors will be biased in the saturation region.

$$\begin{cases} V_{out} \geq (n+1)V_{eff} \\ V_{in} \geq nV_{eff} \end{cases}$$

Typically n is chosen identical to 1. So the output swing will be:

$$V_{out} \geq 2V_{eff}$$

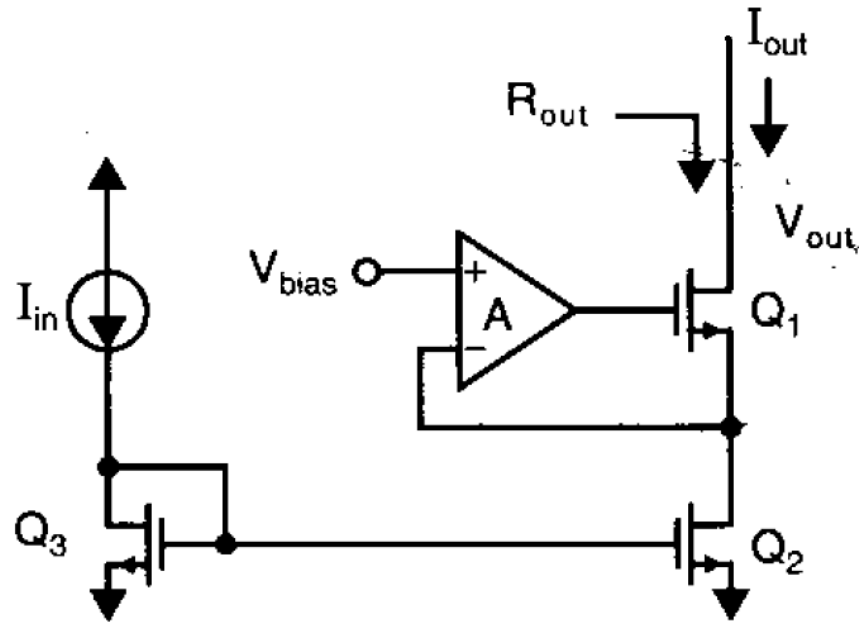Enhanced Output-Impedance Current Mirrors



$$R_{out} \cong g_{m1} r_{ds1} r_{ds2} (1 + A)$$

Implementation of Enhanced Output-Impedance Current Mirror

$$R_{out} \cong g_{m1} r_{ds1} r_{ds2} g_{m3} \frac{r_{ds3}}{2}$$

$$V_{out} \geq V_{tn} + V_{eff3} + V_{eff1}$$


Advantage:

- High Output-Impedance

Disadvantages:

- Low Output-Swing

- Imprecise Current Mirror

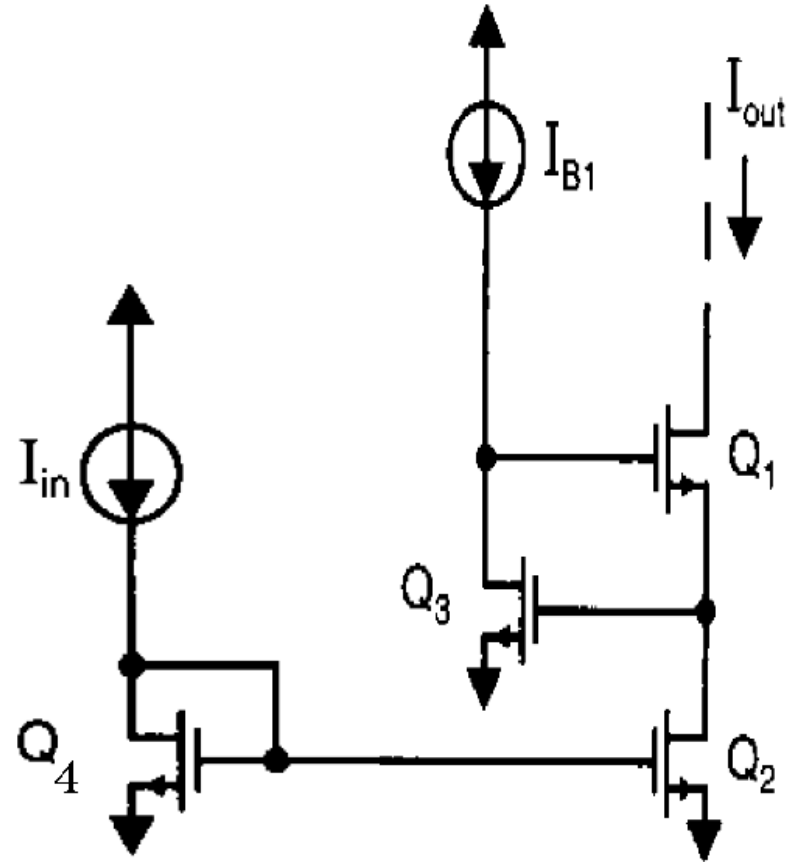

Implementation of Enhanced Output-Impedance Current Mirror

$$R_{out} \cong g_{m1} r_{ds1} r_{ds2} g_{m3} \frac{r_{ds3}}{2}$$


$$V_{out} \geq V_{tn} + V_{eff3} + V_{eff1}$$

Advantages:


- High Output-Impedance
- Precise Current Mirror

Disadvantage:

- Low Output-Swing

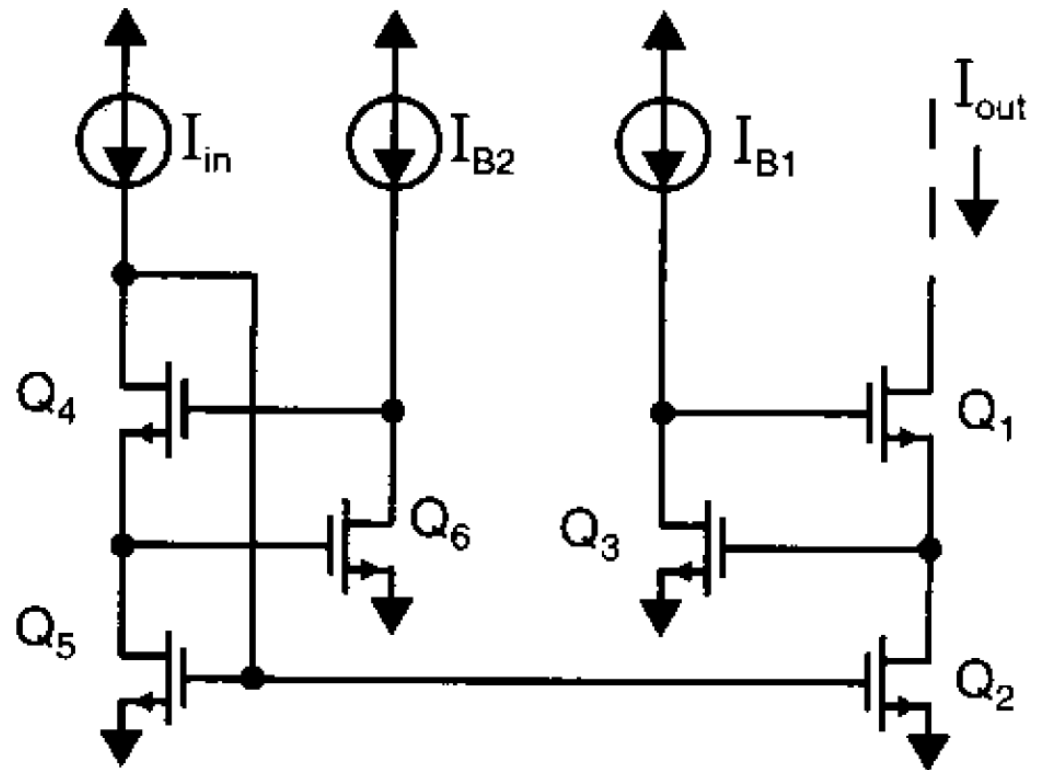

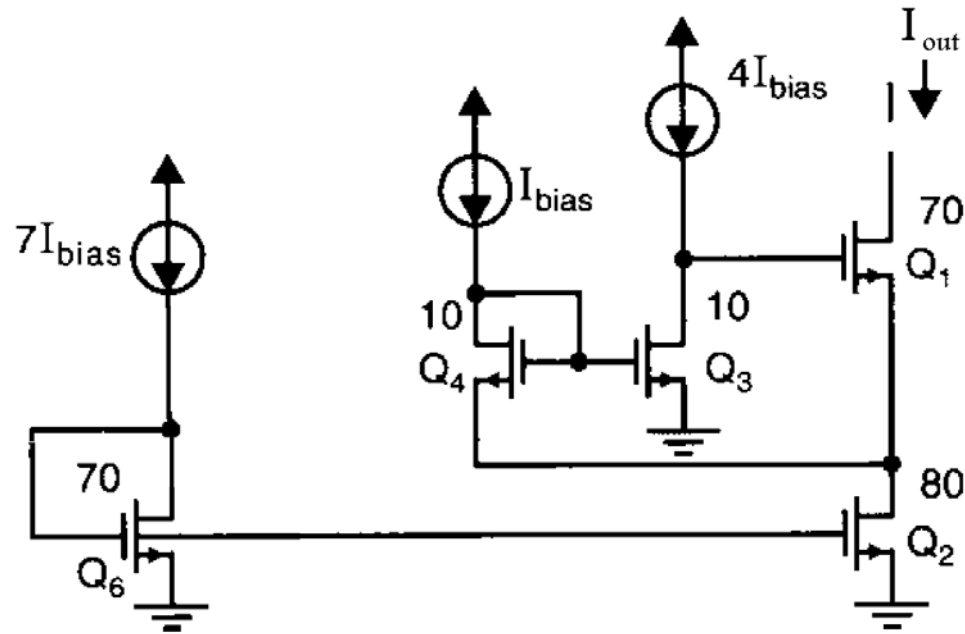Implementation of Enhanced Output-Impedance Current Mirror



$$R_{out} \cong g_{m1} r_{ds1} r_{ds2} g_{m3} \frac{r_{ds3}}{2}$$

$$V_{out} \geq 2V_{eff1}$$


Advantages:

- High Output-Impedance
- High Output-Swing

Disadvantage:

- Imprecise Current Mirror

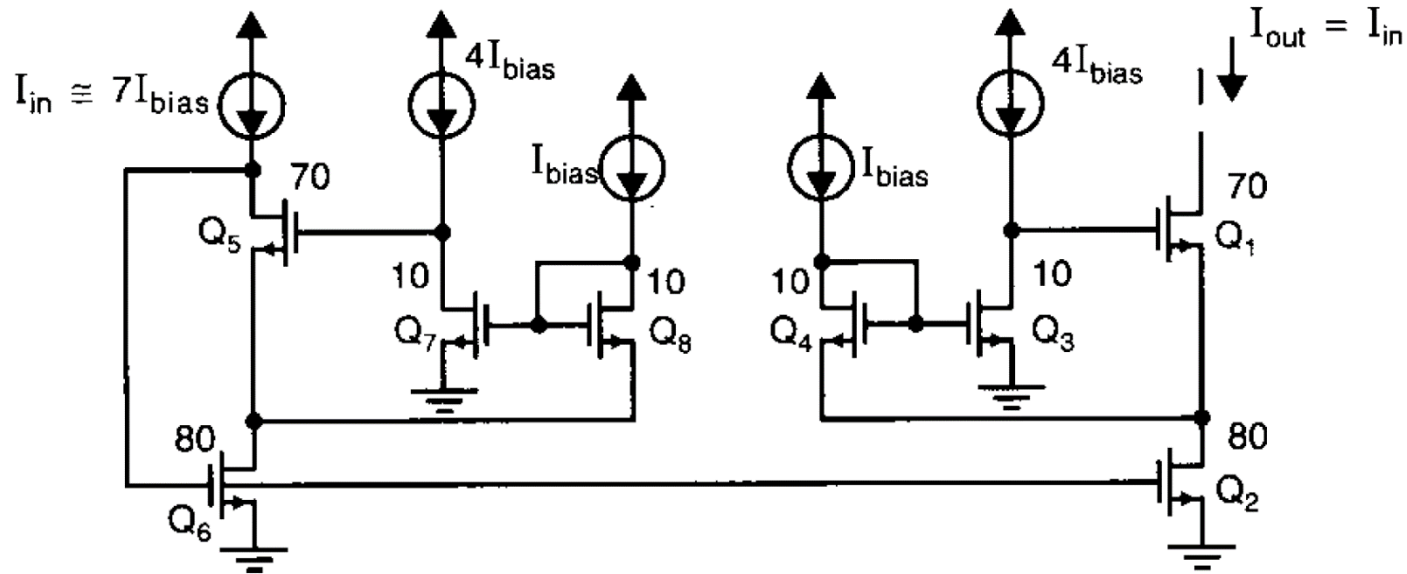Wide-Swing Current Mirror with Enhanced Output-Impedance



$$R_{out} \cong g_{m1} r_{ds1} r_{ds2} g_{m3} \frac{r_{ds3}}{2}$$

$$V_{out} \geq 2V_{eff1}$$







Advantages:

- High Output-Impedance
- Precise Current Mirror
- High Output-Swing


Disadvantage:

- High Power Consumption

Current Mirror Symbol

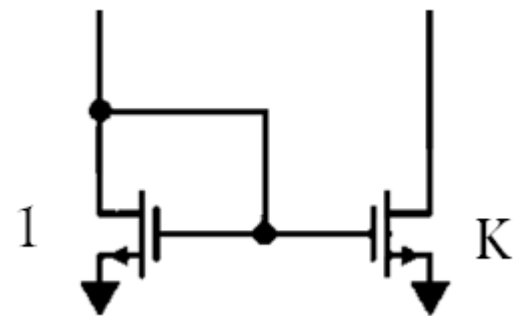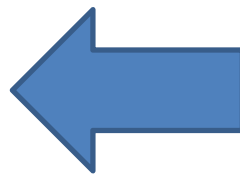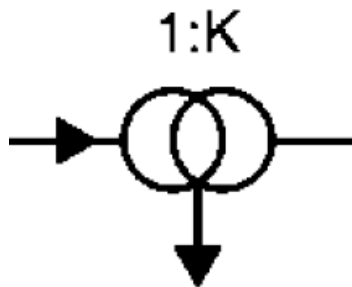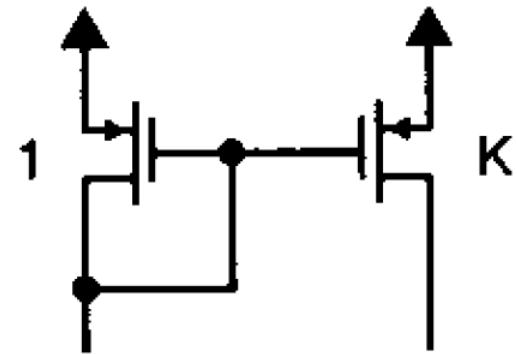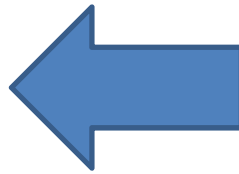
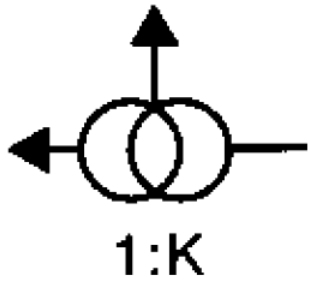


Folded-Cascode Opamp

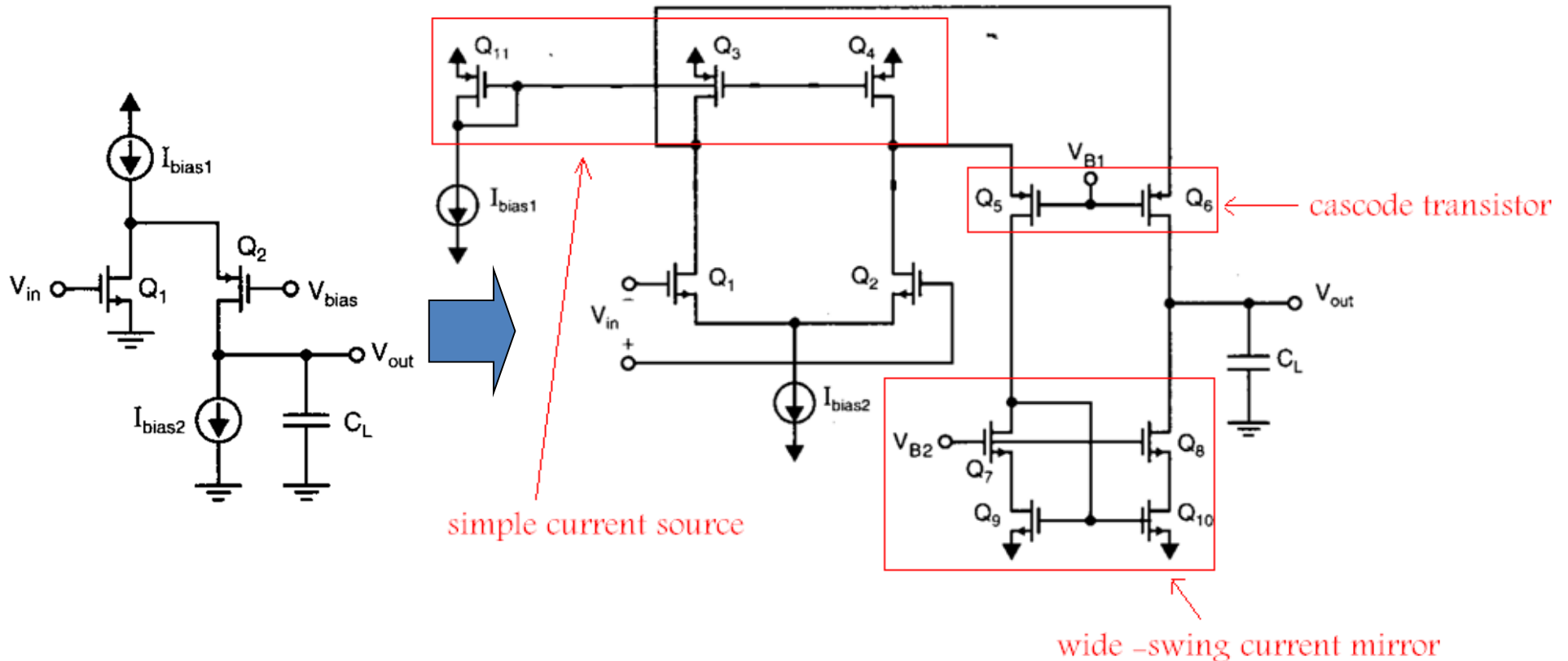


- This opamp is useful when we want to drive capacitive loads.
- One of the most important parameters of this modern opamp is its transconductance value.
- Therefore, some designers refer to this modern opamp as Operational Transconductance Amplifier (OTA).

Remember the wide-swing current mirror

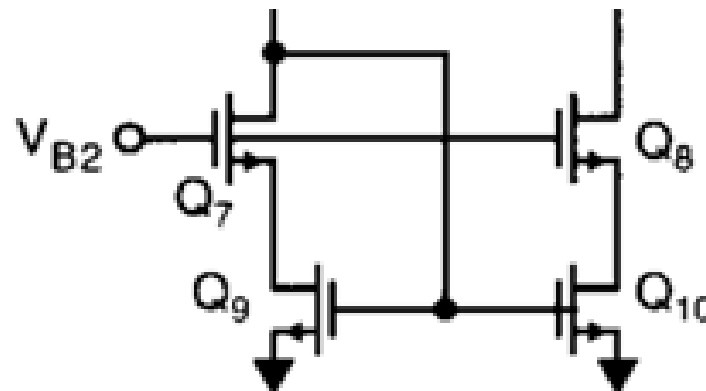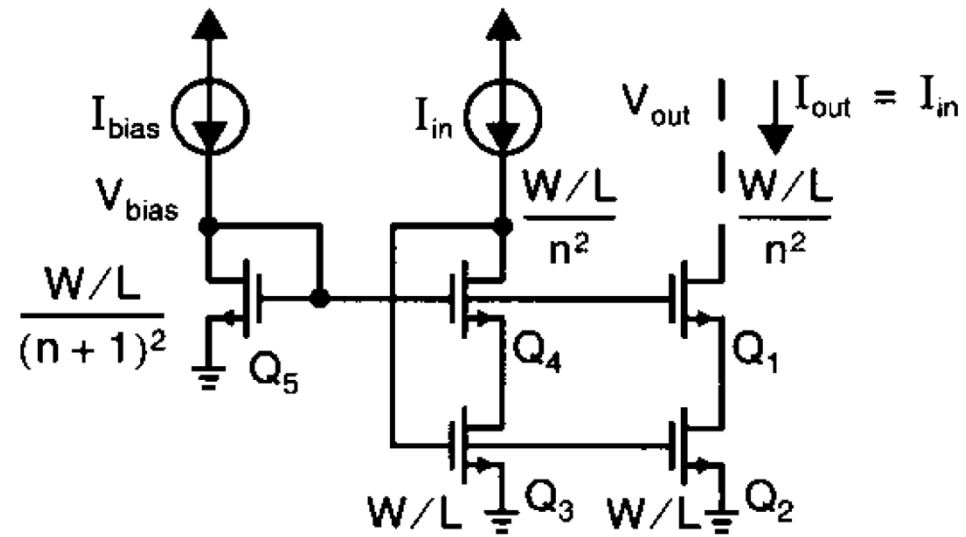

Opamp Gain

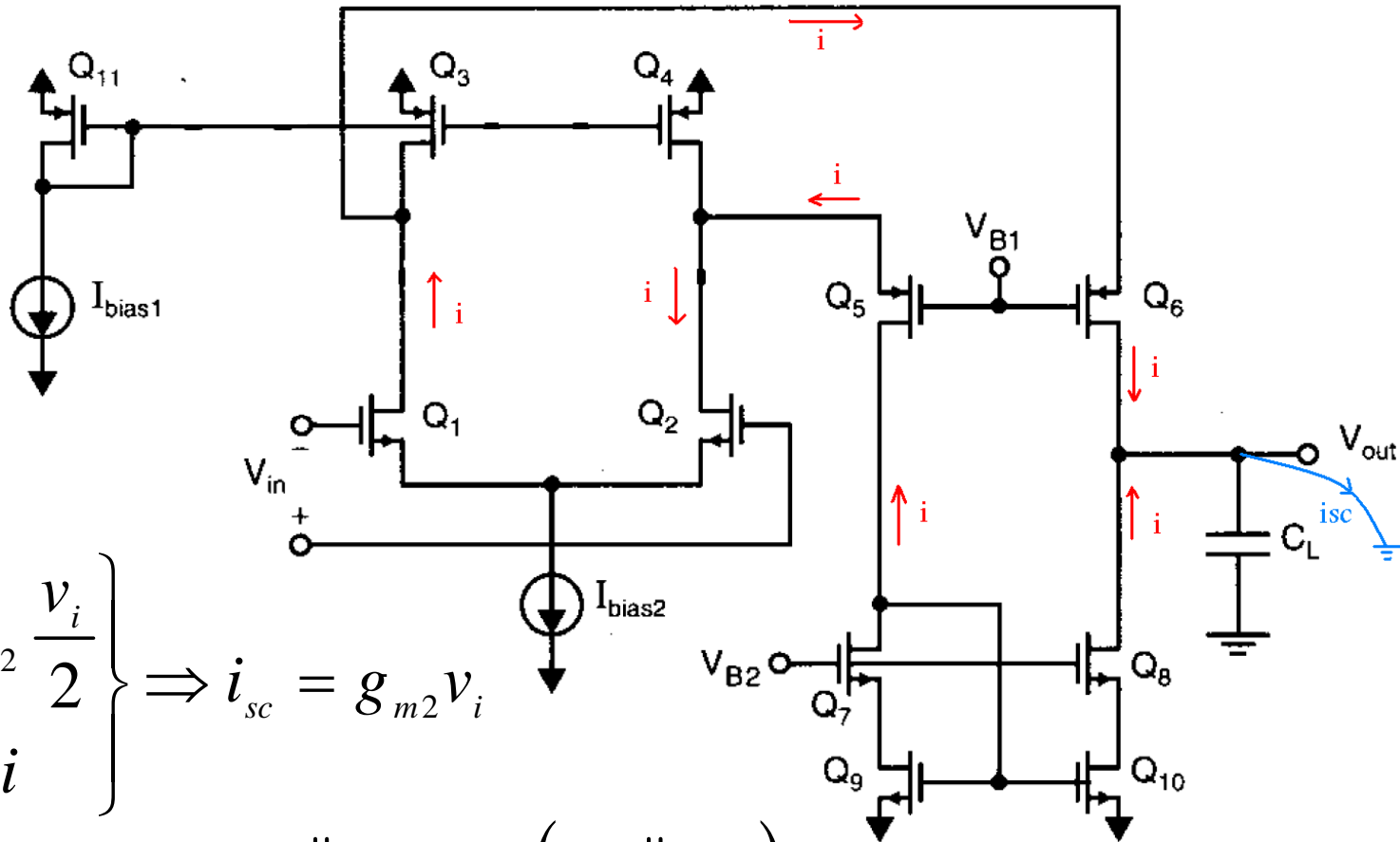

$$\left. \begin{aligned} i &= g_{m2} \frac{v_i}{2} \\ i_{sc} &= 2i \end{aligned} \right\} \Rightarrow i_{sc} = g_{m2} v_i$$

$$r_{out} \cong g_{m8} r_{ds8} r_{ds10} \parallel g_{m6} r_{ds6} (r_{ds3} \parallel r_{ds1})$$

$$v_o = r_{out} i_{sc} \Rightarrow A_V = g_{m1} r_{out}$$

Competition between Two Current Sources


Assume that:

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2$$


$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4$$

If $I_{bias1} > I_{bias2} \rightarrow$ Q1:Triode Q3:Active $I = I_{bias2}$

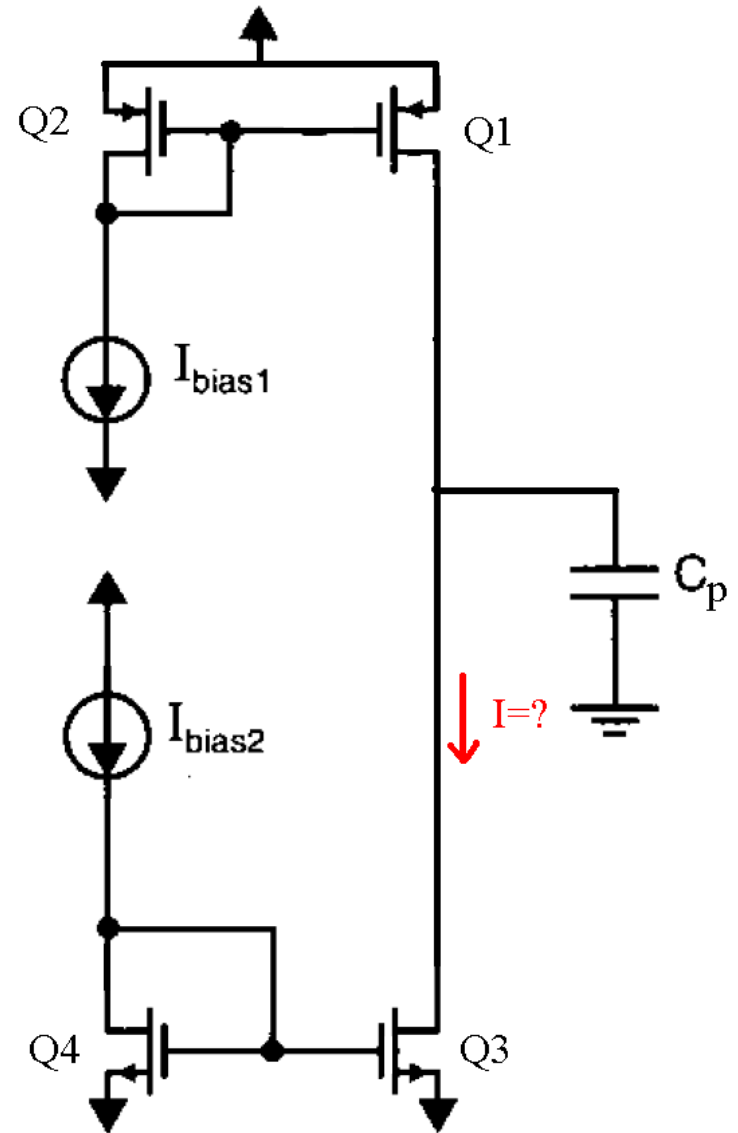If $I_{bias2} > I_{bias1} \rightarrow$ Q1:Active Q3:Triode $I = I_{bias1}$




Slew Rate

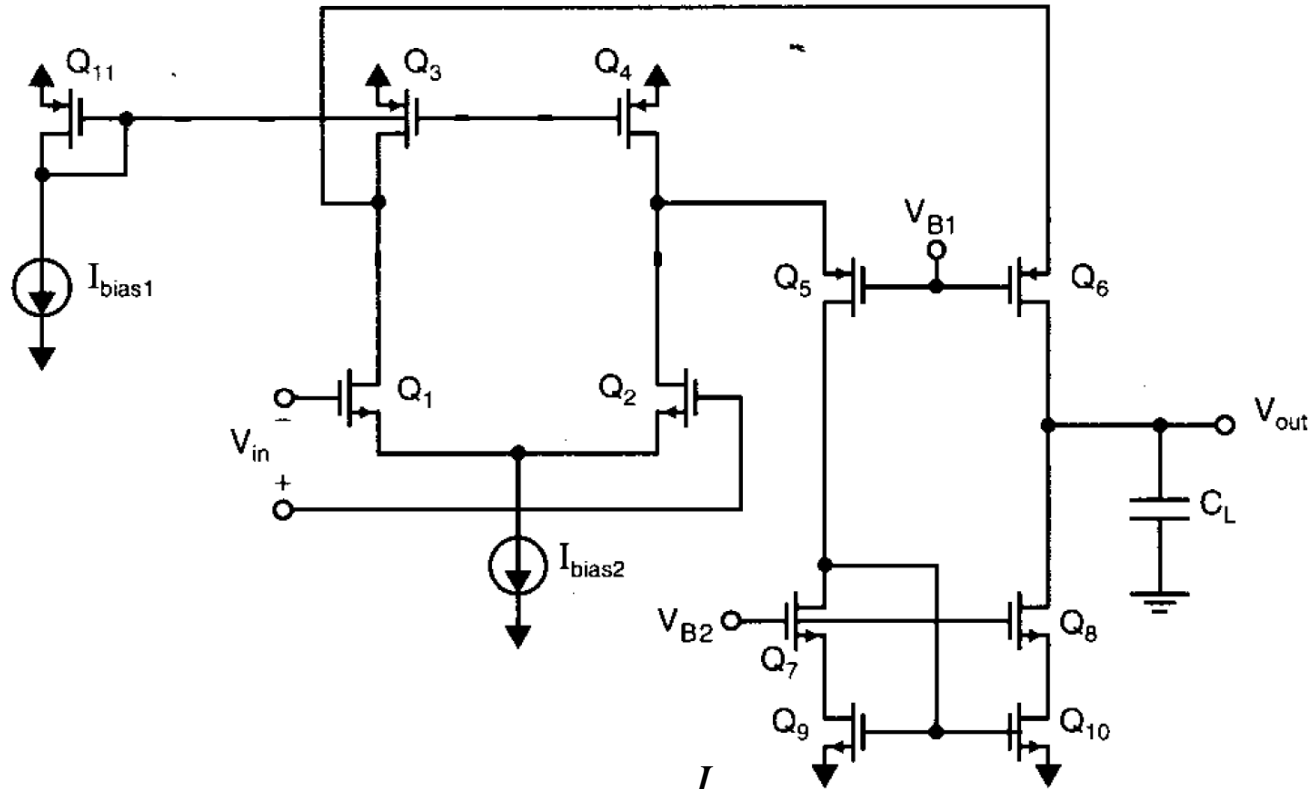

Assuming $I_{bias2} > I_{D4}$ and $V_{in+} \gg V_{in-} \rightarrow SR^+ = \frac{I_{D4}}{C_L}$


Assuming $I_{bias2} > I_{D4}$ and $V_{in-} \gg V_{in+} \rightarrow SR^- = \frac{I_{D4}}{C_L}$

Lemma

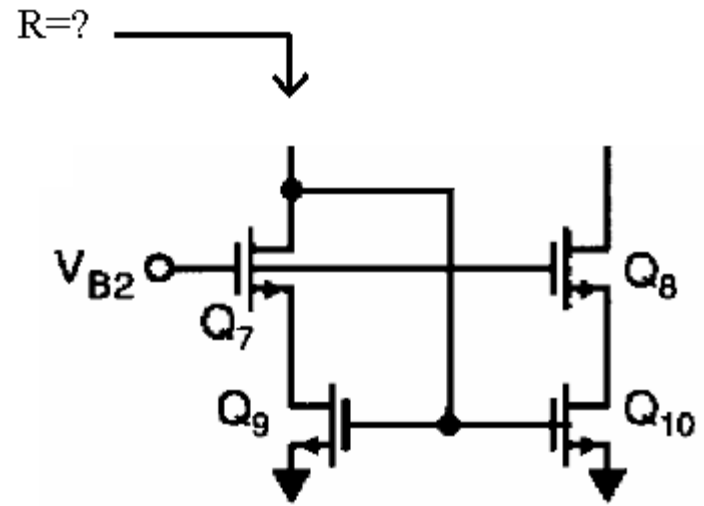

$$R \cong \frac{1}{g_{m9}}$$


Frequency Response

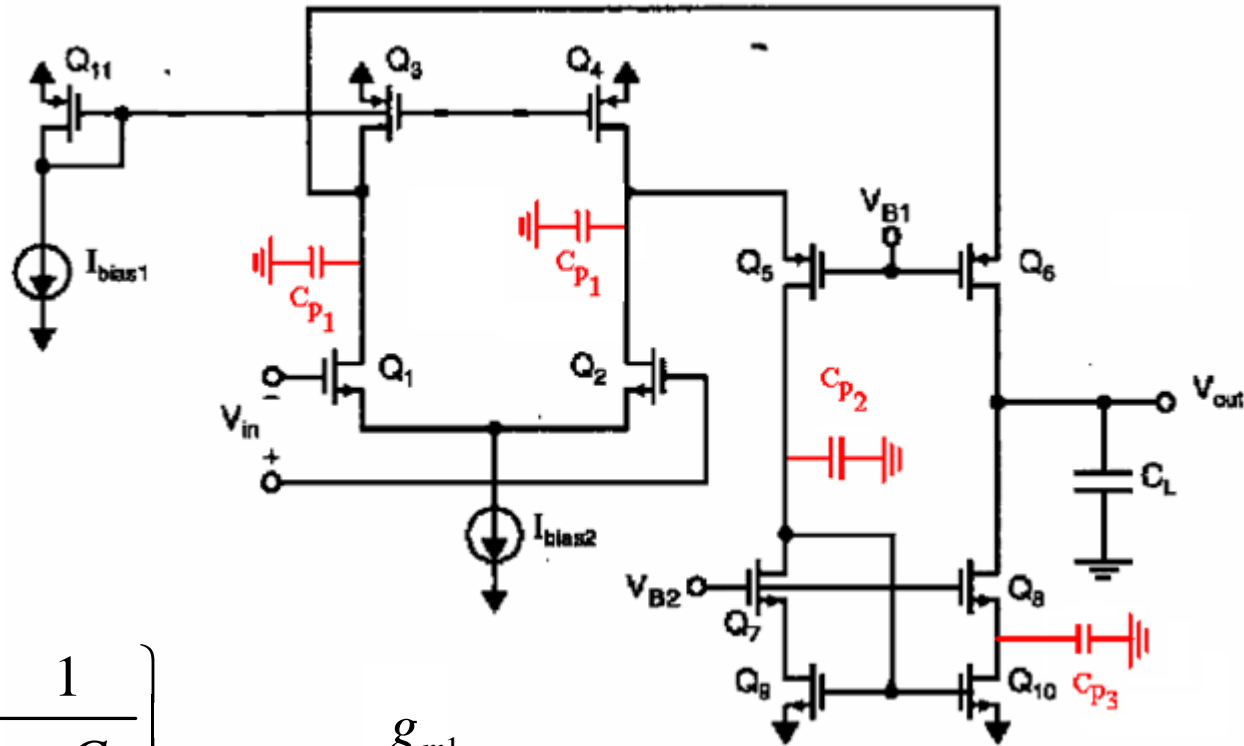


$$\left. \begin{aligned} \omega_{p1} &\cong \frac{1}{r_{out} C_L} \\ A_0 &= g_{m1} r_{out} \end{aligned} \right\} \Rightarrow \omega_{ta} = \frac{g_{m1}}{C_L}$$

$$\omega_{p2} \cong \frac{1}{\frac{1}{g_{m5}} C_{p1} + \frac{1}{g_{m9}} C_{p2} + \frac{1}{g_{m8}} C_{p3}}$$


Folded-Cascode Opamp (pmos-input)

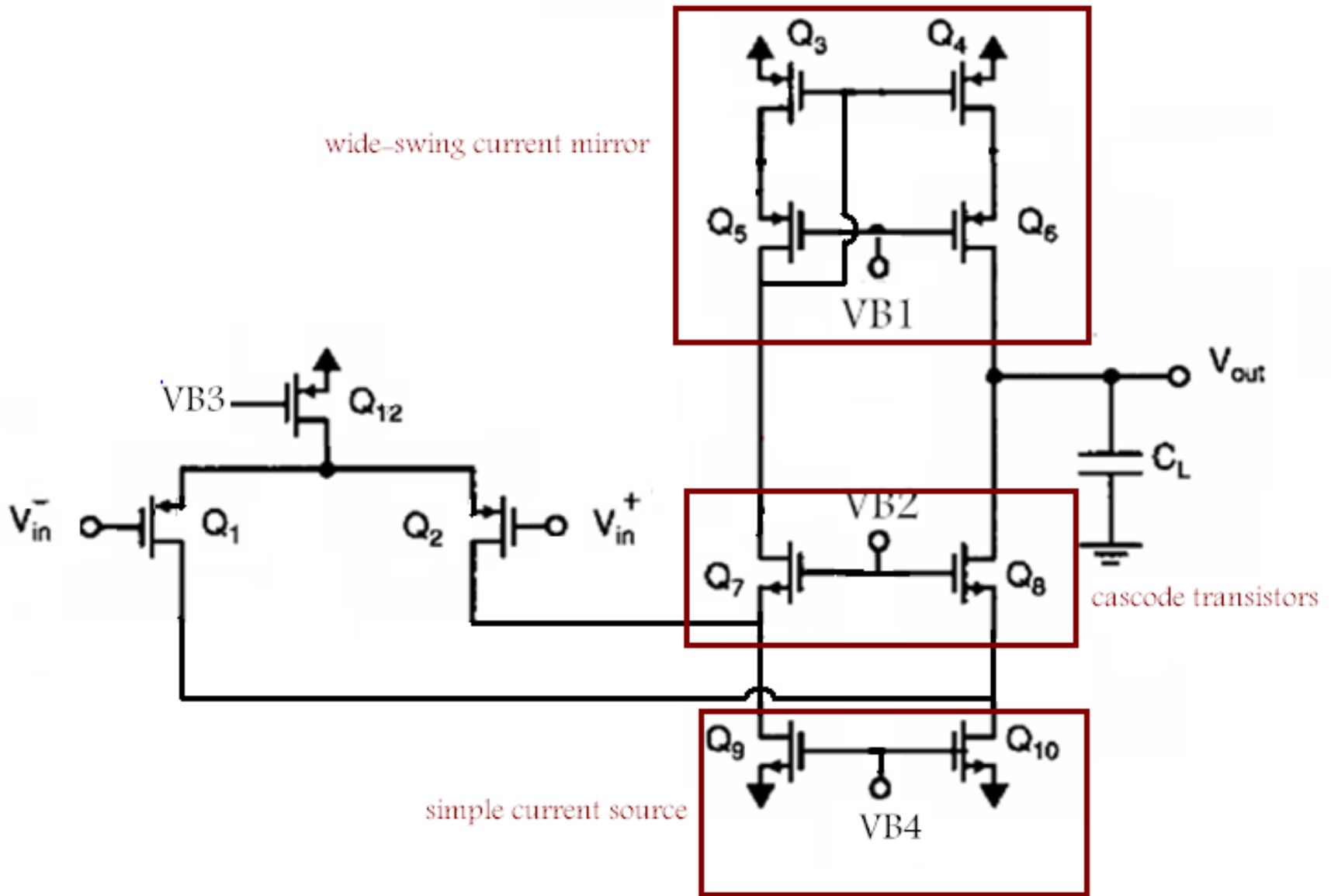

Folded-Cascode Opamp (pmos-input)

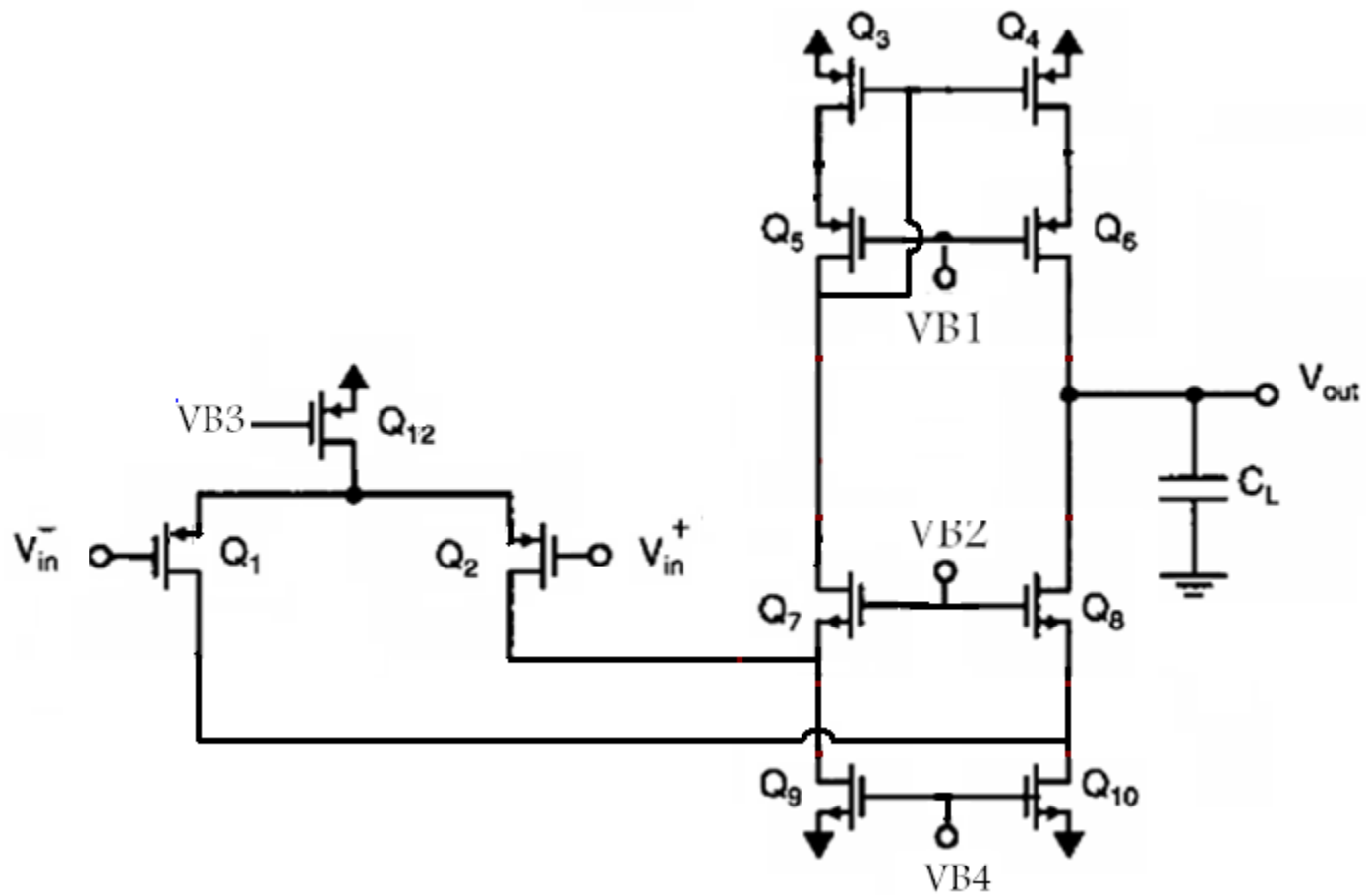

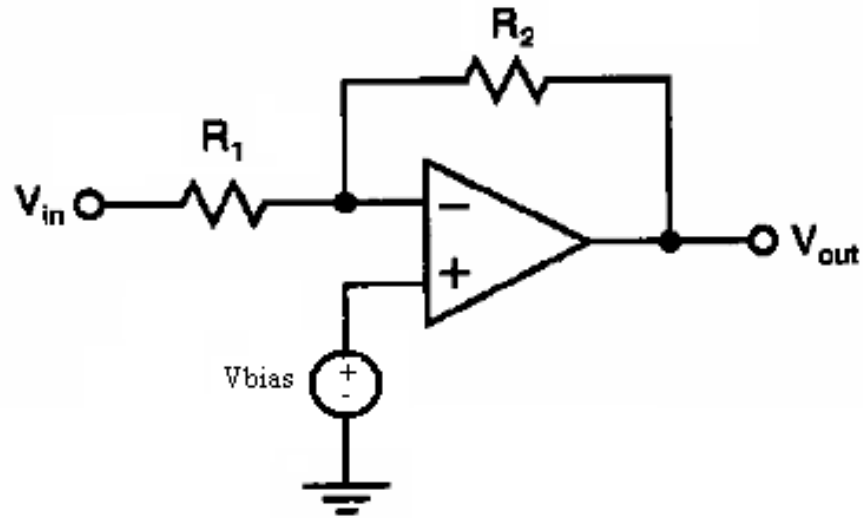
What is the DC voltage of the output node?



In a single-ended opamp, the DC voltage of the output node is determined by the feedback circuit around the opamp.

$$V_{out} = V_{bias} + \frac{R_2}{R_1} (V_{bias} - V_{in})$$

Fully Differential Folded-Cascode Opamp

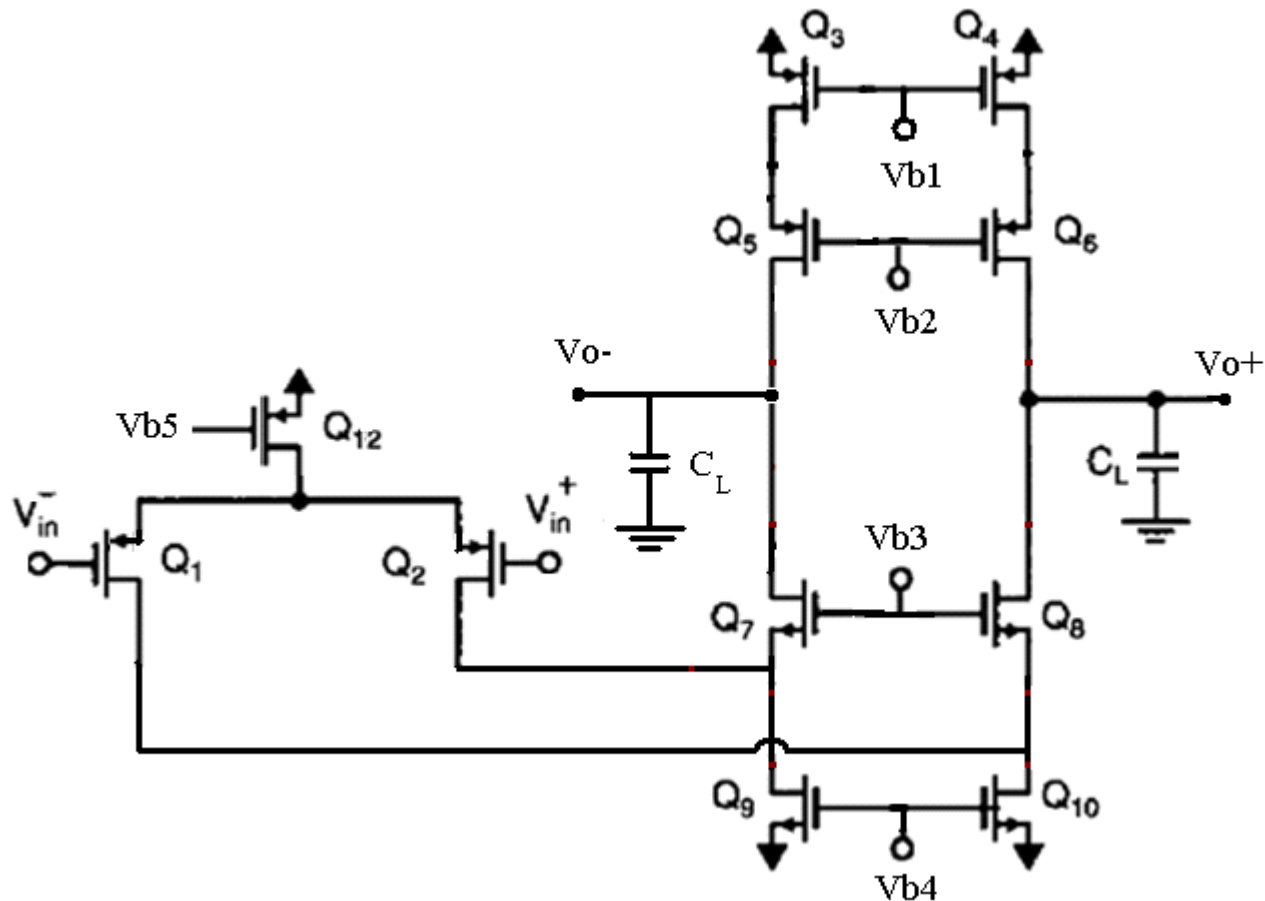

The bias voltages Vb1, Vb4, and Vb5 must be chosen so that the following relation is satisfied!!!


$$I_{D9} = 0.5I_{D12} + I_{D3}$$

The opamp is completely symmetric. So we can use the half-circuit of the opamp for AC analysis.


Fully Differential Folded-Cascode Opamp (half-circuit)

$$\left. \begin{aligned} \omega_{p1} &\approx \frac{1}{r_{out} C_L} \\ A_0 &= g_{m_i} r_{out} \end{aligned} \right\} \Rightarrow \omega_{ta} = \frac{g_{m_i}}{C_L}$$
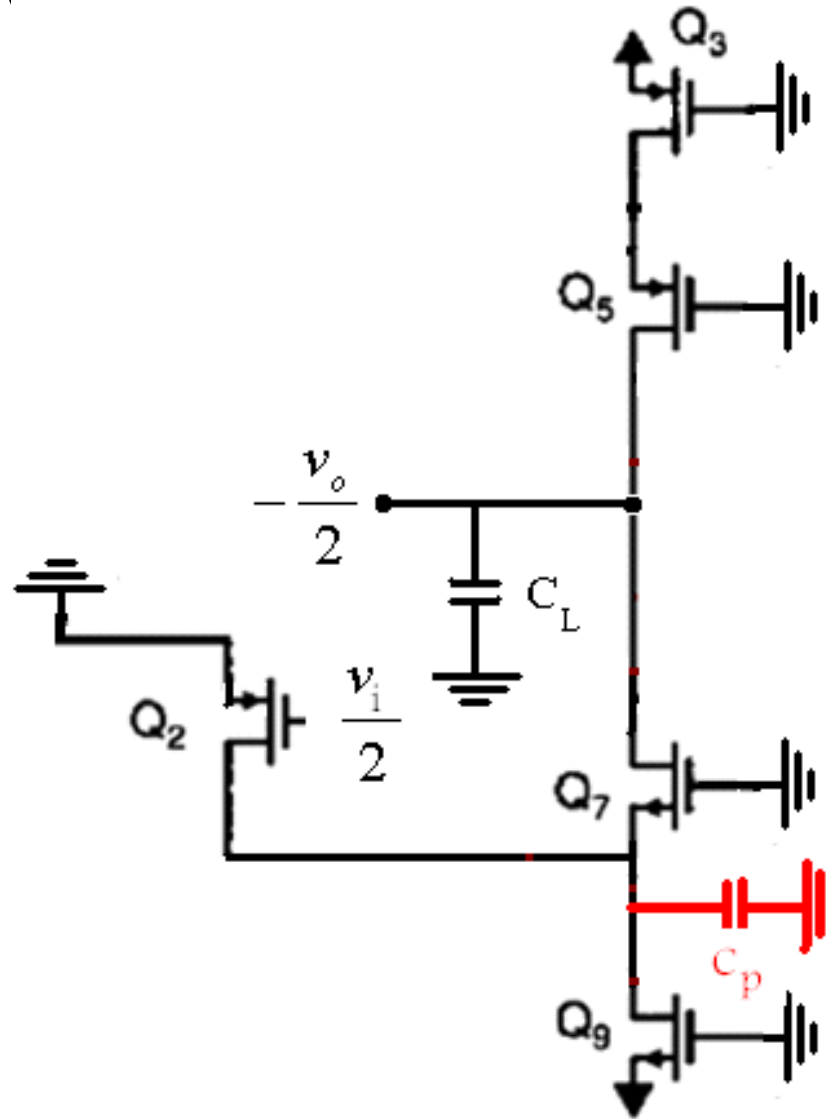
$$\omega_{p2} \approx \frac{1}{\frac{1}{g_{m_7}} C_p}$$



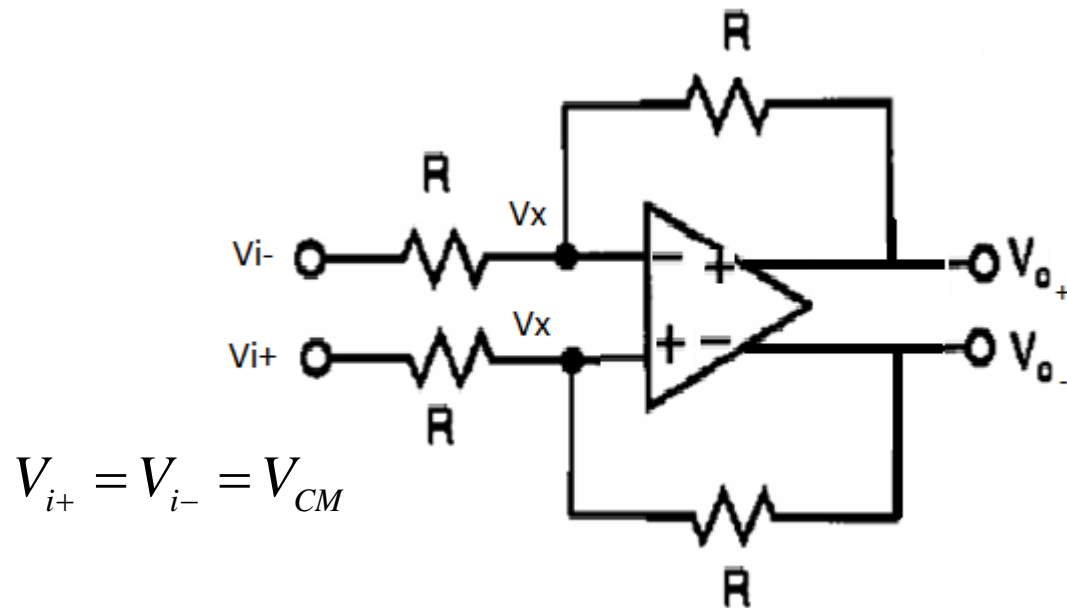What is the DC voltage of the output nodes?



In a single-ended opamp, the DC voltage of the output node is determined by the feedback circuit around the opamp.

$$\left. \begin{array}{l} I = \frac{V_{CM} - V_x}{R} \\ V_{CM} - V_o = 2RI \end{array} \right\} \Rightarrow V_{CM} - V_o = 2(V_{CM} - V_x) \Rightarrow V_{o+} = V_{o-} = V_o = 2V_x - V_{CM}$$


The DC voltage of the output nodes can not be determined!!!

Common-Mode Feedback Circuit (CMFB Circuit)


In a fully differential opamp, the CMFB circuit is employed inside the opamp to adjust the common-mode voltage of the output nodes identical to a predetermined voltage, V_{ref} .

$$\begin{array}{l} \text{CMFB Circuit} \Rightarrow \frac{V_{o+} + V_{o-}}{2} = V_{ref} \\ \text{KVL and KCL} \Rightarrow V_o = 2V_x - V_{CM} \end{array} \quad \Rightarrow \quad \begin{array}{l} V_{o+} = V_{o-} = V_{ref} \\ V_x = \frac{V_{ref} + V_{CM}}{2} \end{array}$$


Ideal CMFB Circuit (1)

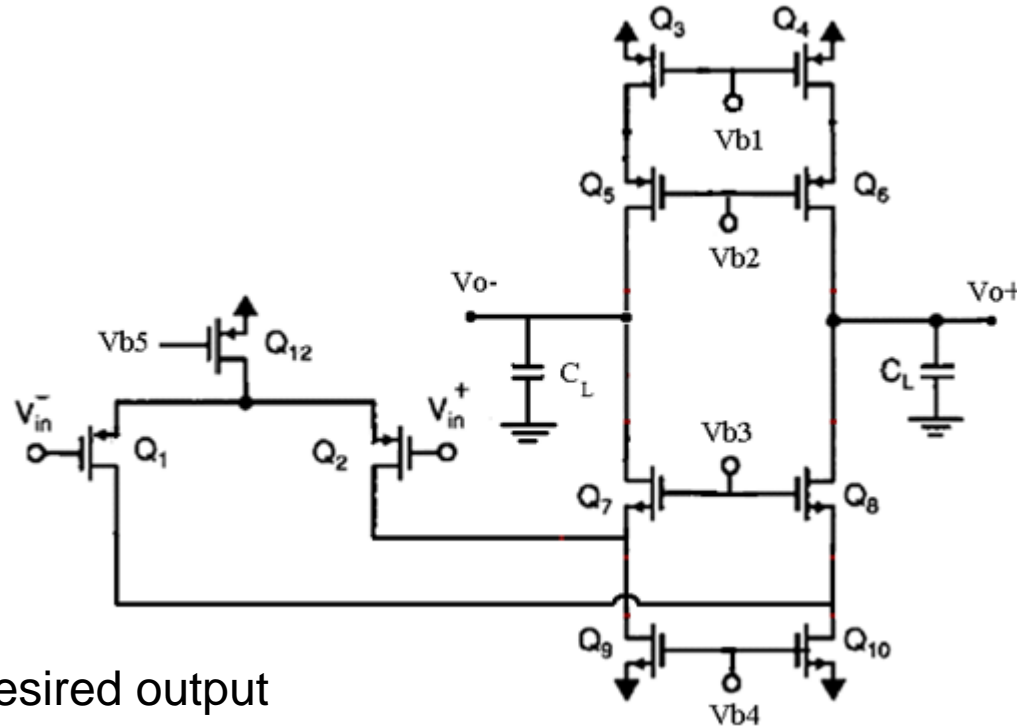

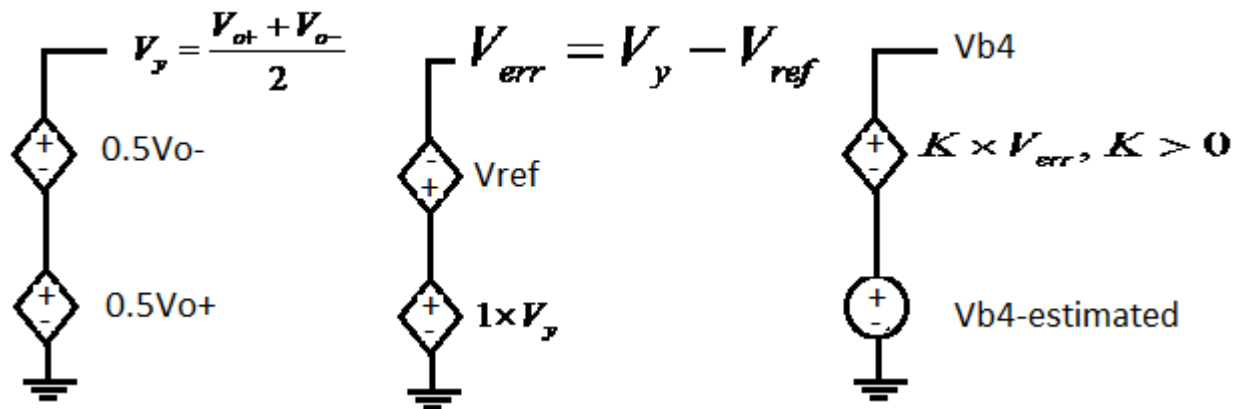
Vref denotes the desired output common-mode voltage.




Ideal CMFB Circuit (2)

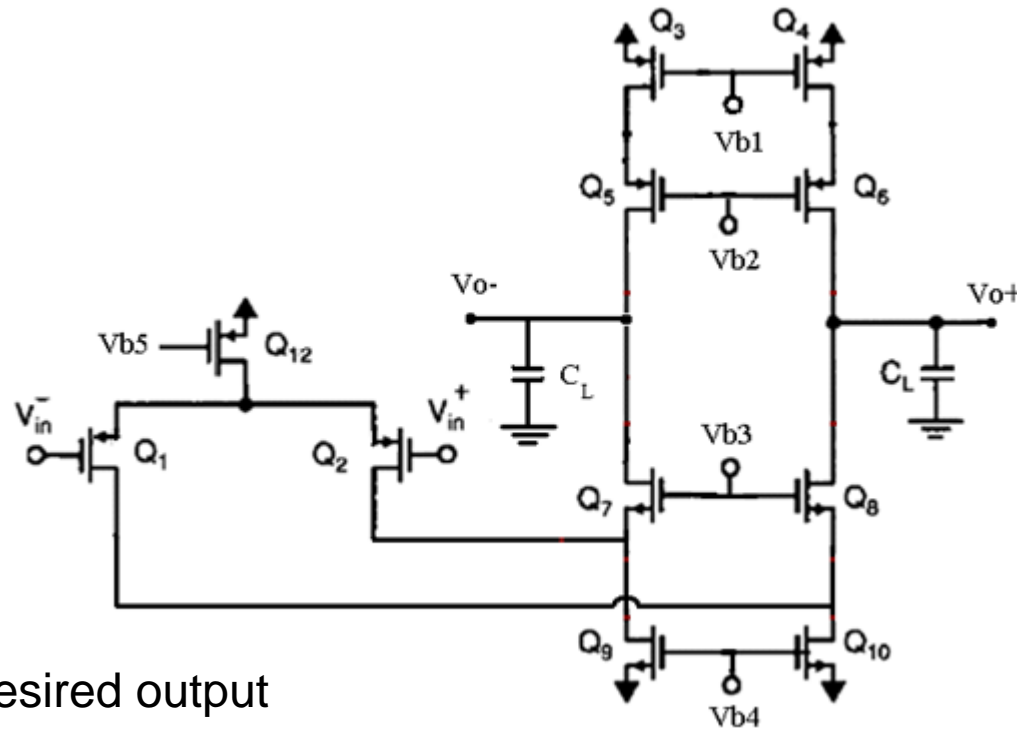

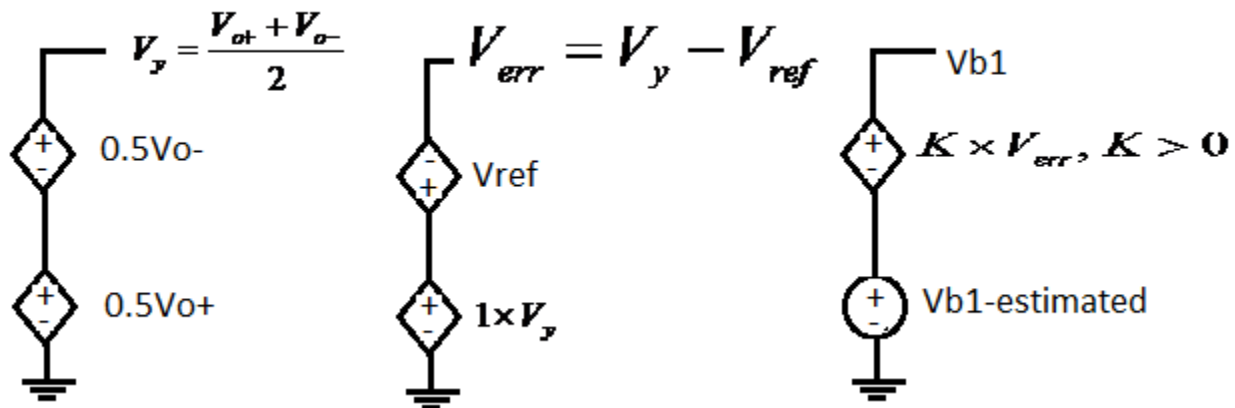
V_{ref} denotes the desired output common-mode voltage.





Ideal CMFB Circuit (3)

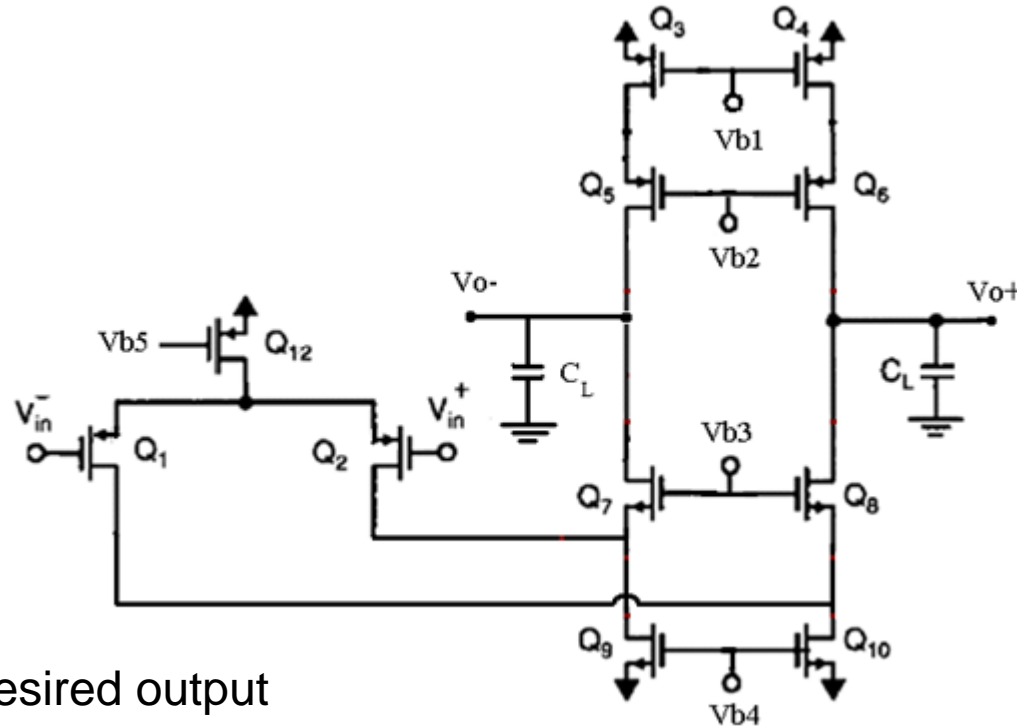

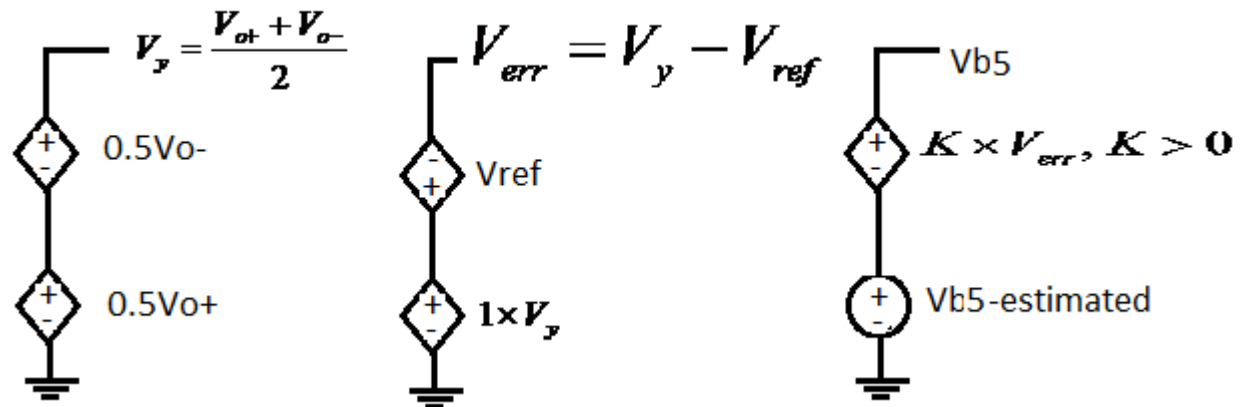V_{ref} denotes the desired output common-mode voltage.



Single-ended Telescopic Opamp

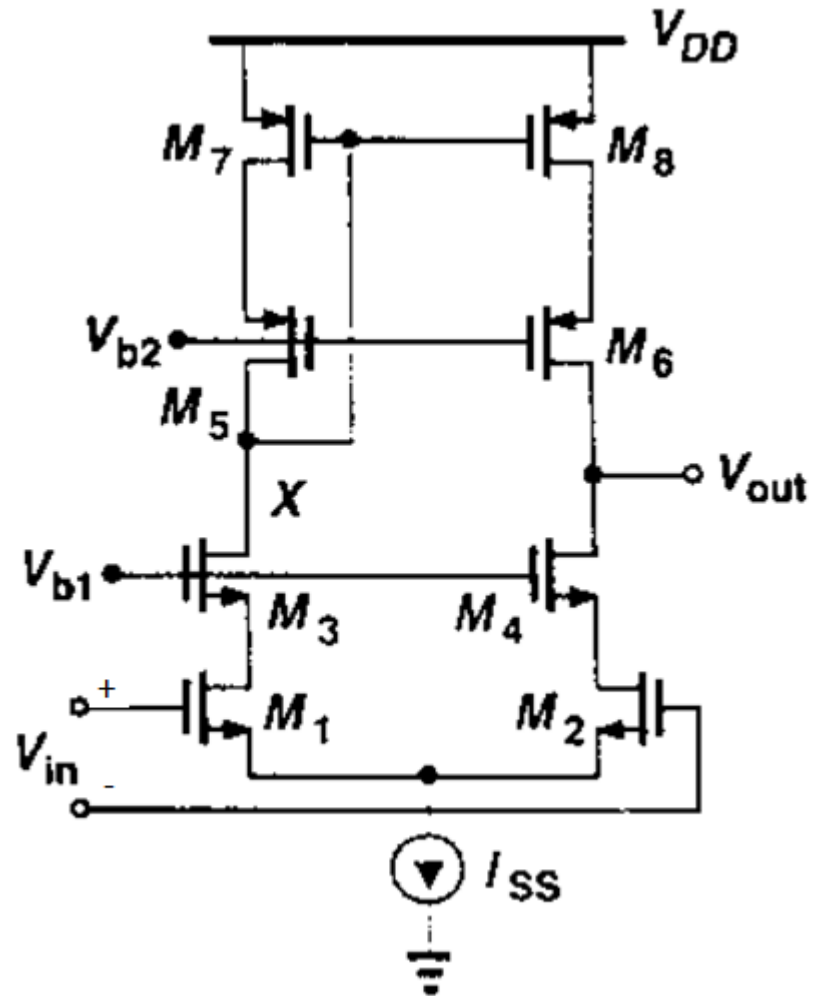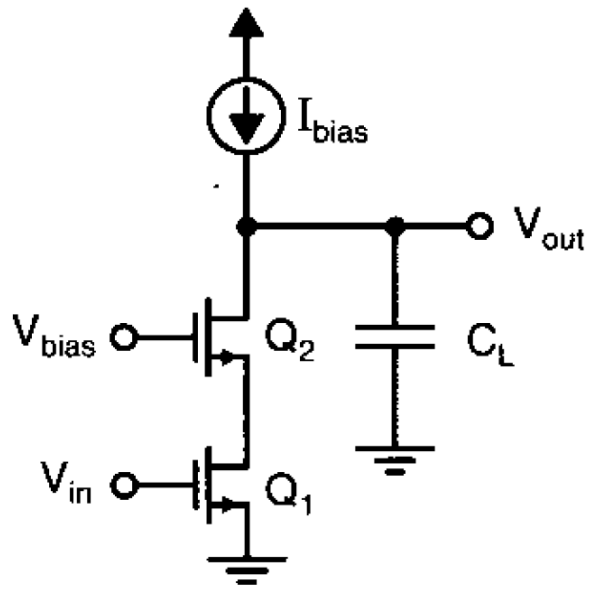


$$i_{sc} = g_{m1} v_i$$

$$r_{out} \cong g_{m4} r_{ds4} r_{ds2} \parallel g_{m6} r_{ds6} r_{ds8}$$

$$v_o = r_{out} i_{sc} \Rightarrow A_V = g_{m1} r_{out}$$

Slew Rate

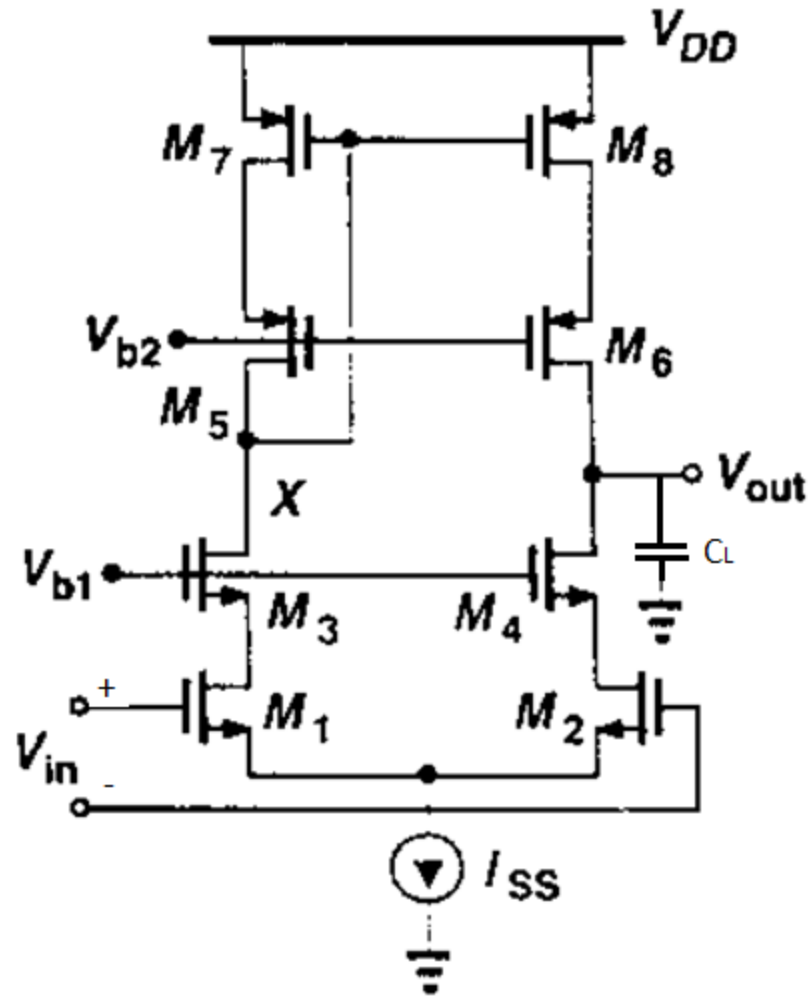


$$SR^+ = SR^- = \frac{I_{SS}}{C_L}$$


Frequency Response

$$\left. \begin{aligned} \omega_{p1} &\cong \frac{1}{r_{out} C_L} \\ A_0 &= g_{m_i} r_{out} \end{aligned} \right\} \Rightarrow \omega_{ta} = \frac{g_{m_i}}{C_L}$$
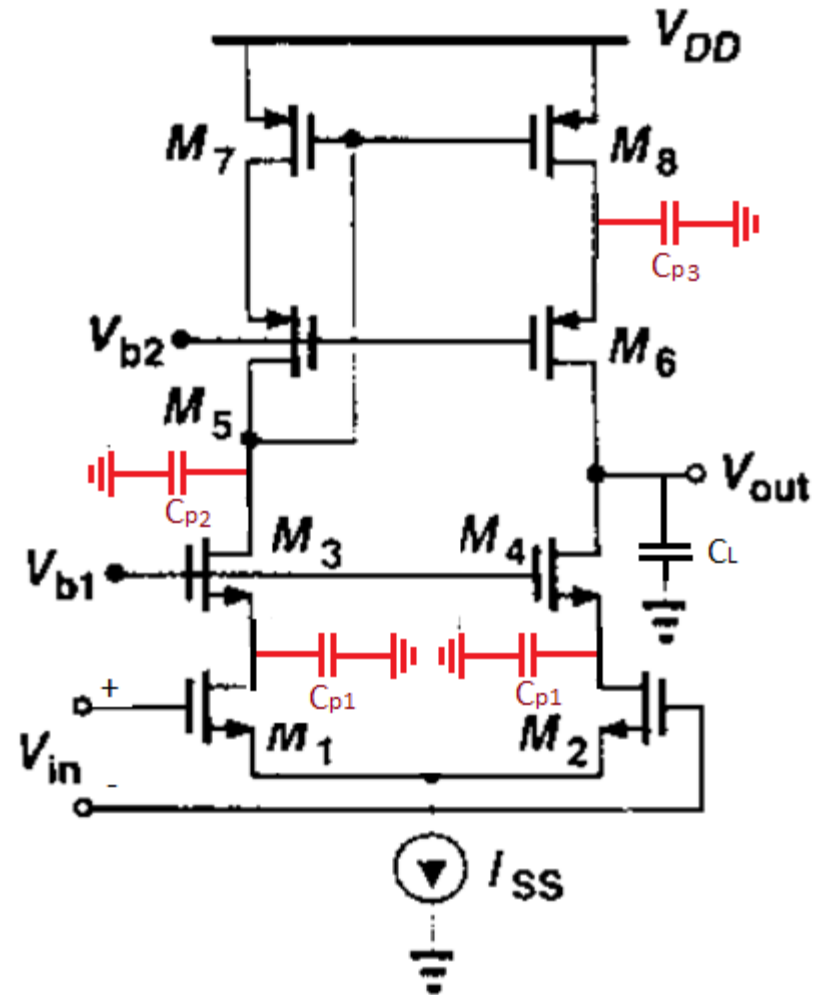
$$\omega_{p2} \cong \frac{1}{\frac{1}{g_{m3}} C_{p1} + \frac{1}{g_{m7}} C_{p2} + \frac{1}{g_{m6}} C_{p3}}$$



Input common-mode range and output swing

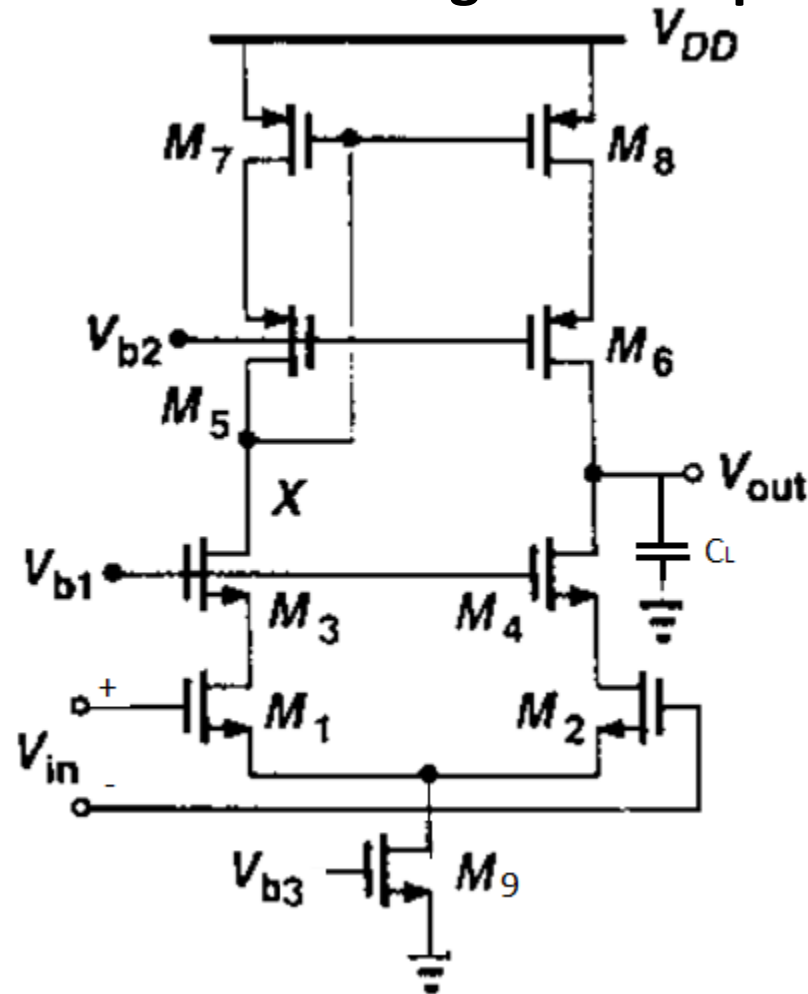


Output swing:

$$V_{B1} - V_{tn} \leq V_{out} \leq V_{B2} + |V_{tp}|$$


Input common-mode range:

$$V_{tn} + V_{eff1} + V_{eff9} \leq V_{cmi} \leq V_{B1} - V_{eff3}$$

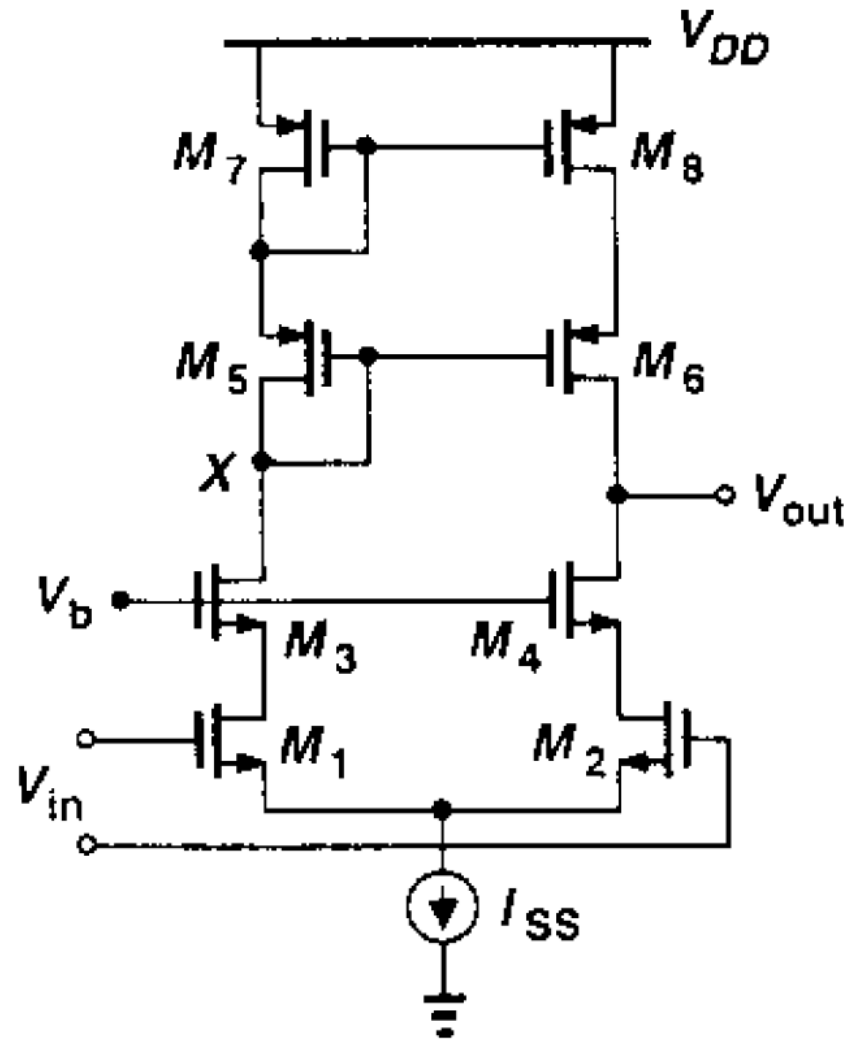Telescopic Opamp without wide-swing current source



Fully Differential Telescopic Opamp

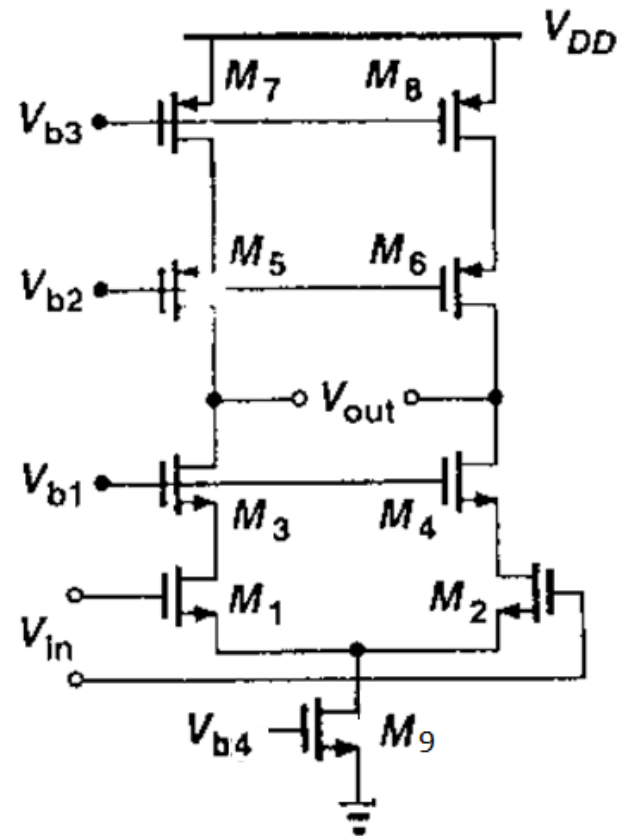

The bias voltages V_{b3} and V_{b4} must be chosen so that the following relation is satisfied!!!


$$I_{D7} = 0.5 I_{D9}$$

The opamp is completely symmetric. So we can use the half-circuit of the opamp for AC analysis.


Fully Differential Telescopic Opamp (half-circuit)

$$\left. \begin{aligned} \omega_{p1} &\cong \frac{1}{r_{out} C_L} \\ A_0 &= g_{m1} r_{out} \end{aligned} \right\} \Rightarrow \omega_{ta} = \frac{g_{m1}}{C_L}$$

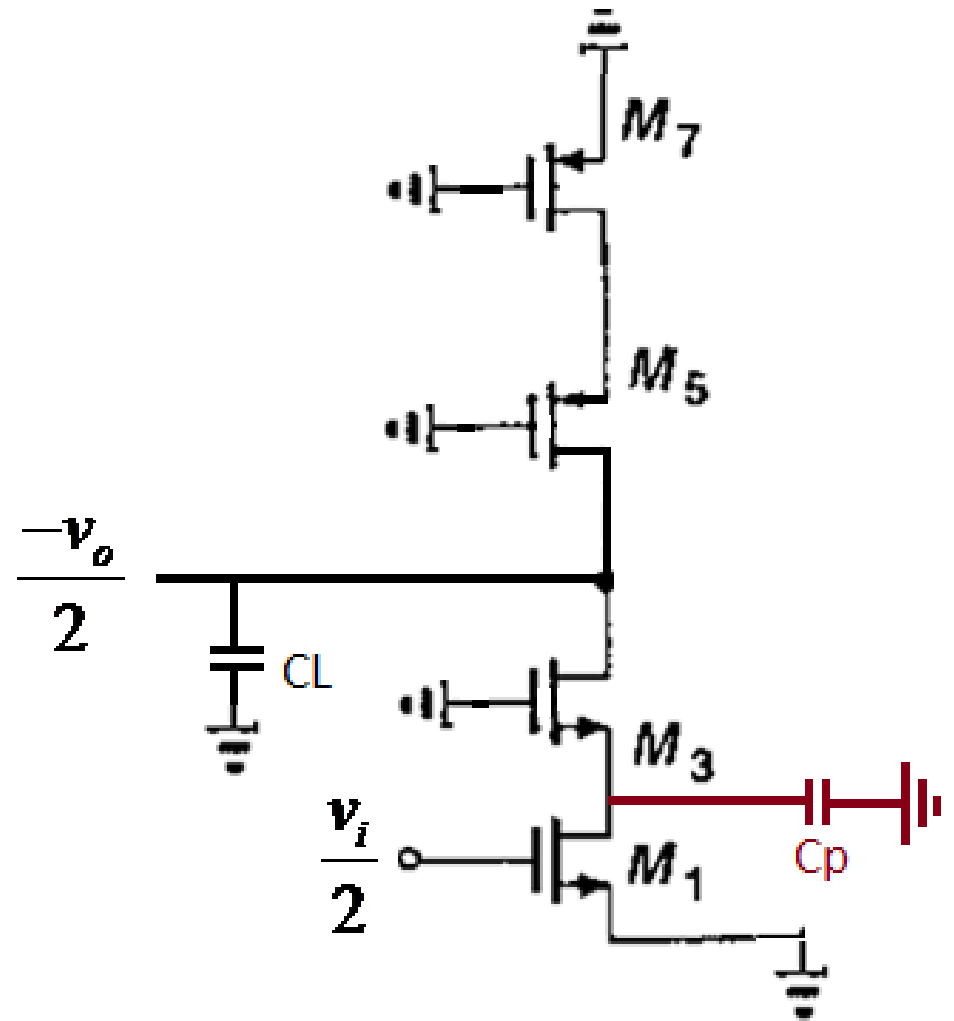
$$\omega_{p2} \cong \frac{1}{\frac{1}{g_{m3}} C_p}$$




Ideal CMFB Circuit (1)

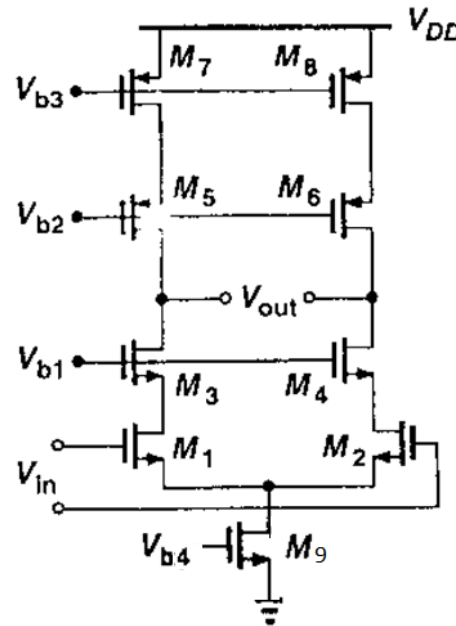

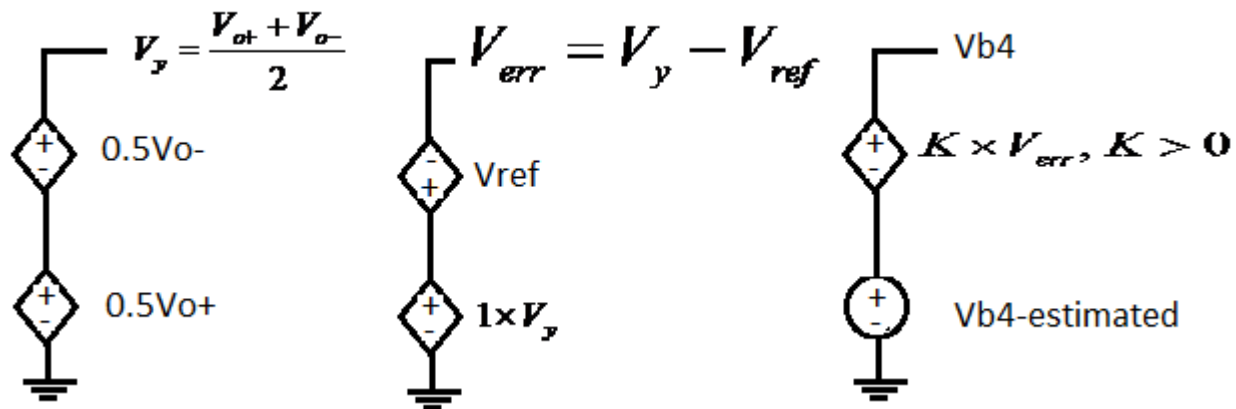
V_{ref} denotes the desired output common-mode voltage.



Ideal CMFB Circuit (2)

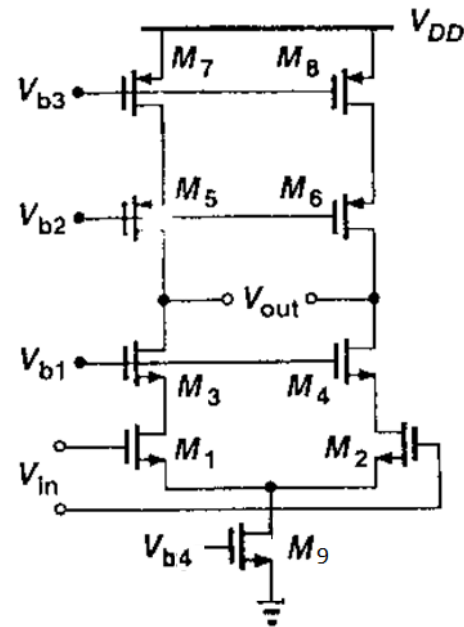

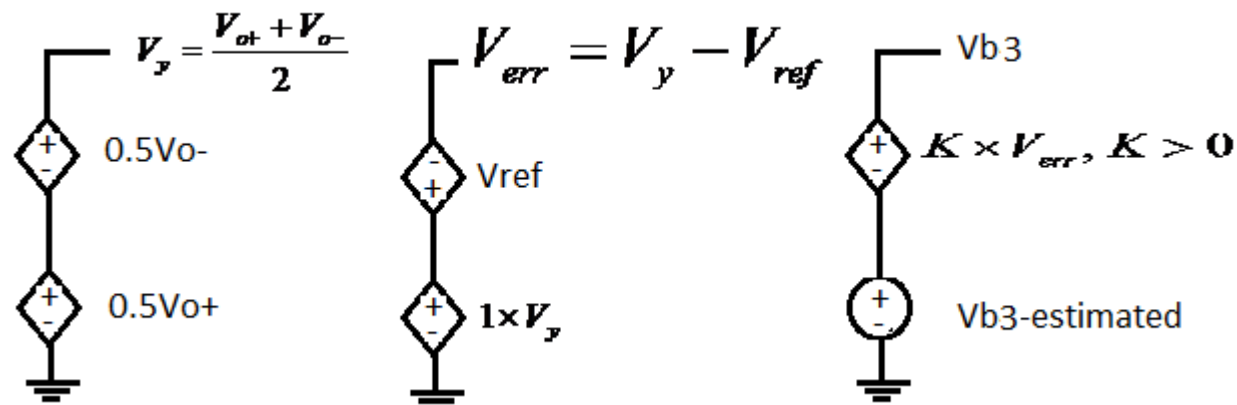V_{ref} denotes the desired output common-mode voltage.




Fully Differential Two-Stage Opamp (nmos input)

$$A_0 = g_{m1} R_1 g_{m5} R_2$$


$$\omega_{ta} = \frac{g_{m1}}{C_M}$$
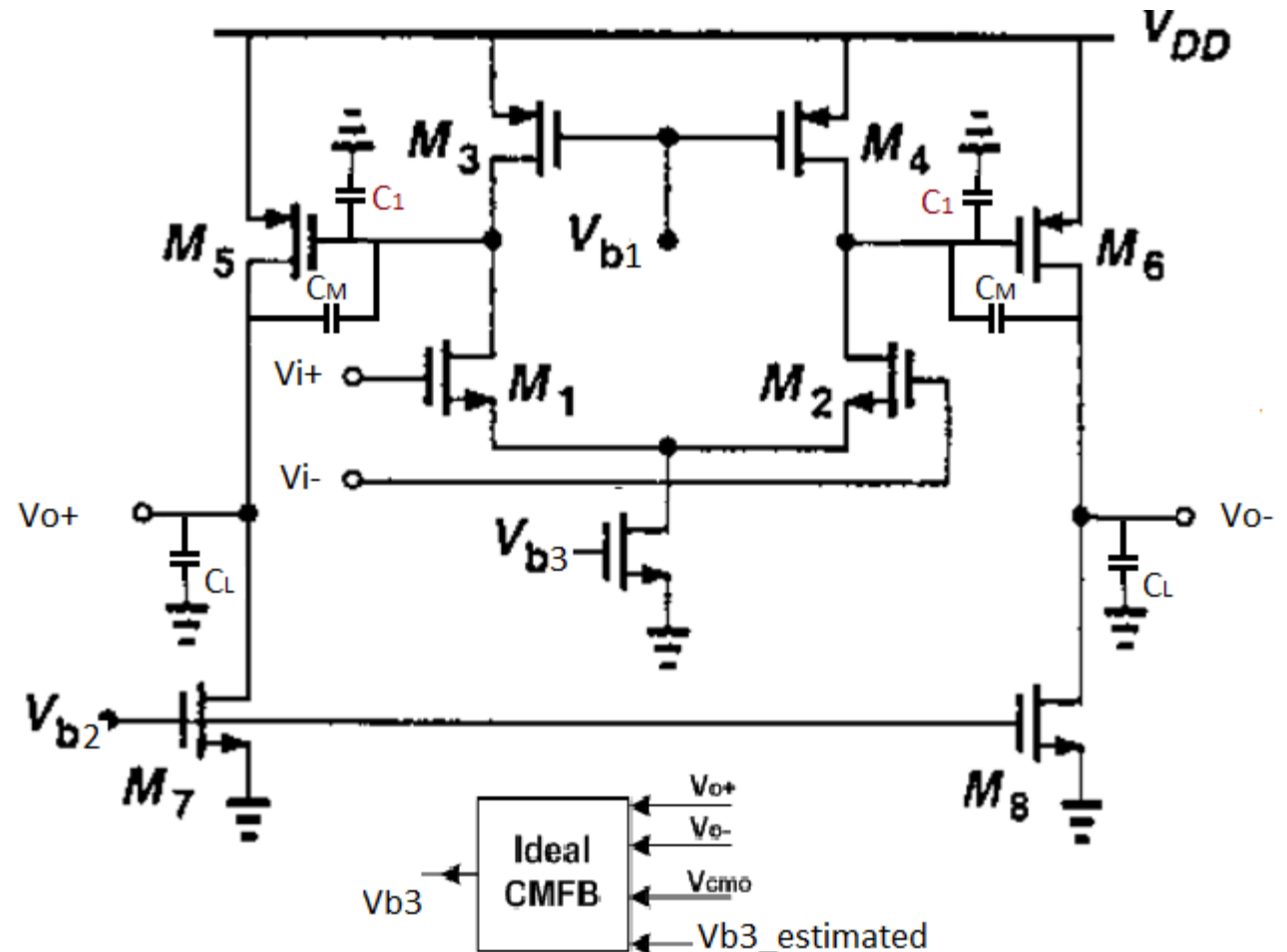
$$\omega_{p2} \cong \frac{g_{m5}}{C_1 + C_L}$$



C1 denotes the parasitic capacitance.

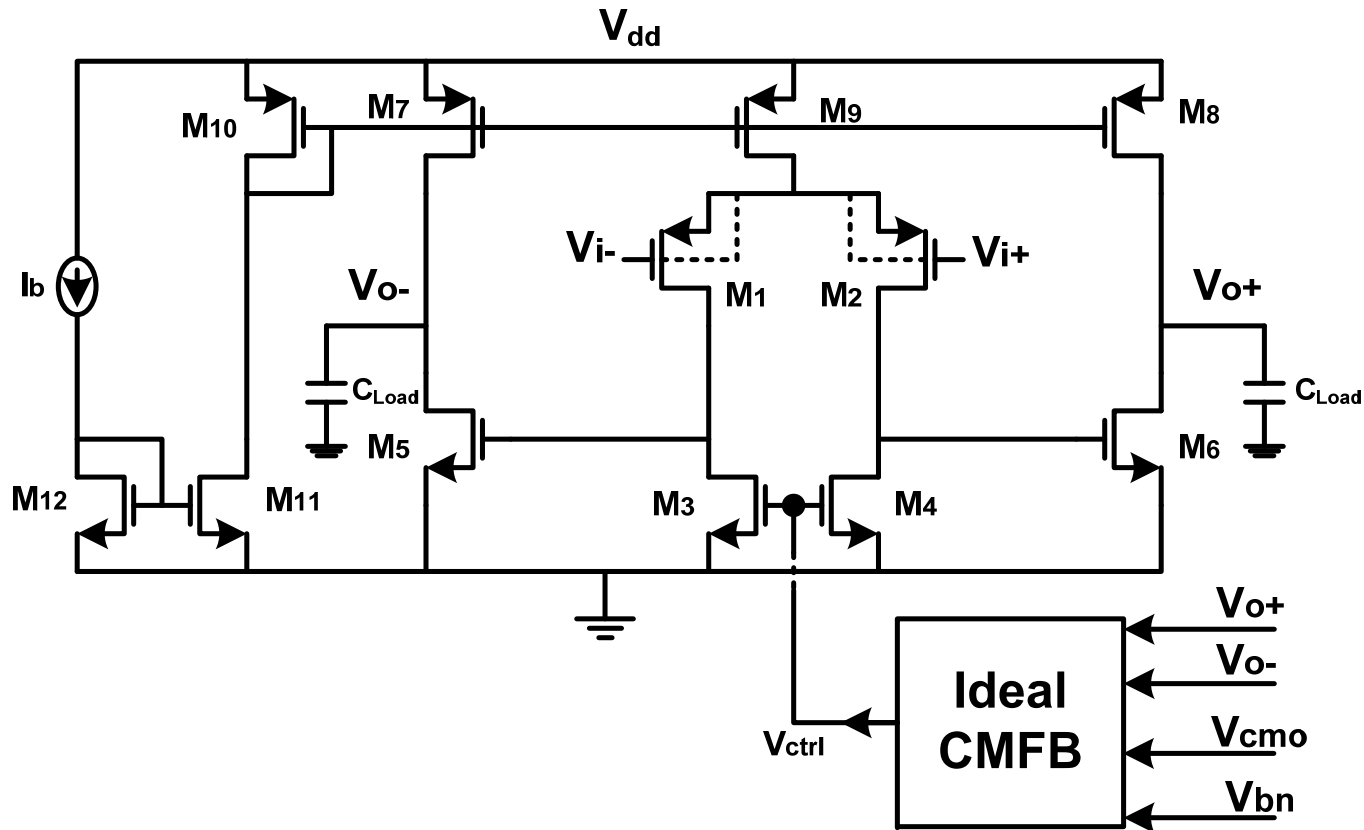Fully Differential Two-Stage Opamp (pmos input)




Fully Differential Two-Stage Opamp (First Stage: Telescopic Cascode)

$$A_0 = g_{m1} R_1 g_{m9} R_2$$



$$\omega_{ta} = \frac{g_{m1}}{C_M}$$
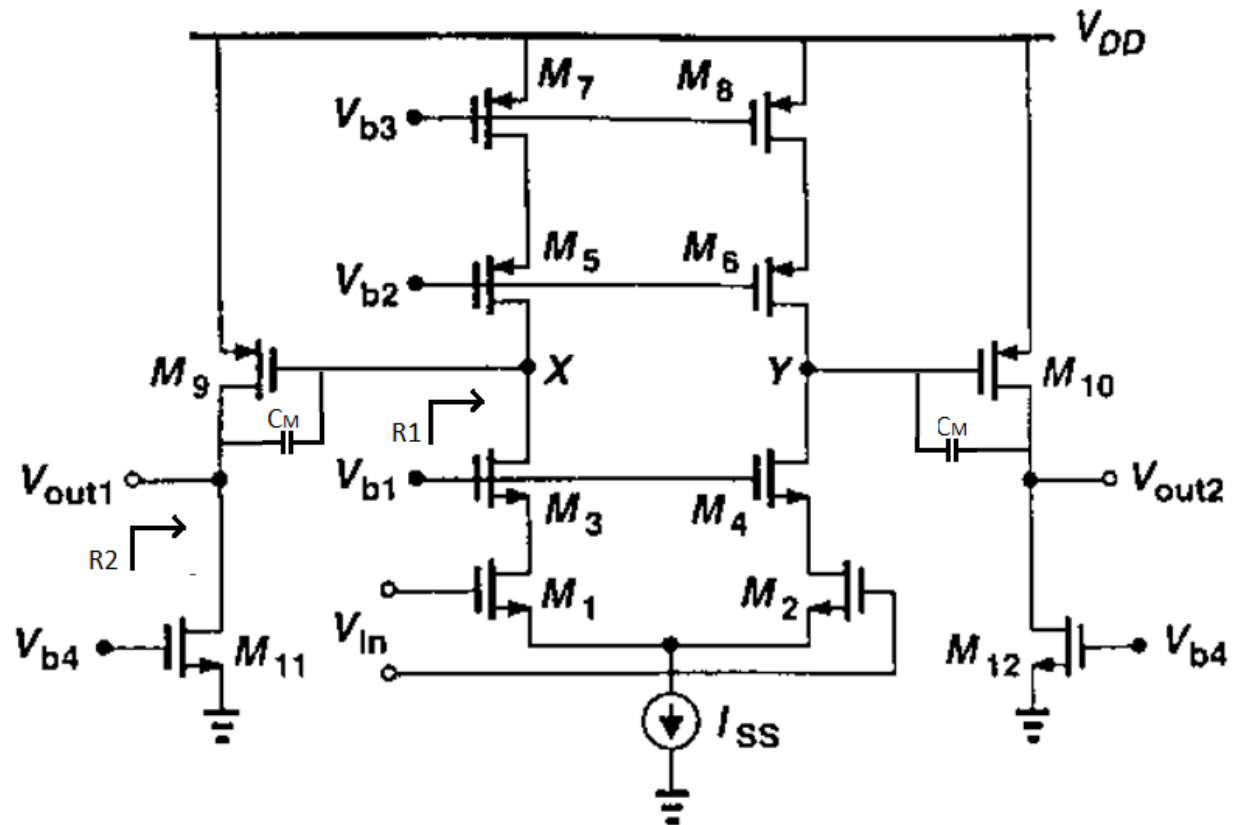
$$\omega_{p2} \cong \frac{g_{m9}}{C_1 + C_L}$$




C1 denotes the parasitic capacitance at node X.
Miller compensation method is utilized.


Gain-Boosting Opamp

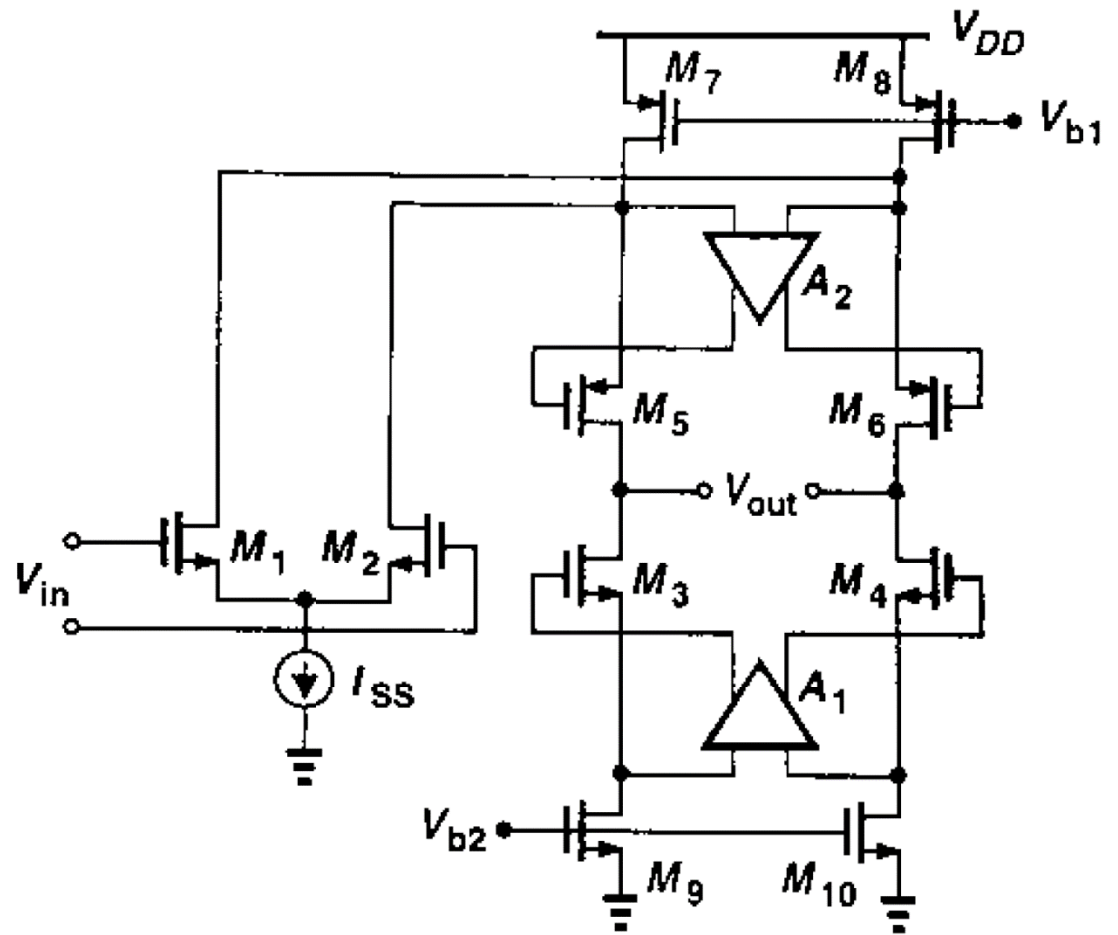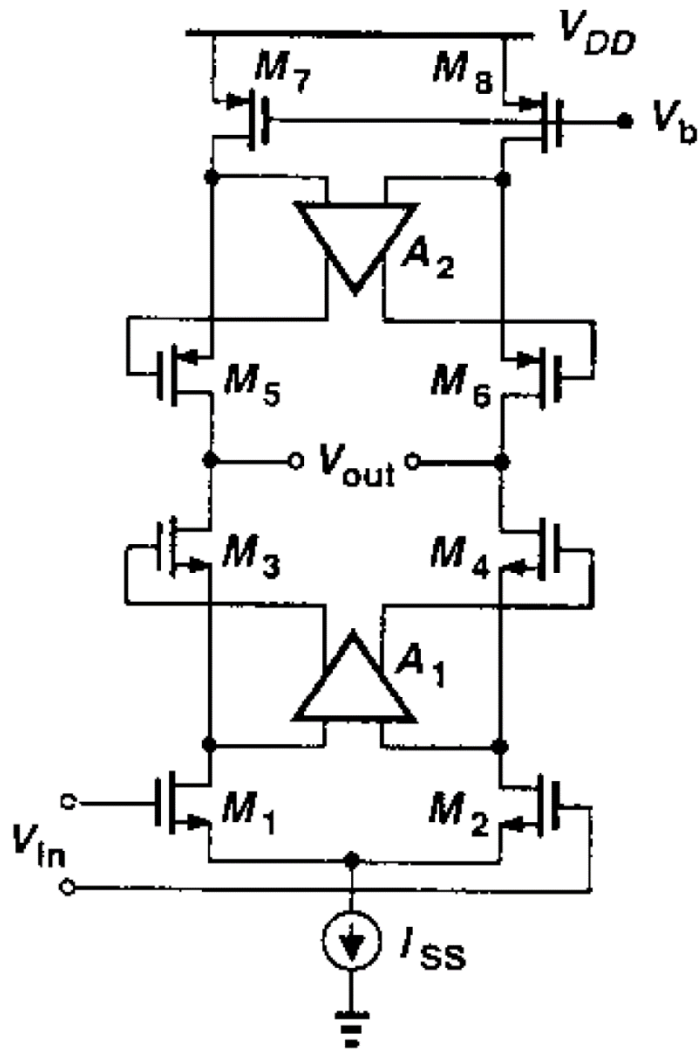

Differential Pair as an Auxiliary Opamp

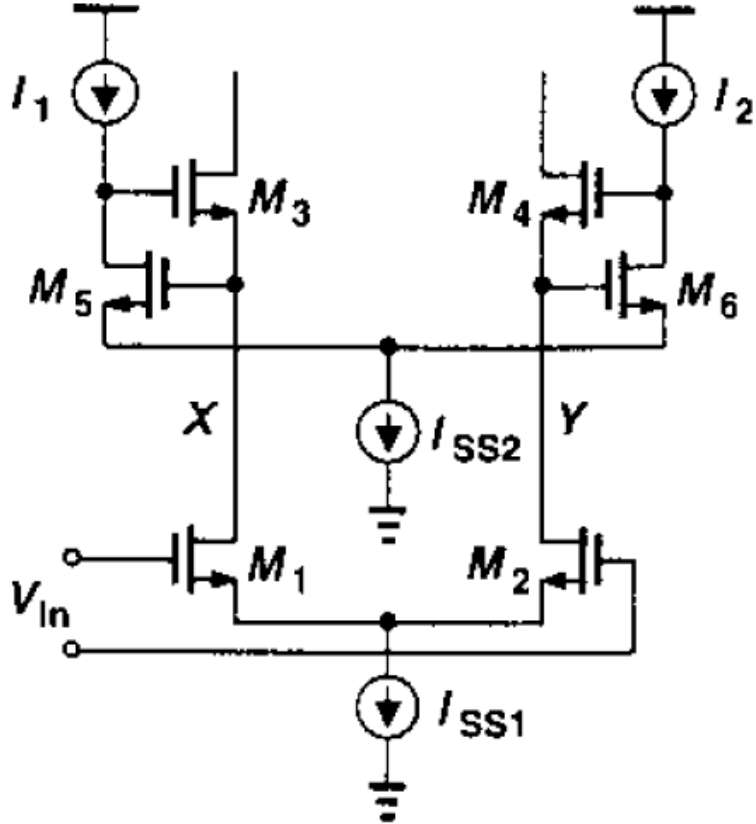

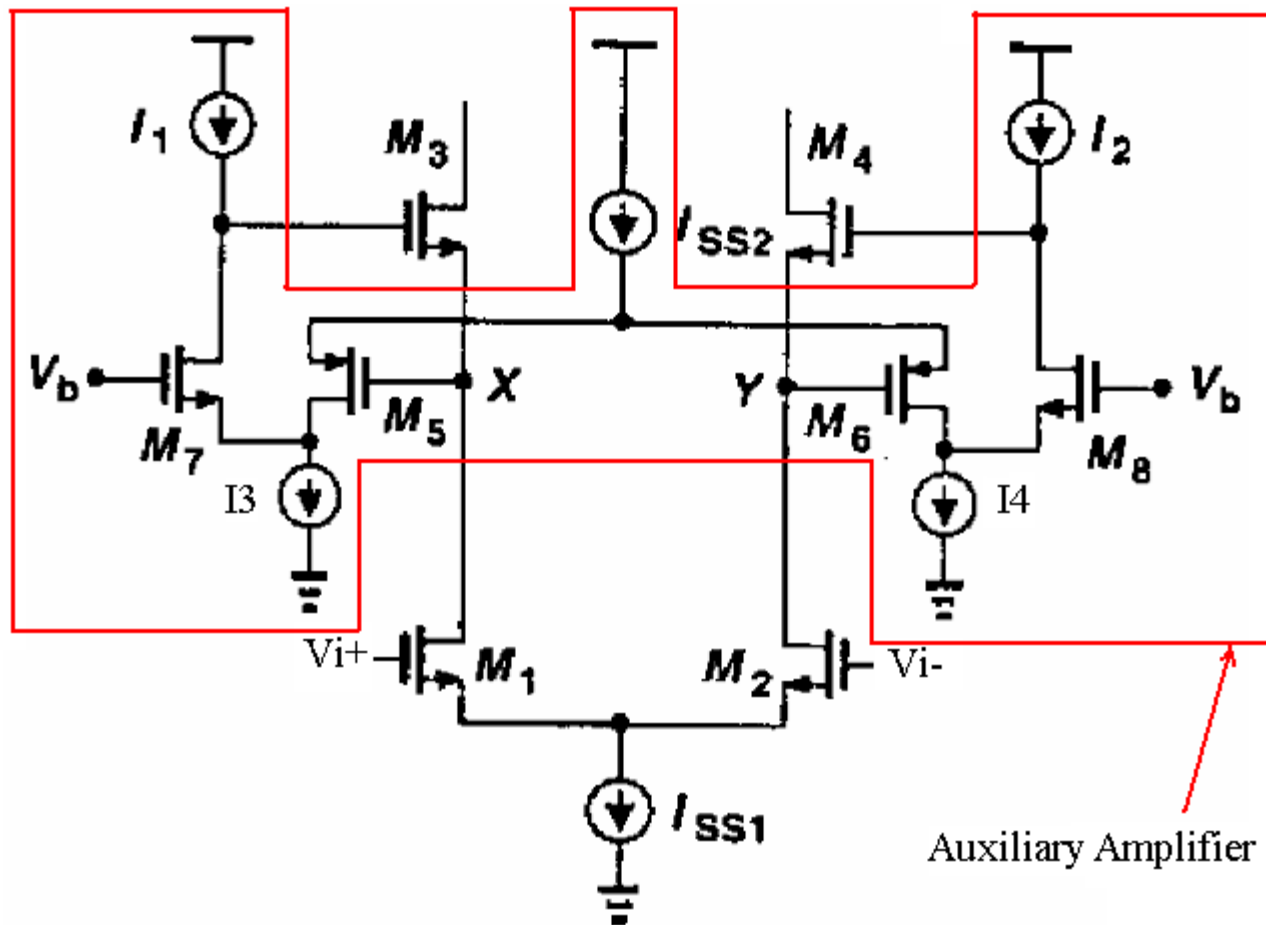Folded-Cascode Circuit as an Auxiliary Opamp



Comparison of Performance of Various Opamp Topologies

	Gain	Output Swing	Speed	Power Dissipation	Noise
Telescopic	Medium	Low	Highest	Low	Low
Folded-Cascode	Medium	Medium	High	Medium	Medium
Two-Stage	High	Highest	Low	Medium	Low
Gain-Boosted	High	Medium	Medium	High	Medium