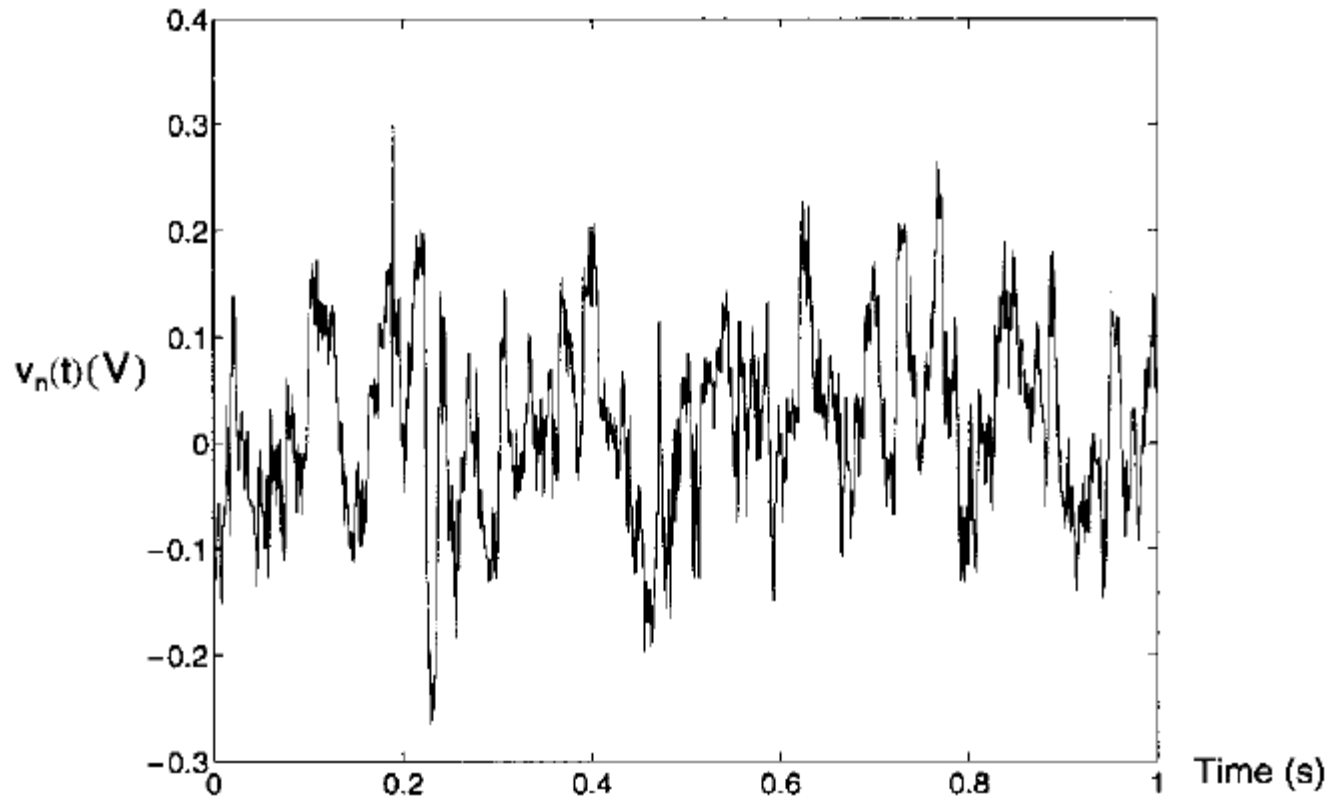


Noise Analysis and Modeling



Throughout this chapter we will assume all noise signals have a mean value of zero. We also assume that random signals are Ergodic.

Time-Domain Analysis

RMS (root mean square) Value is defined:

$$V_{n(\text{rms})} \equiv \left[\frac{1}{T} \int_0^T v_n^2(t) dt \right]^{1/2}$$

where T is a suitable averaging time interval.

The normalized noise power is given by


$$P_{\text{diss}} = \frac{V_{n(\text{rms})}^2}{1 \Omega} = V_{n(\text{rms})}^2$$

SNR is defined as follows:

$$\text{SNR} \equiv 10 \log \left[\frac{\text{signal power}}{\text{noise power}} \right]$$

$$\text{SNR} = 10 \log \left[\frac{V_{x(\text{rms})}^2}{V_{n(\text{rms})}^2} \right] = 20 \log \left[\frac{V_{x(\text{rms})}}{V_{n(\text{rms})}} \right]$$

Noise Summation

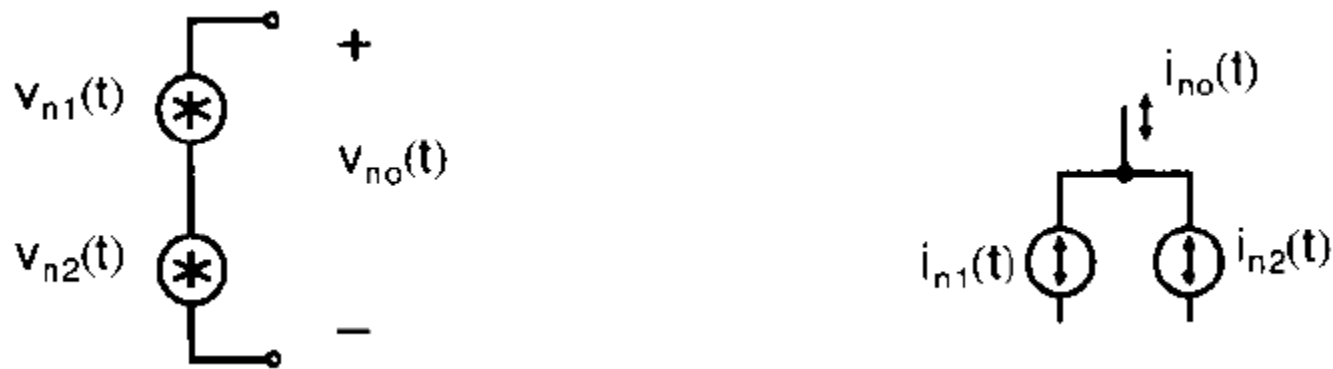

$$v_{no}(t) = v_{n1}(t) + v_{n2}(t)$$

$$V_{no(rms)}^2 = \frac{1}{T} \int_0^T [v_{n1}(t) + v_{n2}(t)]^2 dt$$

$$V_{no(rms)}^2 = V_{n1(rms)}^2 + V_{n2(rms)}^2 + \frac{2}{T} \int_0^T v_{n1}(t)v_{n2}(t) dt$$

Definition of **correlation coefficient**:

$$C \equiv \frac{\frac{1}{T} \int_0^T v_{n1}(t)v_{n2}(t) dt}{V_{n1(rms)} V_{n2(rms)}}$$

Noise Summation

$$V_{no(rms)}^2 = V_{n1(rms)}^2 + V_{n2(rms)}^2 + 2CV_{n1(rms)}V_{n2(rms)}$$

It can be shown that the correlation coefficient always satisfies the condition $-1 \leq C \leq 1$. Also, a value of $C = \pm 1$ implies the two signals are fully correlated, whereas $C = 0$ indicates the signals are uncorrelated.

In the case of two uncorrelated signals, the mean-squared value of their sum is given by



$$V_{no(rms)}^2 = V_{n1(rms)}^2 + V_{n2(rms)}^2$$

In the case of two fully correlated signals, the mean-squared value of their sum is

$$V_{no(rms)}^2 = [V_{n1(rms)} \pm V_{n2(rms)}]^2$$

Frequency-Domain Analysis


Noise Spectral Density: (PSD)

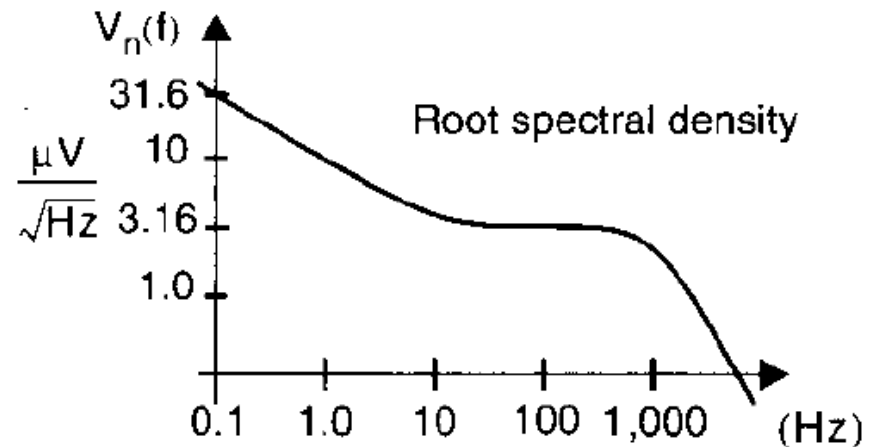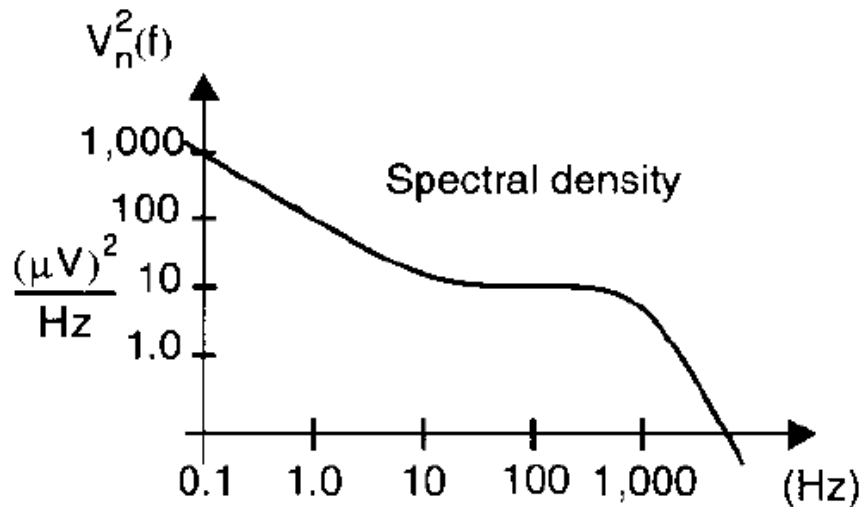

It is proven that:

$$V_{n(\text{rms})}^2 = \int_0^{\infty} V_n^2(f) df$$

White Noise

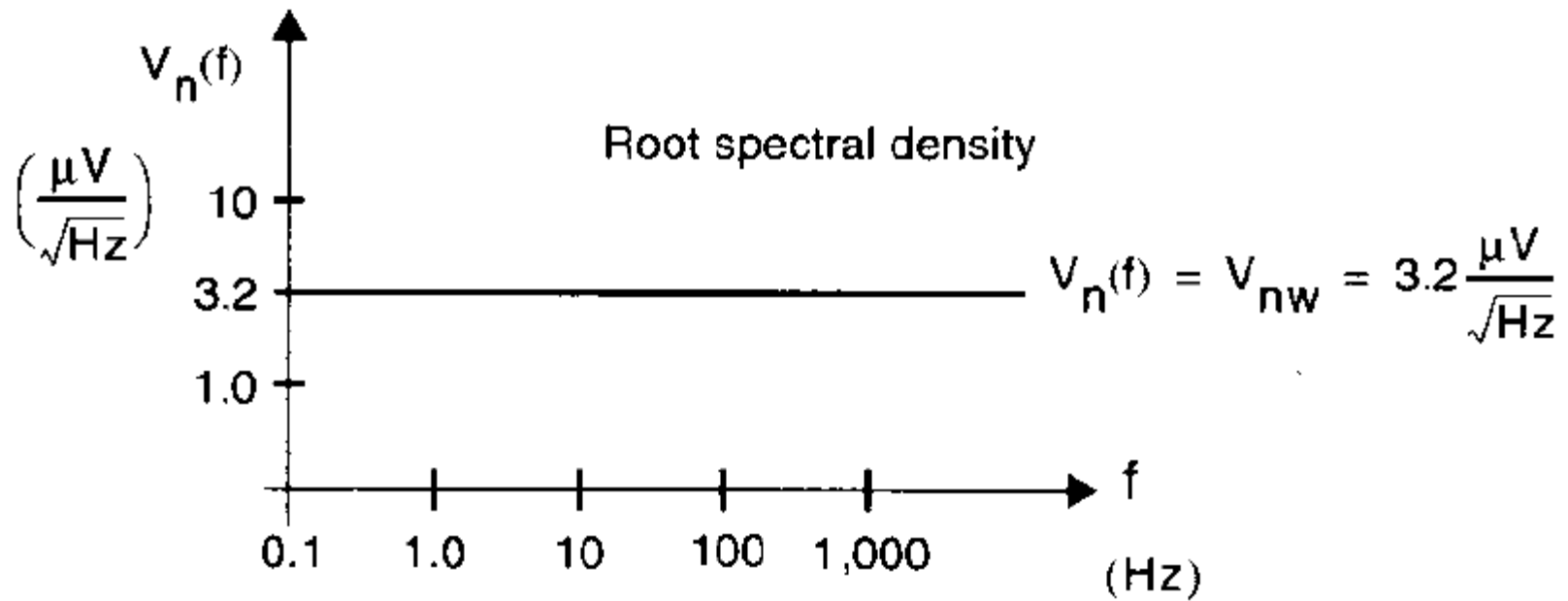


$$V_n(f) = V_{nw}$$

1/f or Flicker Noise

$$V_n^2(f) = \frac{k_v^2}{f}$$

$$V_n(f) = \frac{k_v}{\sqrt{f}}$$

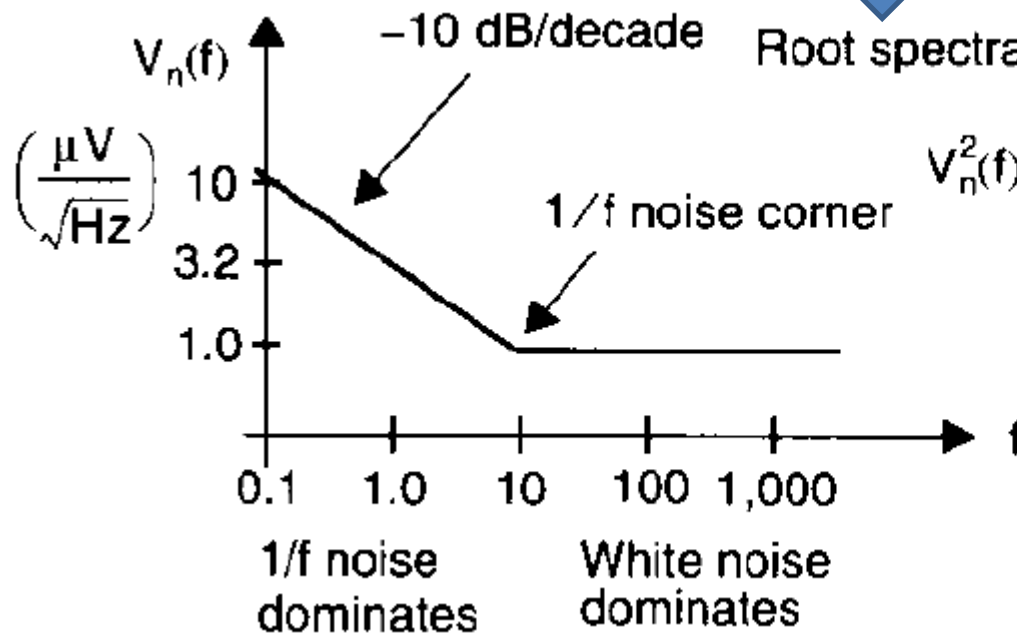
A noise signal that has both 1/f and white noise.



Root spectral density


$$V_n^2(f) \approx \frac{(3.2 \times 10^{-6})^2}{f} + (1 \times 10^{-6})^2$$

Filtered Noise

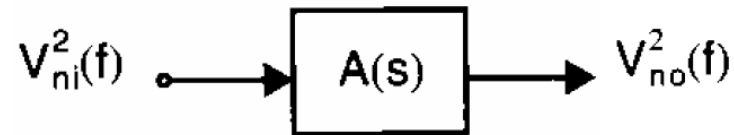

$$V_{no}^2(f) = |A(j2\pi f)|^2 V_{ni}^2(f)$$



$$V_{no(rms)}^2 = \int_0^{\infty} |A(j2\pi f)|^2 V_{ni}^2(f) df$$

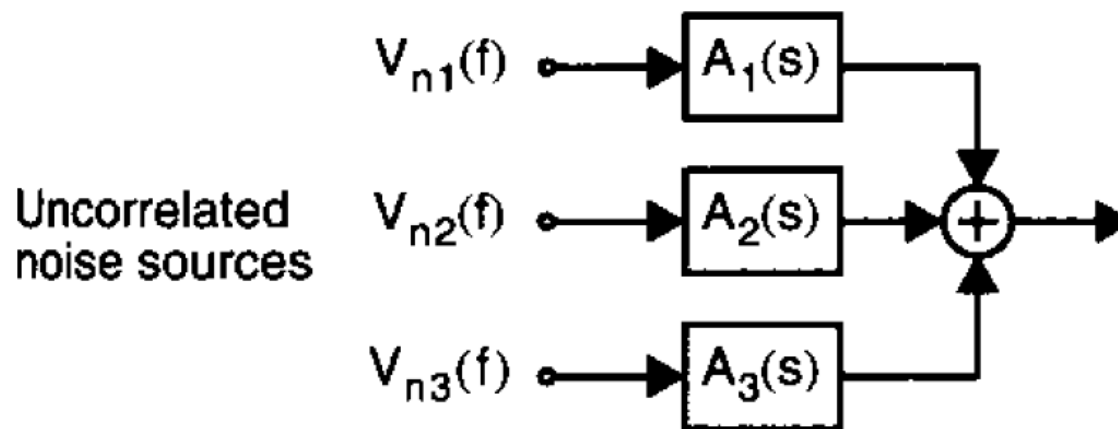



$$V_{no}^2(f) = \sum_{i=1,2,3} |A_i(j2\pi f)|^2 V_{ni}^2(f)$$

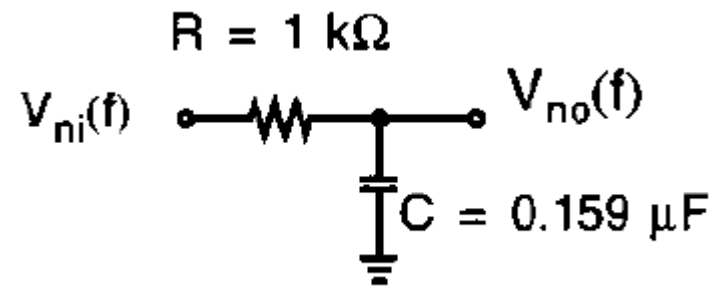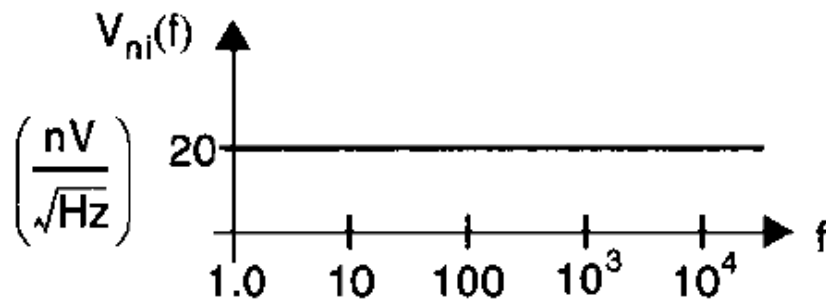Example

Assume a white noise at the input of the filter as shown bellow. What is the PSD of the output noise? What is the rms of the output noise?


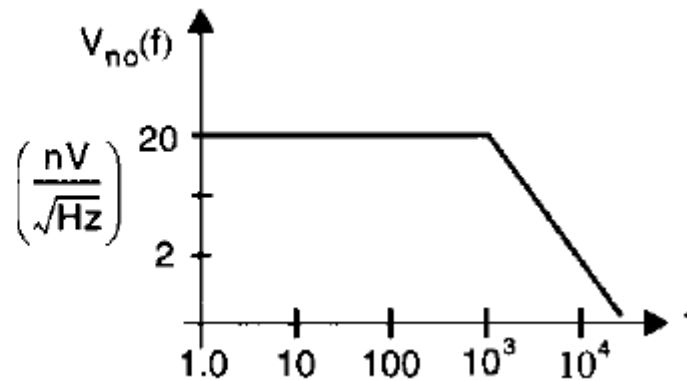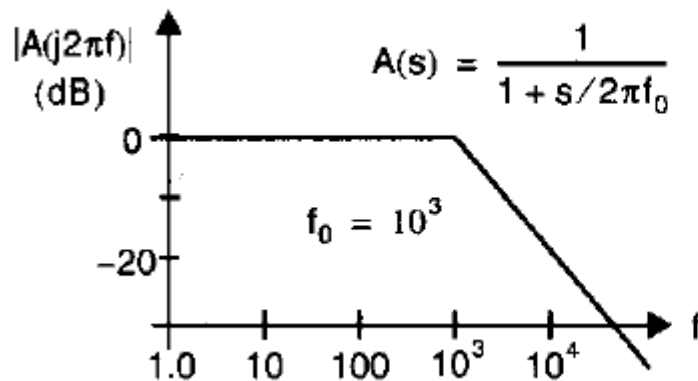
$$f_0 = \frac{1}{2\pi \times 1\text{K} \times 0.159\mu} = 1\text{kHz}$$




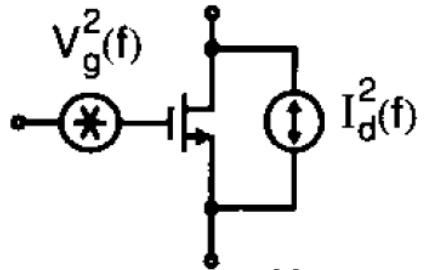
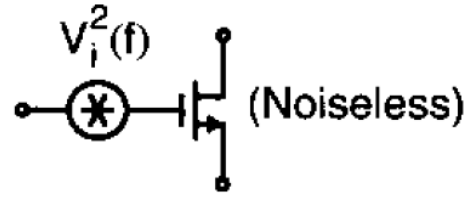
continued

$$V_{no}(f) = \frac{20 \times 10^{-9}}{\sqrt{1 + \left(\frac{f}{f_0}\right)^2}}$$

$$V_{no(rms)}^2 = \int_0^{+\infty} \frac{400 \times 10^{-18}}{1 + \left(\frac{f}{f_0}\right)^2} = 400 \times 10^{-18} f_0 \arctan \frac{f}{f_0} \Big|_0^{+\infty} = 400 \times 10^{-18} \times 1000 \times \frac{\pi}{2} = 6.28 \times 10^{-13}$$

$$V_{no(rms)} = 0.8 \mu V$$


Noise Models for Circuit Elements (MOSFETS)

<p>MOSFET</p>  <p>(Active region)</p>	 $V_g^2(f) = \frac{K}{WLC_{ox}f}$ $I_d^2(f) = 4kT\left(\frac{2}{3}\right)g_m$	 <p>(Noiseless)</p> $V_i^2(f) = 4kT\left(\frac{2}{3}\right)\frac{1}{g_m} + \frac{K}{WLC_{ox}f}$ <p>Simplified model for low and moderate frequencies</p>
--	---	---

$$K = 10^{-25} V^2 F$$

$$I_d^2(f) = 4kT\gamma g_m$$


Noise Calculation of C.S Amplifier

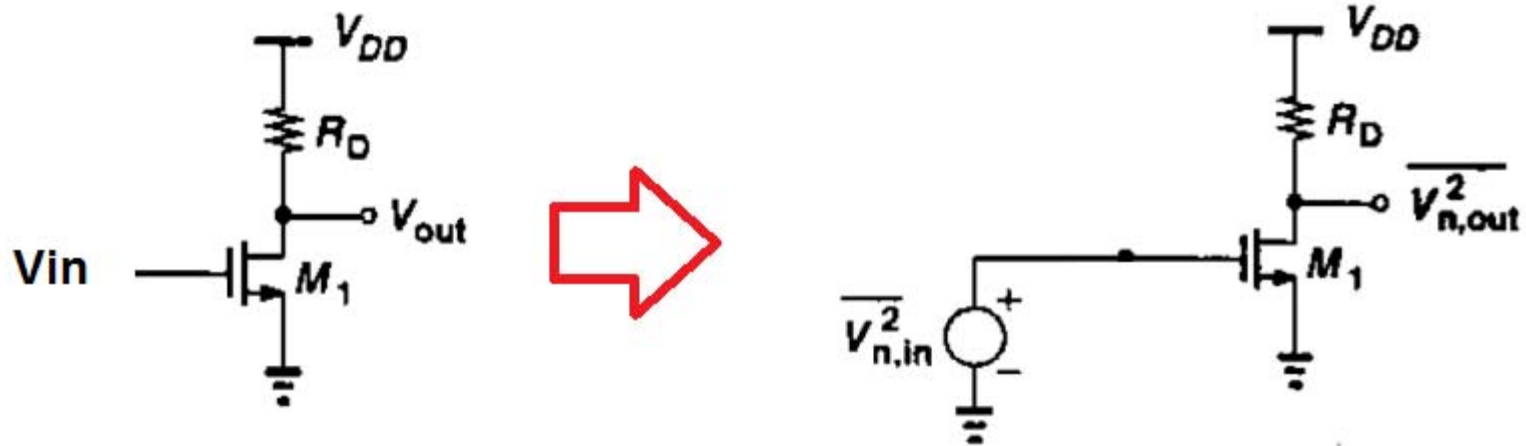

Neglecting the flicker noise, we have:

$$\overline{V_{n,in}^2} = 4kT \left(\frac{\gamma}{g_m} + \frac{1}{g_m^2 R_D} \right)$$


Noise Calculation of C.G Amplifier

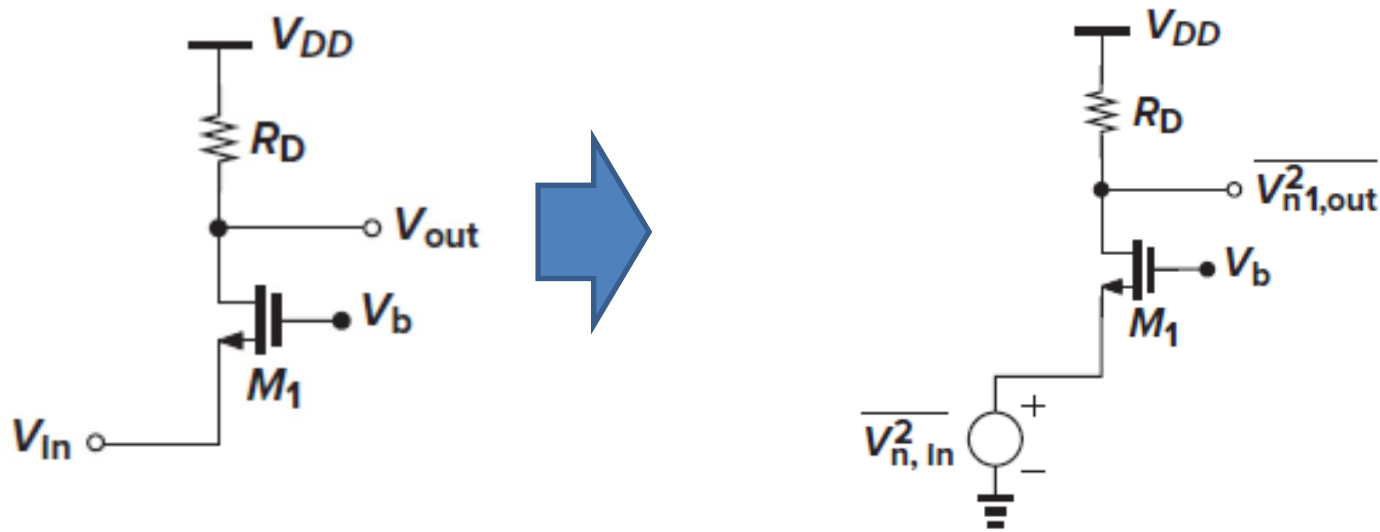

Neglecting the flicker noise and considering the body effect, we have:

$$\overline{V_{n,in}^2} = \frac{4kT(\gamma g_m + 1/R_D)}{(g_m + g_{mb})^2}$$

Noise Calculation of Cascode Amplifier

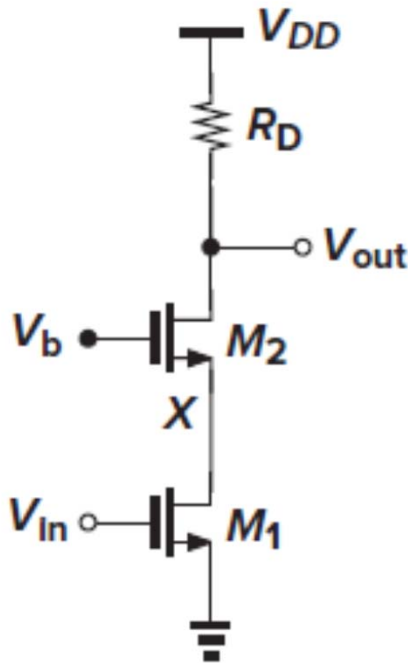


It is proven that we can neglect the noise of M2. So we have:

$$\overline{V_{n,in}^2} |_{M1, R_D} = 4kT \left(\frac{\gamma}{g_{m1}} + \frac{1}{g_{m1}^2 R_D} \right)$$

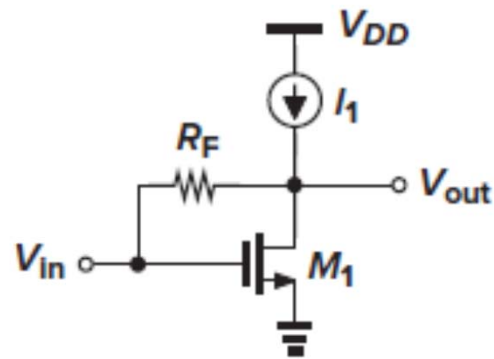
Example

Determine the input-referred noise voltage of the amplifier. Assume that I_1 is noiseless and $\lambda = 0$.



$$\overline{V_{n,in}^2} = \frac{\frac{4kT}{R_F} + 4kT\gamma g_m}{\left(g_m - \frac{1}{R_F}\right)^2}$$

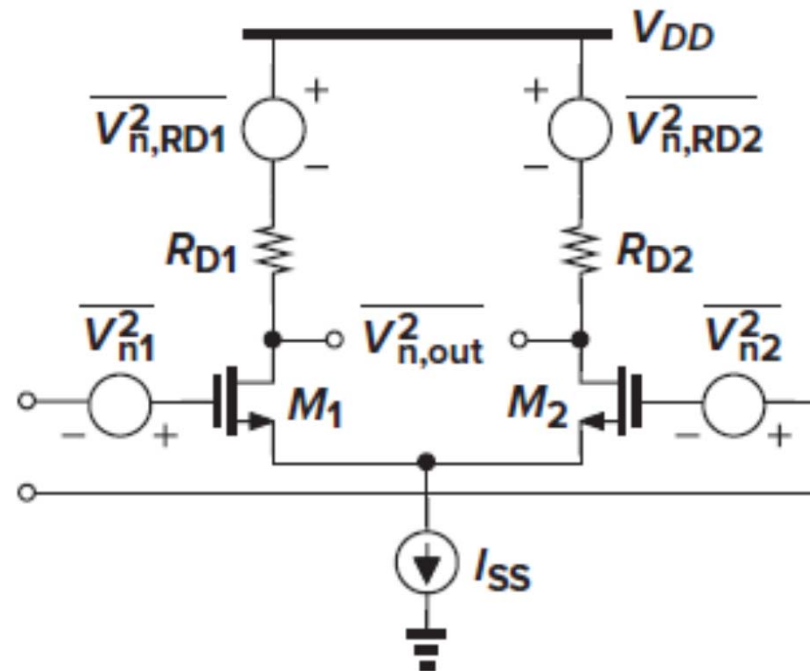
Noise Calculation of Fully Differential Amplifier



$$\overline{V_{n,in,tot}^2} = 8kT \left(\frac{\gamma}{g_m} + \frac{1}{g_m^2 R_D} \right)$$

Example


Calculate the input referred noise.

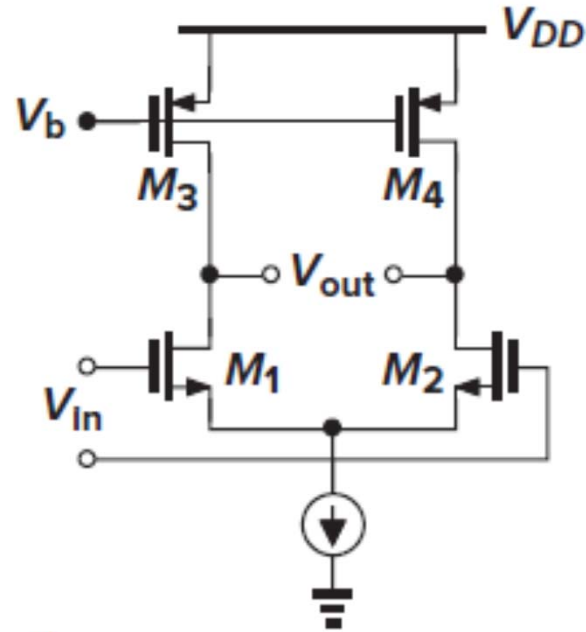

$$\overline{V_{n,in}^2} = 2\overline{V_{n1}^2} + 2\frac{g_{m3}^2}{g_{m1}^2}\overline{V_{n3}^2}$$


$$\overline{V_{n,in}^2} = 8kT\gamma \left(\frac{1}{g_{m1}} + \frac{g_{m3}}{g_{m1}^2} \right)$$

Telescopic Opamp

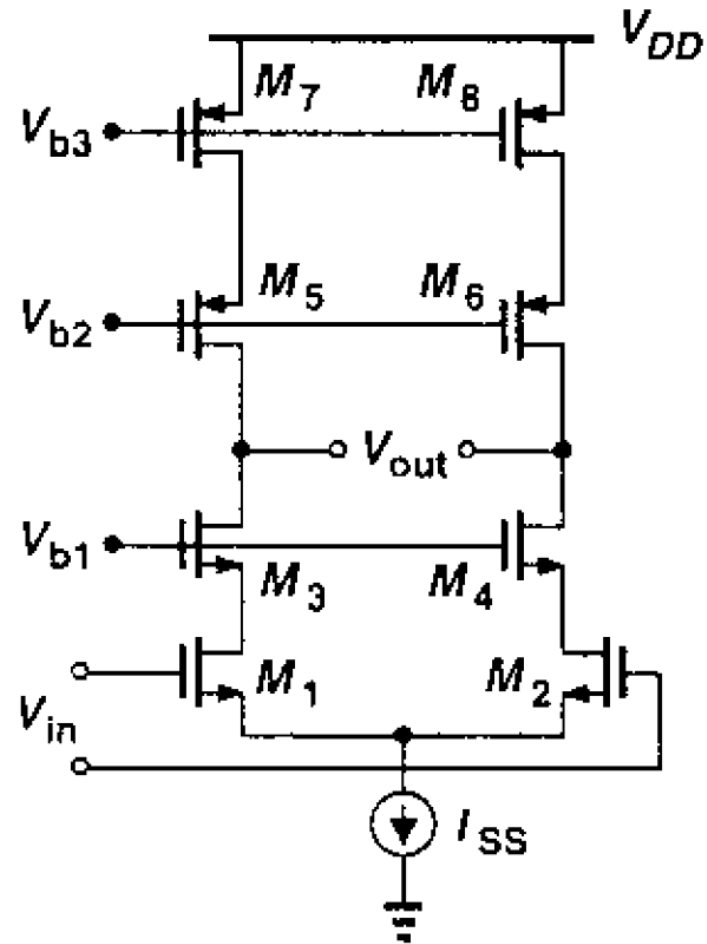

$$\overline{V_n^2} = 4kT \left(2 \frac{\gamma}{g_{m1,2}} + 2 \frac{\gamma g_{m7,8}}{g_{m1,2}^2} \right)$$


Folded-Cascode Opamp

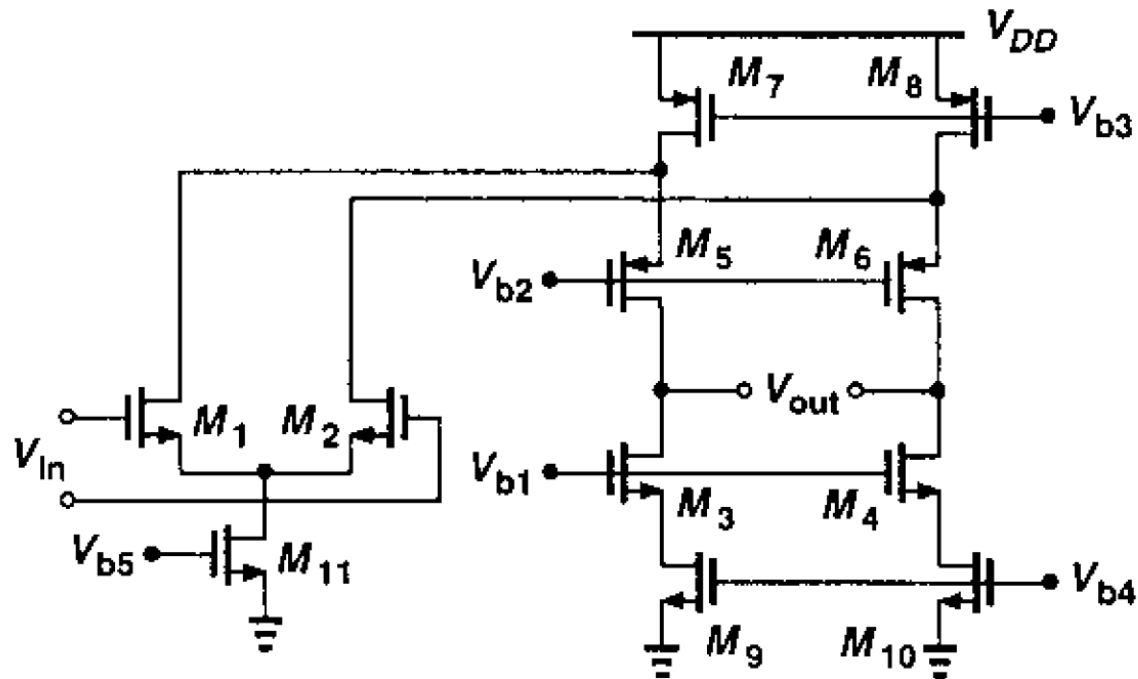

Neglecting the flicker noise, we have:

$$\overline{V_{n,tot}^2} = 8kT\gamma \frac{1}{g_{m1}^2} \left[g_{m1} + g_{m3} + \frac{g_{m5} + g_{m7}}{g_{m5}^2 (r_{O1} \parallel r_{O3})^2} \right]$$

Two-Stage Opamp

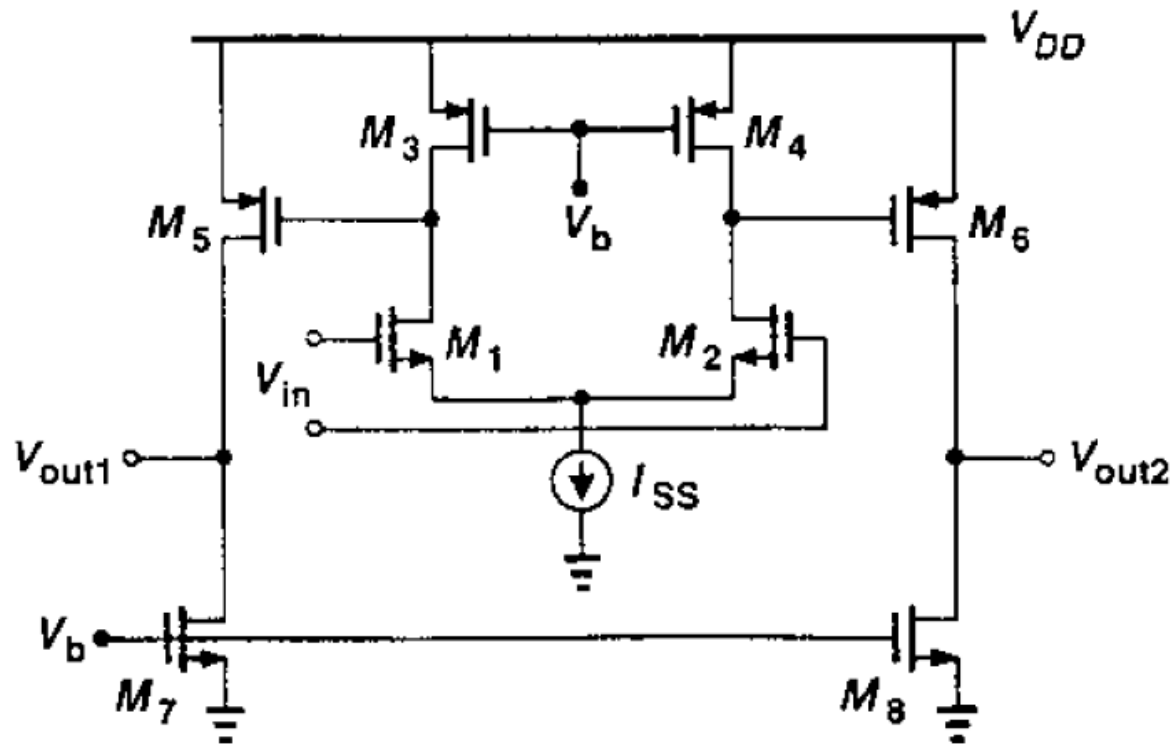

Neglecting the flicker noise, we have:

$$\overline{V_{n,tot}^2} = \frac{16kT}{3} \frac{1}{g_{m1}^2} \left[g_{m1} + g_{m3} + \frac{g_{m5} + g_{m7}}{g_{m5}^2 (r_{O1} \parallel r_{O3})^2} \right].$$