

Analog and Digital Filter Design

Second Edition

Steve Winder



Newnes is an imprint of Elsevier Science.

Copyright © 2002, Elsevier Science (USA). All rights reserved.

No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise, without the prior written permission of the publisher.

Recognizing the importance of preserving what has been written, Elsevier Science prints its books on acid-free paper whenever possible.

Elsevier Science supports the efforts of American Forests and the Global ReLeaf program in its campaign for the betterment of trees, forests, and our environment.

Library of Congress Cataloging-in-Publication Data

Winder, Steve.

Analog and digital filter design / Steve Winder.—2nd ed.

p. cm.

Rev. ed. of: Filter design. c1997.

Includes bibliographical references.

ISBN 0-7506-7547-0 (pbk. : alk. paper)

1. Electric filters—Design and construction. I. Winder, Steve. Filter design. II. Title.

TK7872.F5 W568 2002

621.3815'324—dc21

2002071430

British Library Cataloguing-in-Publication Data

A catalogue record for this book is available from the British Library.

The publisher offers special discounts on bulk orders of this book.

For information, please contact:

Manager of Special Sales

Elsevier Science

225 Wildwood Avenue

Woburn, MA 01801-2041

Tel: 781-904-2500

Fax: 781-904-2620

For information on all Newnes publications available, contact our World Wide Web home page at: <http://www.newnespress.com>

10 9 8 7 6 5 4 3 2 1

Printed in the United States of America

ANALOG AND DIGITAL FILTER DESIGN

Second Edition

STEVE WINDER



Amsterdam Boston London New York Oxford Paris San Diego San Francisco
Singapore Sydney Tokyo

6 Analog and Digital Filter Design

Chebyshev Response	58
Normalized Component Values	63
Equal Load Normalized Component Value Tables	65
Normalized Element Values for Filters with $R_S = 0$ or $R_S = \infty$	67
Inverse Chebyshev Response	69
Component Values Normalized for 1 Rad/s Stopband	71
Normalized 3dB Cutoff Frequencies and Passive Component Values	75
Cauer Response	78
Passive Cauer Filters	78
Normalized Cauer Component Values	80
The Cutoff Frequency	81
References	81
Exercises	82
CHAPTER 3 Poles and Zeros	83
Frequency and Time Domain Relationship	84
The S-Plane	84
Frequency Response and the S-Plane	85
Impulse Response and the S-Plane	88
The Laplace Transform—Converting between Time and Frequency Domains	90
First-Order Filters	90
Pole and Zero Locations	94
Butterworth Poles	94
Bessel Poles	96
Chebyshev Pole Locations	98
Inverse Chebyshev Pole and Zero Locations	109
Inverse Chebyshev Zero Locations	109
Cauer Pole and Zero Locations	117
Cauer Pole Zero Plot	121
References	122
Exercises	122
CHAPTER 4 Analog Lowpass Filters	125
Passive Filters	125
Formulae for Passive Lowpass Filter Denormalization	127
Denormalizing Passive Filters with Resonant Elements	128
Mains Filter Design	129
Active Lowpass Filters	132
First-Order Filter Section	132

CONTENTS

Preface	13
CHAPTER 1 Introduction	19
Fundamentals	19
Why Use Filters?	19
What Are Signals?	19
Decibels	21
The Transfer Function	21
Filter Terminology	22
Frequency Response	23
Phase Response	24
Analog Filters	25
The Path to Analog Filter Design	29
Digital Filters	31
Signal Processing for the Digital World	31
The "Brick Wall" Filter	34
Digital Filter Types	38
The Path to Digital Filter Design	39
Exercises	39
CHAPTER 2 Time and Frequency Response	41
Filter Requirements	41
The Time Domain	44
Analog Filter Normalization	46
Normalized Lowpass Responses	47
Bessel Response	47
Bessel Normalized Lowpass Filter Component Values	49
Butterworth Response	54
Butterworth Normalized Lowpass Component Values	55
Normalized Component Values for $R_L \gg R_S$ or $R_L \ll R_S$	56
Normalized Component Values for Source and Load Impedances within a Factor of Ten	57

Denormalization of State Variable Design	193
Cauer and Inverse Chebyshev Active Filters	194
Denormalizing Biquad Designs	196
Reference	197
Exercises	197
CHAPTER 7 Bandstop Filters	199
Passive Filters	200
Formula for Passive Bandstop Filter Denormalization	204
Passive Cauer and Inverse Chebyshev Bandstop Filters	205
Active Bandstop Filters	209
Bandstop Poles and Zeros	209
The Twin Tee Bandstop Filter	213
Denormalization of Twin Tee Notch Filter	214
Bandstop Using Multiple Feedback Bandpass Section	214
Denormalization of Bandstop Design Using MFBP Section	216
Bandstop Using Dual Amplifier Bandpass (DABP) Section	216
Denormalization of Bandstop Design Using DABP Section	217
State Variable Bandstop Filters	218
Denormalization of Bandstop State Variable Filter Section	219
Cauer and Inverse Chebyshev Active Filters	219
Denormalization of Bandstop Biquad Filter Section	221
References	221
Exercises	221
CHAPTER 8 Impedance Matching Networks	223
Power Splitters and Diplexer Filters	223
Power Splitters and Combiners	226
Designing a Diplexer	228
Impedance Matching Networks	231
Series and Parallel Circuit Relationships	232
Matching Using L, T, and PI Networks	233
Component Values for L Networks	234
Component Values for PI and T Networks	236
Bandpass Matching into a Single Reactance Load	237
Simple Networks and VSWR	238
VSWR of L Matching Network (Type A)	238
VSWR of L Matching Network (Type B)	239
VSWR of T Matching Networks	240
VSWR of PI Matching Networks	240
Exercises	241

CHAPTER 12 Transmission Lines and Printed Circuit Boards as Filters	307
Transmission Lines as Filters	308
Open-Circuit Line	309
Short-Circuit Line	310
Use of Mismatched Lines	310
Printed Circuits as Filters	317
Bandpass Filters	319
References	320
Exercises	320
CHAPTER 13 Filters for Phase-Locked Loops	321
Loop Filters	324
Higher-Order Loops	326
Analog versus Digital Phase-Locked Loop	329
Practical Digital Phase-Locked Loop	329
Phase Noise	332
Capture and Lock Range	332
Reference	334
Chapter 14 Filter Integrated Circuits	335
Continuous Time Filters	335
Integrated Circuit Filter UAF42	336
Integrated Circuit Filter MAX274	337
Integrated Circuit Filter MAX275	338
Integrated Circuit Filter MAX270/MAX271	339
Switched Capacitor Filters	339
Switched Capacitor Filter IC LT1066-1	341
Microprocessor Programmable ICs MAX260/MAX261/MAX262	342
Pin Programmable ICs MAX263/MAX264/MAX267/MAX268	343
Other Switched Capacitor Filters	344
An Application of Switched Capacitor Filters	344
Resistor Value Calculations	347
Synthesizer Filtering	350
Reference	351
CHAPTER 15 Introduction to Digital Filters	353
Analog-to-Digital Conversion	353
Under-Sampling	354
Over-Sampling	355

Sallen and Key Lowpass Filter	133
Denormalizing Sallen and Key Filter Designs	135
State Variable Lowpass Filters	136
Cauer and Inverse Chebyshev Active Filters	137
Denormalizing State Variable or Biquad Designs	138
Frequency Dependent Negative Resistance (FDNR) Filters	140
Denormalization of FDNR Filters	144
References	146
Exercises	146

CHAPTER 5 Highpass Filters	147
Passive Filters	147
Formulae for Passive Highpass Filter Denormalization	150
Highpass Filters with Transmission Zeros	152
Active Highpass Filters	154
First-Order Filter Section	156
Sallen and Key Highpass Filter	157
Using Lowpass Pole to Find Component Values	158
Using Highpass Poles to Find Component Values	158
Operational Amplifier Requirements	159
Denormalizing Sallen and Key or First-Order Designs	159
State Variable Highpass Filters	161
Cauer and Inverse Chebyshev Active Filters	162
Denormalizing State Variable or Biquad Designs	166
Gyrator Filters	167
Reference	171
Exercises	172

CHAPTER 6 Bandpass Filters	173
Lowpass to Bandpass Transformation	173
Passive Filters	174
Formula for Passive Bandpass Filter Denormalization	178
Passive Cauer and Inverse Chebyshev Bandpass Filters	180
Active Bandpass Filters	182
Bandpass Poles and Zeros	182
Bandpass Filter Midband Gain	185
Multiple Feedback Bandpass Filter	187
Denormalizing MFBP Active Filter Designs	188
Dual Amplifier Bandpass (DABP) Filter	190
Denormalizing DABP Active Filter Designs	191
State Variable Bandpass Filters	192

CHAPTER 9 Phase-Shift Networks (All-Pass Filters)	243
Phase Equalizing All-Pass Filters	243
Introduction to the Problem	243
Detailed Analysis	244
The Solution: All-Pass Networks	246
Passive First-Order Equalizers	247
Passive Second-Order Equalizers	249
Active First-Order Equalizers	253
Active Second-Order Equalizers	254
Equalization of Butterworth and Chebyshev Filters	255
Group Delay of Butterworth Filters	256
Equalization of Chebyshev Filters	263
Chebyshev Group Delay	263
Quadrature Networks and Single Sideband Generation	273
References	283
Exercises	284

CHAPTER 10 Selecting Components for Analog Filters	285
Capacitors	285
Inductors	289
Resistors	291
The Printed Circuit Board (PCB)	292
Surface-Mount PCBs	293
Assembly and Test	294
Operational Amplifiers	295
Measurements on Filters	296
Reference	297
Exercises	297

CHAPTER 11 Filter Design Software	299
Filter Design Programs	299
Supplied Software	299
Active_F	300
Filter2	301
Ellipse	302
Diplexer	303
Match2A	304
References	305

Denormalization	400
Lowpass Filter Design	401
Highpass Frequency Scaling	403
Bandpass Frequency Scaling	405
Bandstop Frequency Scaling	406
IIR Filter Stability	407
Reference	408
Appendix	
Design Equations	409
Bessel Transfer Function	409
Butterworth Filter Attenuation	412
Butterworth Transfer Function	412
Butterworth Phase	413
Nonstandard Butterworth Passband	414
Normalized Component Values for Butterworth Filter with RL >> RS or RL << RS	415
Normalized Component Values for Butterworth Filter; Source and Load Impedances within a Factor of Ten	415
Chebyshev Filter Response	416
Equations to Find Chebyshev Element Values	417
Chebyshev with Zero or Infinite Impedance Load	417
Chebyshev Filter with Source and Load Impedances within a Factor of Ten	418
Load Impedance for Even-Order Chebyshev Filters	419
Inverse Chebyshev Filter Equations	419
Elliptic or Cauer Filter Equations	421
Noise Bandwidth	422
Butterworth Noise Bandwidth	423
Chebyshev Noise Bandwidth	424
Pole and Zero Location Equations	426
Butterworth Pole Locations	426
Chebyshev Pole Locations	427
Inverse Chebyshev Pole and Zero Locations	429
Inverse Chebyshev Zeros	431
Cauer Pole and Zero Locations	432
Scaling Pole and Zero Locations	434
Digital Filter Equations	435
Finding FIR Filter Zero Coefficient Using L'Hopital's Rule	435
Appendix References	436
Bibliography	437
Answers	439
Index	447

Decimation	355
Interpolation	356
Digital Filtering	356
Digital Lowpass Filters	357
Truncation (Applied to FIR Filters)	361
Transforming the Lowpass Response	362
Bandpass FIR Filter	363
Highpass FIR Filter	363
Bandstop FIR Filter	363
DSP Implementation of an FIR Filter	364
Introduction to the Infinite Response Filter	365
DSP Mathematics	366
Binary and Hexadecimal	367
Two's Complement	367
Adding Two's Complement Numbers	369
Subtracting Two's Complement Numbers	370
Multiplication	370
Division	373
Signal Handling	373
So, Why Use a Digital Filter?	375
Reference	375
Exercises	375
CHAPTER 16	
Digital FIR Filter Design	377
Frequency versus Time-Domain Responses	380
Denormalized Lowpass Response Coefficients	380
Denormalized Highpass Response Coefficients	381
Denormalized Bandpass Response Coefficients	381
Denormalized Bandstop Response Coefficients	382
Windows	384
Fourier Method of FIR Filter Design	384
Window Types	385
Summary of Fixed FIR Windows	390
Number of Taps Needed by Fixed Window Functions	390
FIR Filter Design Using the Remez Exchange Algorithm	392
Number of Taps Needed by Variable Window Functions	392
FIR Filter Coefficient Calculation	393
A Data-Sampling Rate-Changer	394
References	394
CHAPTER 17	
IIR Filter Design	395
Bilinear Transformation	397
Pre-Warping	400