

First U.S. Edition, 1960
 First Wiley Eastern Reprint, April 1976
 Second Wiley Eastern Reprint, August 1980
 Third Wiley Eastern Reprint, March 1982
 Fourth Wiley Eastern Reprint, January 1983
 Fifth Wiley Eastern Reprint, April 1984

Authorized reprint of the edition published by
 John Wiley & Sons, Inc., New York, Chichester, Brisbane and Toronto
 Copyright © 1960, John Wiley & Sons, Inc.
 All rights reserved. No part of this book may be reproduced
 in any form without the written permission of Wiley-Interscience, Inc.

Sales Area: India, Bangladesh and Sri Lanka

10 9 8 7 6 5

Price: Rs. 35.00

ISBN 0 85226 891 2

Published by Mohinder Singh Sejwal for Wiley Eastern Limited
 4835/24 Ansari Road, Daryaganj, New Delhi 110002 and printed by
 Pramodh Kapur at Rajbandhu Industrial Co., New Delhi 110064
 Printed in India

m.e. van valkenburg

introduction to modern network synthesis

CONTENTS	
x	4.3 The Computation of Residues 93
	4.4 Even and Odd Functions 97
	4.5 Sturm's Theorem 100
	4.6 An Alternative Test for Positive Real Character 104 Problems 108
5	Driving-Point Synthesis with LC Elements 113
	5.1 Elementary Synthesis Operations 113
	5.2 LC Network Synthesis 121 Problems 137
6	RC and RL Networks 140
	6.1 Properties of RC Network Functions 140
	6.2 Foster Form of RC Networks 145
	6.3 Foster Form of RL Networks 148
	6.4 The Cauer Form of RC and RL Net- works 150 Problems 157
7	RLC One Terminal-Pairs 161
	7.1 Minimum Positive Real Functions 161
	7.2 Brune's Method of RLC Synthesis 164
	7.3 The Method of Bott and Duffin 173
	7.4 Actual Realization Difficulties 180 Problems 182
8	Parts of Network Functions 189
	8.1 Properties of Ev $Z(s)$ when $Z(s)$ is Positive Real 189
	8.2 The Bruns-Gewertz Method 192
	8.3 Bode's Method 196
	8.4 From Magnitude to Phase 197
	8.5 From Phase to Magnitude 201 Problems 205
9	Approximation I 209
	9.1 Introduction 209
	9.2 A Method of Cut and Try 210
	9.3 Break-point Approximation: General Con- siderations 213
	9.4 Semilog Plots of Network Function Fac- tors 217
	9.5 Combinations of Factors: Analysis 227
	9.6 Approximation by Straight-Line Asymp- totes 228

Contents

1	Introduction	1
	1.1 Identification of the Network Synthesis Problem 1	
	1.2 Network Equilibrium Equations 6	
	1.3 Network Functions and the Models They Describe 11	
	1.4 Poles and Zeros of Network Functions 16	
	1.5 Complex Frequency 19 Problems 23	
2	Network Analysis	27
	2.1 Network Functions for Series-Parallel Structures 27	
	2.2 Network Functions for General Structures 31	
	2.3 The Open-Circuit Impedance and Short-Cir- cuit Admittance Functions 36	
	2.4 Transfer Functions in Terms of the y and z Functions 43	
	2.5 Scaling Network Functions 48 Problems 54	
3	Positive Real Functions	62
	3.1 Driving-Point Functions 62	
	3.2 Brune's Positive Real Functions 67	
	3.3 Properties of Positive Real Functions 73 Problems 79	
4	Testing Driving-Point Functions	82
	4.1 An Application of the Maximum Modulus Theorem 82	
	4.2 Properties of Hurwitz Polynomials 85	

14.3	Properties of Z_{11} for the Lossless Terminated Network	411
14.4	Lossless Terminated Network Synthesis Problems	415 420
15	Double-Terminated Networks	424
15.1	Properties of Double-Terminated Coupling Networks	424
15.2	The Darlington Procedure	428
15.3	RC Grounded Coupling Networks Problems	437 445
16	The Image Parameter Method	447
16.1	The Image Parameters	447
16.2	Image Parameters for the Symmetrical Lattice	451
16.3	More Complicated Lattices	458
16.4	Design of Filters with Resistive Terminations	464
16.5	The Ladder Equivalent of the Lattice Filter	470
16.6	The Design of Composite Filters	472
16.7	Frequency Transformations Problems	479 487
	Selected Bibliography	491
	Index	493

9.7	Approximation from Phase Plots	233
9.8	The Potential Analog Problems	234 239
10	Two Terminal-Pair Synthesis by Ladder Development	248
10.1	Some properties of $-y_{11}$ and z_{11}	250
10.2	The LC Ladder Development	260
10.3	Other Considerations	270
10.4	The RC Ladder Development Problems	276 289
11	Series and Parallel Realizations	297
11.1	The Ideal Transformer	297
11.2	Further Restrictions on z_{11}	305
11.3	The Residue Condition and Related Topics	308
11.4	Cauer's Partial Fraction Network Realization	313
11.5	RC Synthesis with Parallel Ladders (Guillemin's Method) Problems	322 330
12	Symmetrical Lattice and Constant-Resistance Networks	337
12.1	Impedance Equations for the Lattice	337
12.2	Several Synthesis Procedures for the Unloaded Lattice	340
12.3	The Constant-Resistance Symmetrical Lattice	346
12.4	Lattice Decomposition	352
12.5	Bartlett's Bisection Theorem	356
12.6	Constant-Resistance Bridged-T and Ladder Networks Problems	358 368
13	Approximation II	373
13.1	The Butterworth Form of Response	373
13.2	Chebyshev Polynomials in Approximation	376
13.3	The Maximally Flat Delay Form of Response	386
13.4	Frequency Transformations Problems	392 393
14	Resistively Terminated Networks	397
14.1	Elementary Synthesis Procedures	399
14.2	Darlington's Driving-Point Synthesis Method	402